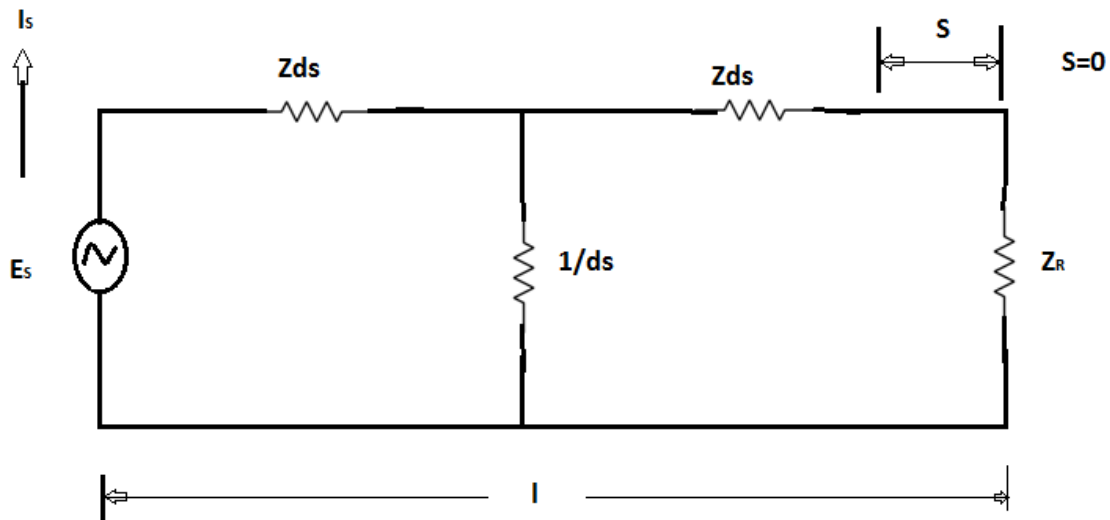


**PHYSICAL SIGNIFICANCE OF TRANSMISSION LINE (or) INFINITE LINE (or) THE TWO STANDARD FORM FOR INPUT IMPEDANCE OF THE TRANSMISSION LINE TERMINATED BY AN IMPEDANCE**

$Z_R$

Equation for the current and voltage may be written for the sending end current ' $I_s$ ' of a line of length ' $l$ ' is,



The sending current equation is given by,

$$I_s = I_R \cosh \sqrt{ZY} \cdot l + \frac{E_R}{Z_0} \sinh \sqrt{ZY} \cdot l \quad [E_R = I_R Z_R]$$

Sub  $E_R$  value in above equ,

$$I_s = I_R \cosh \sqrt{ZY} \cdot l + \frac{I_R Z_R}{Z_0} \sinh \sqrt{ZY} \cdot l$$

$$I_s = I_R \left[ \cosh \sqrt{ZY} \cdot l + \frac{Z_R}{Z_0} \sinh \sqrt{ZY} \cdot l \right] \quad \dots\dots(1)$$

The sending voltage equation is given by,

$$E_s = E_R \cosh \sqrt{ZY} \cdot l + I_R Z_0 \sinh \sqrt{ZY} \cdot l$$

$$[E_R = I_R Z_R]$$

$$[I_R = \frac{E_R}{Z_R}]$$

Sub  $I_R$  value in above equ,

$$E_s = E_R \cosh \sqrt{ZY} \cdot l + \frac{E_R Z_0}{Z_R} \sinh \sqrt{ZY} \cdot l$$

$$E_S = E_R \left[ \cosh \sqrt{ZY} \cdot l + \frac{Z_0}{Z_R} \sinh \sqrt{ZY} \cdot l \right] \quad \dots\dots(2)$$

Since, We know that,

Propagation Constant  $\gamma = \sqrt{ZY}$

Characteristic Impedance  $Z_0 = \sqrt{\frac{Z}{Y}}$

Sub  $\gamma$  value in equ (1) and (2),

From equ (1),

$$I_S = I_R \left[ \cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l \right] \quad \dots\dots(3)$$

From equ (2),

$$E_S = E_R \left[ \cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right] \quad \dots\dots(4)$$

Input Impedance  $Z_S = \frac{E_S}{I_S}$  [E = IZ]

$$Z_S = \frac{E_R \left[ \cosh \gamma l + \frac{Z_0}{Z_R} \sinh \gamma l \right]}{I_R \left[ \cosh \gamma l + \frac{Z_R}{Z_0} \sinh \gamma l \right]}$$

$$Z_S = Z_R \left[ \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right]$$

$$E_R = I_R Z_R$$

$$Z_R = \frac{E_R}{I_R}$$

$$Z_S = Z_R \left[ \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right] \times \frac{Z_0}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l}$$

$$Z_S = Z_0 \left[ \frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right] \quad \dots\dots(5)$$

This is the first standard form of input impedance of the transmission line.

$$\text{Cosh} \theta = \frac{e^\theta + e^{-\theta}}{2}$$

$$\text{Sinh} \theta = \frac{e^\theta - e^{-\theta}}{2}$$

Sub the above formula in equ (5),

$$Z_S = Z_0 \left[ \frac{Z_R \left( \frac{e^{\gamma l} + e^{-\gamma l}}{2} \right) + Z_0 \left( \frac{e^{\gamma l} - e^{-\gamma l}}{2} \right)}{Z_0 \left( \frac{e^{\gamma l} + e^{-\gamma l}}{2} \right) + Z_R \left( \frac{e^{\gamma l} - e^{-\gamma l}}{2} \right)} \right]$$

$$Z_S = \frac{2Z_0}{2} \left[ \frac{Z_R(e^{\gamma l} + e^{-\gamma l}) + Z_0(e^{\gamma l} - e^{-\gamma l})}{Z_0(e^{\gamma l} + e^{-\gamma l}) + Z_R(e^{\gamma l} - e^{-\gamma l})} \right]$$

$$Z_S = Z_0 \left[ \frac{Z_R e^{\gamma l} + Z_R e^{-\gamma l} + Z_0 e^{\gamma l} - Z_0 e^{-\gamma l}}{Z_0 e^{\gamma l} + Z_0 e^{-\gamma l} + Z_R e^{\gamma l} - Z_R e^{-\gamma l}} \right]$$

$$Z_S = Z_0 \left[ \frac{e^{\gamma l} [Z_R + Z_0] + e^{-\gamma l} [Z_R - Z_0]}{e^{\gamma l} [Z_R + Z_0] - e^{-\gamma l} [Z_R - Z_0]} \right]$$

$$Z_S = Z_0 \frac{[Z_R + Z_0]}{[Z_R + Z_0]} \left[ \frac{e^{\gamma l} + e^{-\gamma l} \left[ \frac{Z_R - Z_0}{Z_R + Z_0} \right]}{e^{\gamma l} - e^{-\gamma l} \left[ \frac{Z_R - Z_0}{Z_R + Z_0} \right]} \right]$$

$$Z_S = Z_0 \left[ \frac{e^{\gamma l} + e^{-\gamma l} \left[ \frac{Z_R - Z_0}{Z_R + Z_0} \right]}{e^{\gamma l} - e^{-\gamma l} \left[ \frac{Z_R - Z_0}{Z_R + Z_0} \right]} \right] \dots\dots\dots(6)$$

This is the second standard form of input impedance of the transmission line.

