



ROHINI

COLLEGE OF ENGINEERING AND TECHNOLOGY

Approved by AICTE and affiliated to Anna University Chennai (An ISO Certified Institution)

Accredited by NAAC with A+ Grade

DEPARTMENT OF BIOMEDICAL ENGINEERING

BM3491 Biomedical Instrumentation


UNIT-IV MEASUREMENT OF BIO SIGNALS

4.3 Pressure amplifiers - systolic, diastolic, mean detector circuit.


- The pressure amplifier produces an analog waveform with a **peak amplitude** representing the **systolic pressure**, and a minimum, or 'valley,' that represents the **diastolic pressure**.
- Additional circuitry is required that recognizes** these points, and from them produce a steady DC voltage or current that can be used to drive a display meter.
- The pressure amplifier used for bedside applications is less complex and thus is less flexible and often somewhat less accurate.
- While its simplicity allows less well-trained personnel to successfully operate the instrument, it is more accurate than most indirect methods.
- In ICU/CCU/OR settings, the operator is usually a physician, nurse, or monitoring technician who has duties other than equipment operation and has limited time to calibrate pressure equipment.
- For these busy people, it is a valid trade-off to sacrifice a small amount of accuracy for simpler operation.
- In applications where superior accuracy is needed, a mercury or aneroid manometer is used to calibrate pressure equipment every time it is used.
- clinical pressure monitors have an internal calibration signal that is used for day-to-day operation, and it is checked periodically.

Systolic, Diastolic, and Mean Detector Circuits:

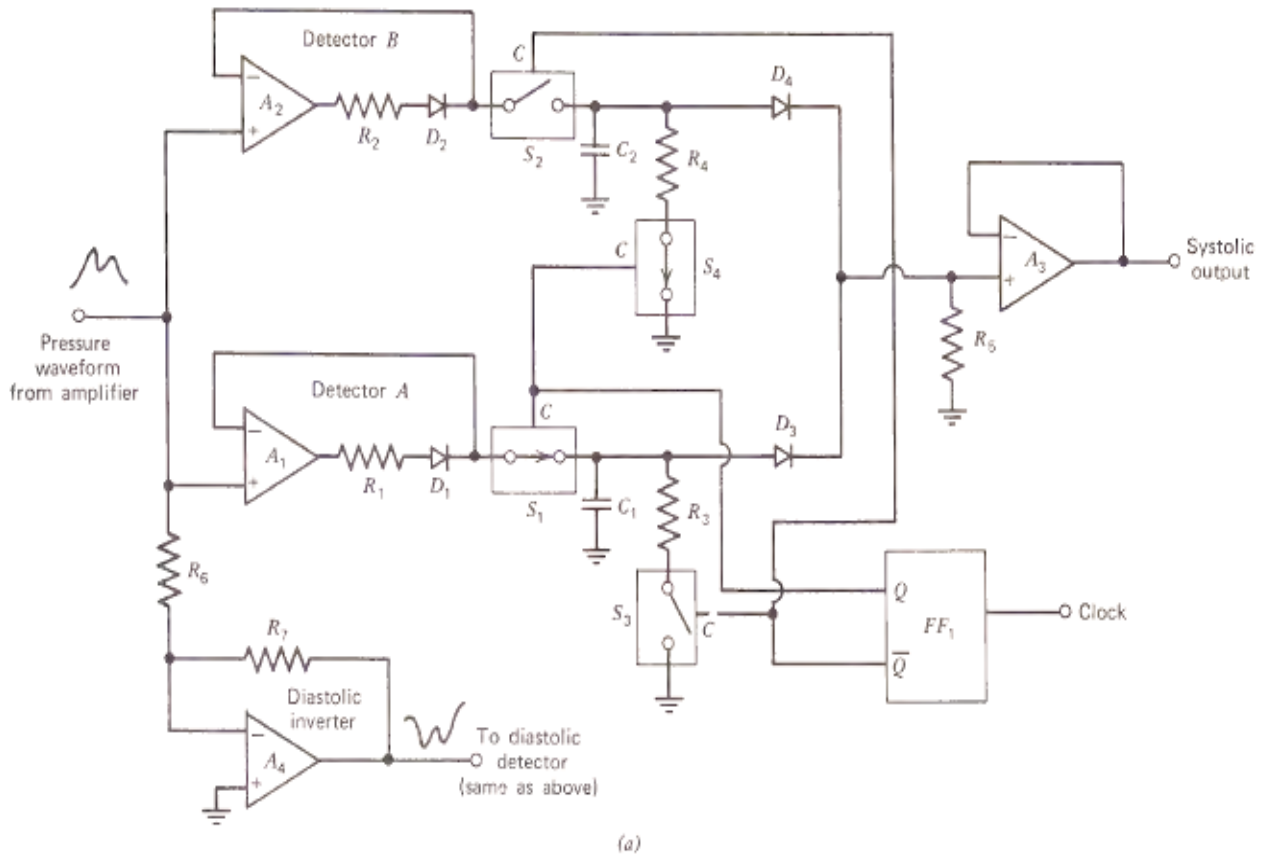- ❑ The partial schematic of a pressure detector is shown in Figure (a), while the timing diagram is shown in Figure (b).
- ❑ Amplifiers A_1 through A_3 ; are **operational amplifiers**.
- ❑ Switches S_1 through S_4 are CMOS **electronic switches**.
- ❑ Note that the operational amplifiers **may be integrated types, as shown, or may be constructed of discrete components** in older models.



(a) Systolic detector circuit

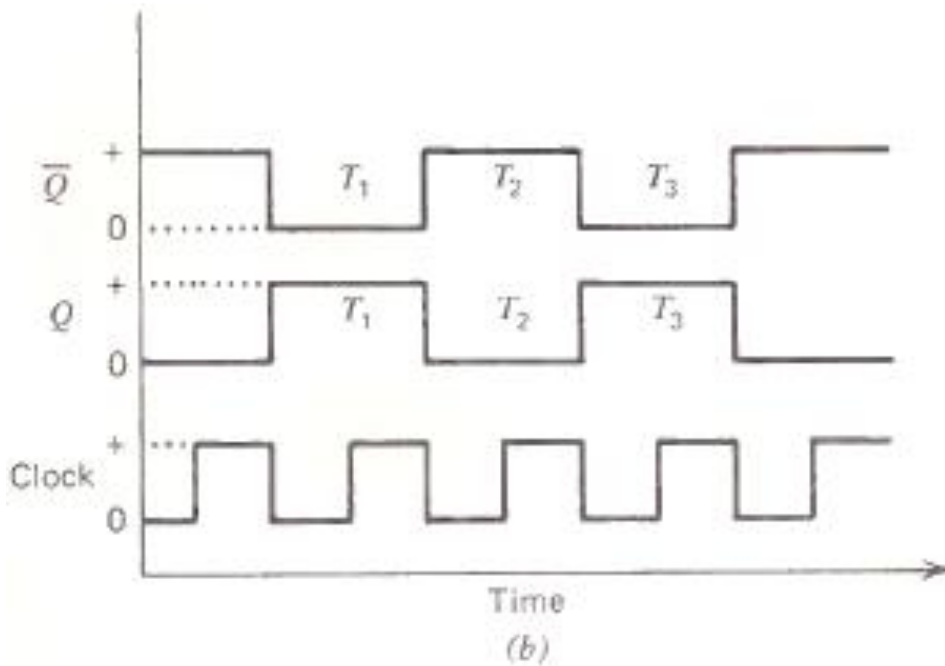

(b) Timing diagram

- ❑ This circuit operates from a two-phase clock created by flip-flop FF₁. The Q and not-Q (\bar{Q}) outputs are complementary, so one will be high when the other is low.
- ❑ Switches S₁ and S₄ are turned on when the Q is high, and switches S₂ and S₃ are turned on when the \bar{Q} is high.
- ❑ The analog waveform from the output of the pressure amplifier is applied simultaneously (i.e., in parallel) to the inputs of A₁ and A₂. The waveform, therefore, appears simultaneously at the outputs of A₁; and A₂.
- ❑ During period T₁, (Figure b), the Q output of FF₁ is high, so switches S₁ and S₄ are closed. When S₄ is closed, capacitor C₂ is discharged, so it has no effect on the output. Closing switch S₁ allows the signal appearing at the output of A₁ to charge capacitor C₁ to the peak voltage, representing the **systolic pressure**.
- ❑ The voltage across capacitor C₁ forward biases diode D₃, which then conducts and applies the voltage to the input of amplifier A₃. The output of amplifier A₃ goes to the systolic output meter.
- ❑ The situation reverses during the time T₂: The not-Q of FF₁ becomes high and the Q is low. This turns on switches S₂ and S₃ and turns off S₁ and S₄. Closing S₂ causes capacitor C₂ to rapidly charge to the peak

voltage of the input signal. This will occur within less than a second in most cases.


- ❑ Switch S₃; closes to allow capacitor C₁ to discharge slowly through resistor R₃. The charge on C₂ will reach peak before any appreciable decay of the C₁ charge takes place. In some models each charge switch is operated directly from FF₁, while the discharge switch is operated by the same signal after it has passed through an R-C network delay line. This network insures that one capacitor is fully charged before the other begins to decay.
- ❑ The voltage at the output of Figure (a) represents the peak of the waveform, which corresponds to the systolic pressure. The same circuit may be used to detect the diastolic voltage by inverting the waveform so that the diastolic feature becomes the peak.
- ❑ **The mean arterial pressure** is found by taking the time average (i.e., integrating) the pressure waveform (Figure). An example of a simple mean value integrator is shown in Figure 6-165. Most pressure monitors use a simple R-C integrator with buffering amplifiers rather than regular operational amplifier integrators.
- ❑ The mean reading may create a bit of con-fusion to some medical and nursing personnel, who were taught the functional definition of mean arterial pressure, which is


$$\bar{P} = P_d + \frac{P_s - P_d}{3}$$


where \bar{P} is the mean arterial pressure in mm Hg

P_d is the diastolic pressure in mm Hg

P_s is the systolic pressure in mm Hg

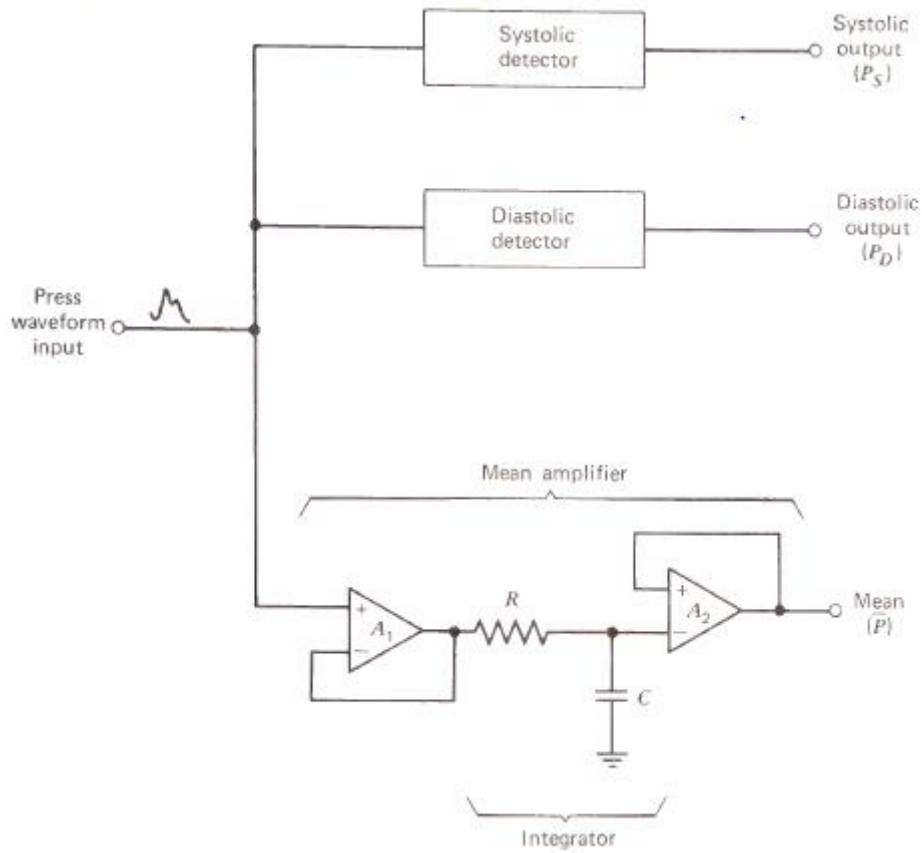

Mean arterial pressure detector.

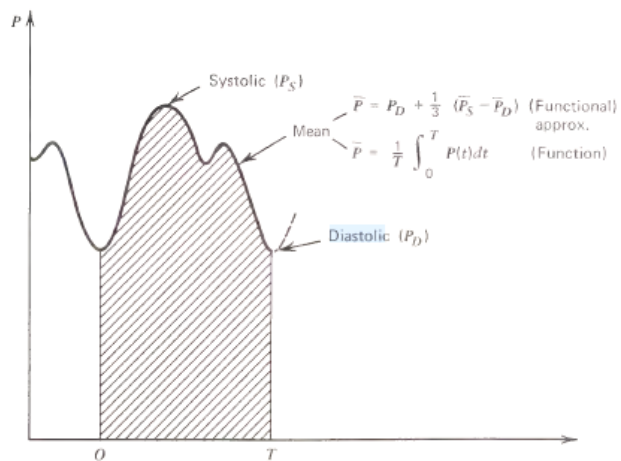

Graphical and mathematical meaning of (b) "mean arterial pressure."
