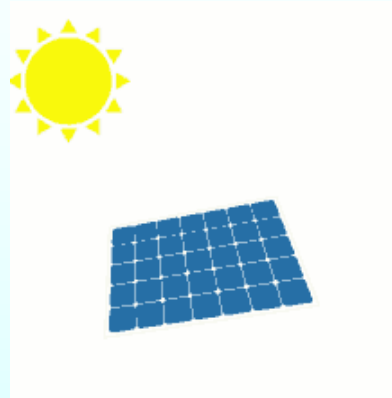


# DC – Transient Response of RLC Series Circuit




**Mr.Ebbie Selva Kumar C**

Assistant Professor/ EEE

*Rohini College of Engineering and Technology*



## SERIES RESONANCE

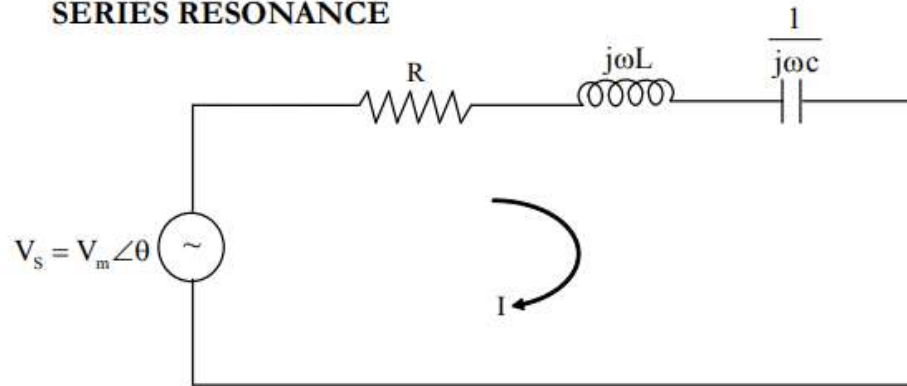

*Fig. 5.1 Series RLC Circuit*

Resonance occurring in a series circuit is known as series resonance. Consider a series RLC circuit as shown in figure 3.1.

The impedance of the given circuit is,

$$\begin{aligned} Z &= \frac{V_s}{I} = R + j\omega L + \frac{1}{j\omega C} \\ &= R + j\left(\omega L - \frac{1}{\omega C}\right) \end{aligned}$$

Resonance results when imaginary part is zero.

$$\therefore \omega L - \frac{1}{\omega C} = 0$$



Value of  $\omega$  that satisfies this condition is called resonant frequency, “ $\omega_0$ ”.

$$\therefore \omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

Since,  $\omega_0 = 2\pi f_0$ , we can write

$$2\pi f_0 = \frac{1}{\sqrt{LC}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz.}$$

where,  $f_0 \rightarrow$  resonant frequency in Hz (or) rad/sec.

### **Variance of Impedance with Frequency for RLC Series Circuit :**

The circuit impedance is,  $Z = R + j(X_L - X_C) = R + jX$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$


At resonant frequency as  $X = 0$ , the impedance  $|Z|$  is equal to  $R$ . At all other frequencies, reactance value is not equal to zero. Hence  $|Z|$  is greater than  $R$ .

i.e., At  $f = f_0$ ,  $|Z| = R$


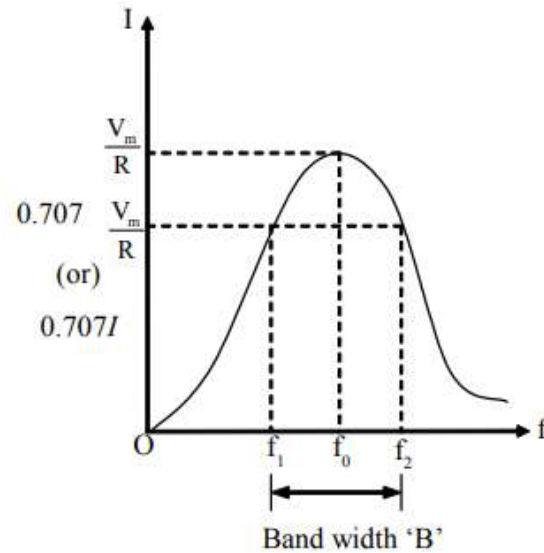
## BAND WIDTH - HALF POWER FREQUENCIES :

The current Vs frequency curve of a RLC series circuit is symmetrical about the resonant frequency. At  $f_0$ , the current is maximum and is given by  $\frac{V_m}{R}$ . There will be two frequencies  $f_1$ ,  $f_2$  on either side of the resonant frequency  $f_0$  at which the power is half the power at resonance. (Refer fig.5.7). Hence they are called half power frequencies.



$$\therefore f_1 = f_0 - \frac{R}{4\pi L}$$

$$\therefore f_2 = f_0 + \frac{R}{4\pi L}$$

*Fig. 5.7 Current Vs frequency curve of a RLC series circuit*

$f_1 \rightarrow$  Lower half power frequency

$f_2 \rightarrow$  Upper half power frequency



### Bandwidth :

It is defined as the band of frequency between the two half power frequencies  $f_2$  &  $f_1$ .

$$\text{Bandwidth} = f_2 - f_1 = f_0 + \frac{R}{4\pi L} - \left( f_0 - \frac{R}{4\pi L} \right)$$

$$B W = \frac{2R}{4\pi L} = \frac{R}{2\pi L}$$

The Q-factor relates the maximum or peak energy stored to the energy dissipated in the circuit per cycle of oscillation.

$$Q = 2\pi \frac{\text{Peak energy stored in the circuit}}{\text{Energy dissipated by the circuit in one period at resonance}}$$

(or)

It is the measure of energy storage property in relation to its energy dissipation property.

$$\therefore Q = 2\pi \frac{\frac{1}{2} LI^2}{\frac{1}{2} I^2 R \left( \frac{1}{f_0} \right)} = \frac{2\pi f_0 L}{R}$$

$$\text{(or)} \quad Q = \frac{\omega_0 L}{R} \quad \text{-----(6)}$$

The quality factor is also given by,  $Q = \frac{f_0}{f_2 - f_1} = \frac{f_0}{BW}$

$$= \frac{f_0}{R/2\pi L} = \frac{2\pi f_0 L}{R} = \frac{\omega_0 L}{R}$$

$$\text{Selectivity} = \frac{f_0}{BW} = \frac{f_0}{f_2 - f_1}$$



**Thank You**

