

1. Superposition Theorem

Statement: In linear, active, bilateral network current flowing through any component is the algebraic sum of currents due to individual sources taking one at a time, replacing remaining sources with their internal impedances.

Proof: Consider the network shown in fig(1), in which Z_1, Z_2, Z_3 are impedances and V_1 and V_2 are applied sources.

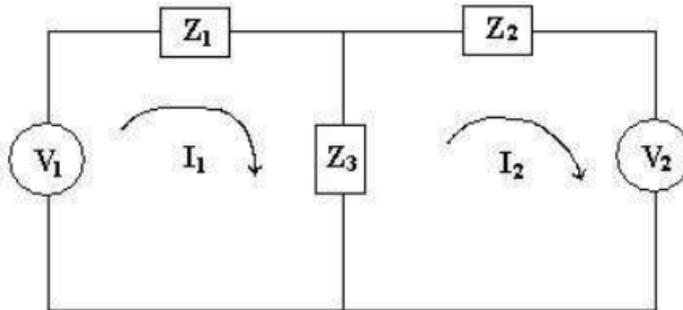


Fig. 1

Let I_1, I_2 be the mesh currents, writing mesh equations for fig(1).

$$(Z_1 + Z_3) I_1 - Z_3 I_2 = V_1 \quad \text{----- (1)}$$

$$-Z_3 I_1 + (Z_2 + Z_3) I_2 = V_2 \quad \text{-----(2)}$$

Now keeping the source V_1 and replacing V_2 with its internal impedance. The modified ckt is shown in fig(2).

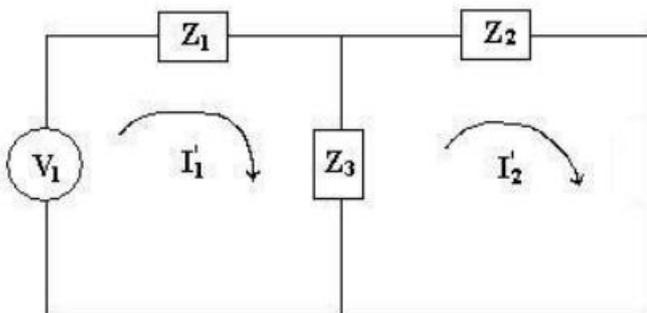


Fig. 2

Let I_1', I_2' be mesh currents, mesh equations for fig(2)

$$(Z_1 + Z_3)I_1' - Z_3I_2' = V_1 \quad \text{----- (3)}$$

$$-Z_3 I_1' + (Z_2 + Z_3) I_2' = 0 \quad \text{-----(4)}$$

Consider the V_2 and replace V_1 with its internal impedance as shown in fig(3)

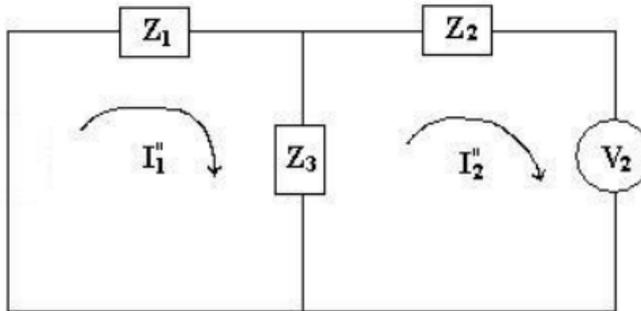


Fig. 3

Let I_1'', I_2'' be the mesh currents , mesh equations for fig(3),

$$(Z_1 + Z_3) I_1'' - Z_3 I_2'' = 0 \quad \text{----- (5)}$$

$$-Z_3 I_1'' + (Z_2 + Z_3) I_2'' = V_2 \quad \text{-----(6)}$$

Adding eq(3) & eq(5) and eq(4) & eq(6), we get

$$(Z_1 + Z_3)(I_1' + I_1'') - Z_3(I_2' + I_2'') = V_1 \quad \text{-----(7)}$$

$$-Z_3(I_1' + I_1'') + (Z_2 + Z_3)(I_2' + I_2'') = V_2 \quad \text{-----(8)}$$

Comparing eq(1) & eq(7) and eq(2) & eq(8), we have

$$I_1 = (I_1' + I_1'')$$


$$I_2 = (I_2' + I_2'')$$

It is clear from the above equations that the current flowing through any component is algebraic sum of currents due to individual sources taking on at a time. Hence

Superposition theorem is proved.

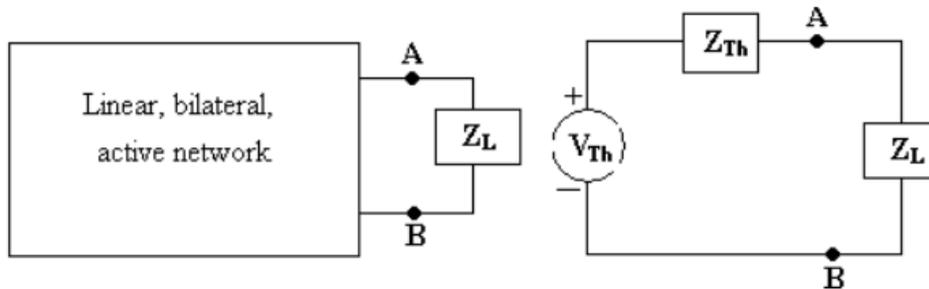2. THEVENIN'S THEOREM

Statement: Any linear, bilateral, active network connected between two terminal A, B can be replaced by a voltage source supplying voltage V_{TH} in series with an impedance Z_{TH} . Where V_{TH} known as Thevenin's voltage and is the open terminal voltage across A, B terminals. Z_{TH} is known as Thevenin's impedance and is measured across open terminals A, B by replacing all energy sources with their internal impedance.



Proof: Consider the network shown in fig(1), in which Z_1, Z_2 and Z_3 are impedances, V is the applied voltage and Z_L is the load impedance.

Let I_1, I_L be the mesh currents, mesh equations for fig(1)

$$(Z_1 + Z_3) I_1 - Z_3 I_L = V \quad \text{----- (1)}$$

$$- Z_3 I_1 + (Z_2 + Z_3 + Z_L) I_L = 0 \quad \text{----- (2)}$$

From eq(2), we have

$$Z_3 I_1 = (Z_2 + Z_3 + Z_L) I_L$$

$$I_1 = \frac{(Z_2 + Z_3 + Z_L) I_L}{Z_3} \quad \text{----- (3)}$$

Substituting I_1 value from eq(3) in eq(1) we get

$$(Z_1 + Z_3) \frac{(Z_2 + Z_3 + Z_L) I_L}{Z_3} - Z_3 I_L = V$$

$$\frac{(Z_1 + Z_3)(Z_2 + Z_3 + Z_L) I_L}{Z_3} - Z_3^2 I_L = V$$

$$(Z_1 + Z_3)(Z_2 + Z_3 + Z_L) I_L - Z_3^2 I_L = V Z_3$$

$$I_L [(Z_1 + Z_3)(Z_2 + Z_3 + Z_L) - Z_3^2] = V Z_3$$

$$I_L = \frac{V Z_3}{[(Z_1 + Z_3)(Z_2 + Z_3 + Z_L) - Z_3^2]} \quad \text{----- (4)}$$

$$I_L = \frac{V Z_3}{[Z_1 Z_2 + Z_1 Z_3 + Z_1 Z_L + Z_3 Z_2 + Z_3^2 + Z_3 Z_L - Z_3^2]}$$

$$I_L = \frac{V Z_3}{(Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1) + Z_L (Z_1 + Z_3)} \quad \text{----- (5)}$$

Thevenin's Voltage (V_{TH})

To measure Thevenin's voltage make the terminals A, B open by removing the load impedance connected between them. The modified circuit diagram is shown in fig(2).

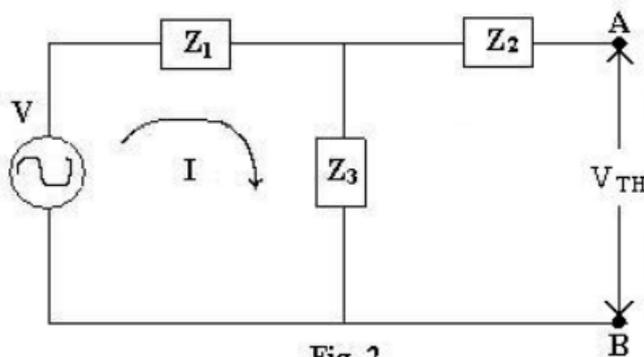


Fig. 2

voltage across terminals AB (V_{TH}) = voltage across Z_3

$$V_{TH} = I \times Z_3 \quad \text{----- (6)}$$

But from fig(2)

$$I = \frac{V}{Z_1 + Z_3}$$

Substituting I value in eq(6) we get

$$V_{TH} = \frac{VZ_3}{Z_1 + Z_3} \quad \text{----- (7)}$$

Thevenin's Impedance (Z_{TH})

Thevenin's impedance is measured across open terminals AB by replacing all energy sources with their internal impedances. The modified circuit diagram is shown in fig(3).

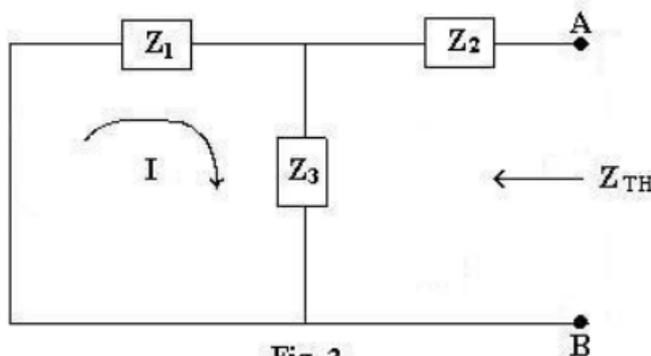


Fig. 3

$$Z_{TH} = (Z_1 \parallel Z_3) + Z_2$$



$$Z_{TH} = \frac{Z_1 Z_3}{Z_1 + Z_3} + Z_2$$

$$Z_{TH} = \frac{Z_1 Z_3 + Z_2(Z_1 + Z_3)}{Z_1 + Z_3}$$

$$Z_{TH} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1 + Z_3} \quad \text{----- (8)}$$

Thevenin's Equivalent Circuit

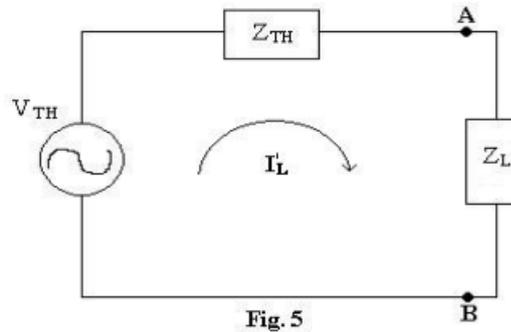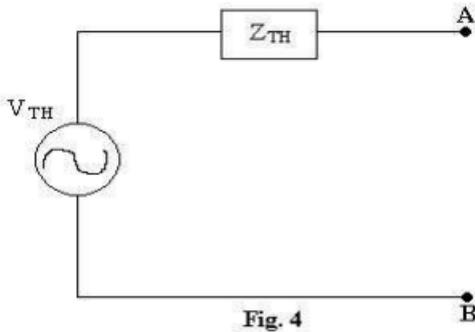Thevenin's equivalent circuit can be constructed by connecting voltage source supplying voltage V_{TH} in series with an impedance Z_{TH} as shown in fig.(4). Finally connect the load impedance which was removed from the circuit.



The current in the Thevenin's equivalent circuit is given by

$$I' = \frac{V_{TH}}{Z_{TH} + Z_L} \quad \text{-----(9)}$$

Substituting V_{TH} and Z_{TH} values in eq (9), we get

$$I'_L = \frac{\frac{VZ_3}{Z_1 + Z_3}}{\frac{(Z_1Z_2 + Z_2Z_3 + Z_3Z_1)}{(Z_1 + Z_3)} + Z_L}$$

$$I'_L = \frac{\frac{VZ_3}{Z_1 + Z_3}}{\frac{(Z_1Z_2 + Z_2Z_3 + Z_3Z_1) + Z_L(Z_1 + Z_3)}{(Z_1 + Z_3)}}$$

$$I'_L = \frac{VZ_3}{(Z_1Z_2 + Z_2Z_3 + Z_3Z_1) + Z_L(Z_1 + Z_3)} \quad \text{----- (10)}$$

Comparing eq(5) & eq(10), we get

$$I_L = I'_L$$

That is the current flowing through load resistor in a given circuit is equal to the current flowing through the load resistor in Thevenin's equivalent circuit. Hence Thevenin's theorem is proved.