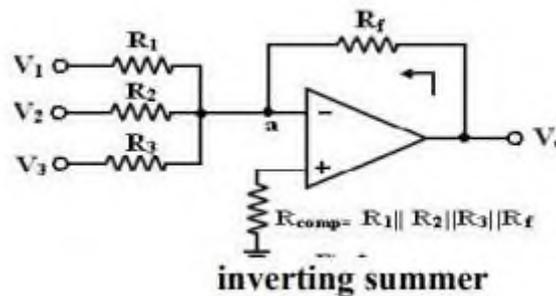


Adder:

Op-amp may be used to design a circuit whose output is the sum of several input signals. Such a circuit is called a summing amplifier or a summer or adder. An inverting summer or a non-inverting summer may be discussed now.

Inverting Summing Amplifier:



A typical summing amplifier with three input voltages V_1 , V_2 and V_3 three input resistors R_1 , R_2 , R_3 and a feedback resistor R_f is shown in figure 2. The following analysis is carried out assuming that the op-amp is an ideal one, $AOL = \infty$. Since the input bias current is assumed to be zero, there is no voltage drop across the resistor R_{comp} and hence the non-inverting input terminal is at ground potential.

$$I = V_1/R_1 + V_2/R_2 + \dots + V_n/R_n;$$

$$V_o = - R_f$$


$$I = R_f/R (V_1 + V_2 + \dots + V_n).$$

To find R_{comp} , make all inputs $V_1 = V_2 = V_3 = 0$.

So the effective input resistance $R_i = R_1 \parallel R_2 \parallel R_3$.

Therefore, $R_{comp} = R_i \parallel R_f = R_1 \parallel R_2 \parallel R_3 \parallel R_f$.

Non-Inverting Summing Amplifier:

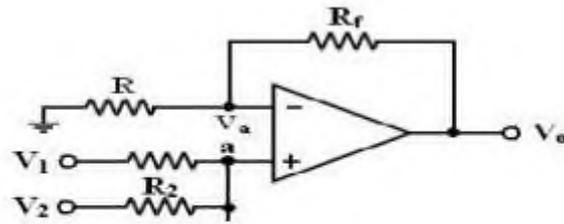

Non inverting summer

A summer that gives a non-inverted sum is the non-inverting summing amplifier of figure. Let the voltage at the (-) input terminal be V_a , which is a non-inverting weighted sum of inputs.

Let $R_1 = R_2 = R_3 = R = R_f/2$, then $V_o = V_1 + V_2 + V_3$

Subtractor using Operational Amplifier

If all resistors are equal in value, then the output voltage can be derived by using superposition principle.

Subtractor:

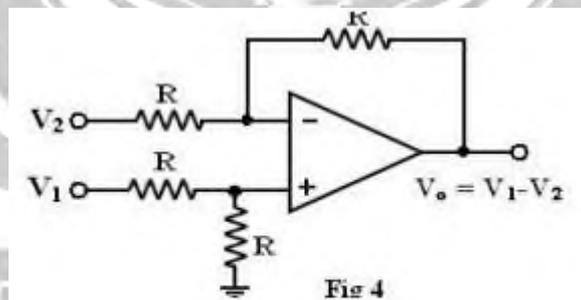


Fig 4

Subtractor

A basic differential amplifier can be used as a subtractor as shown in the above figure. If all resistors are equal in value, then the output voltage can be derived by using superposition principle.

To find the output V_{o1} due to V_1 alone, make $V_2 = 0$.

Then the circuit of figure as shown in the above becomes a non-inverting amplifier having input voltage $V_1/2$ at the non-inverting input terminal and the output becomes

$$V_{01} = V_1/2(1+R/R) = V_1 \text{ when all resistances are } R \text{ in the circuit.}$$


Similarly the output V_{02} due to V_2 alone (with V_1 grounded) can be written simply for an inverting amplifier as

$$V_{02} = -V_2$$

Thus the output voltage V_0 due to both the inputs can be written as

$$V_0 = V_{01} - V_{02} = V_1 - V_2$$

Adder/Subtractor:

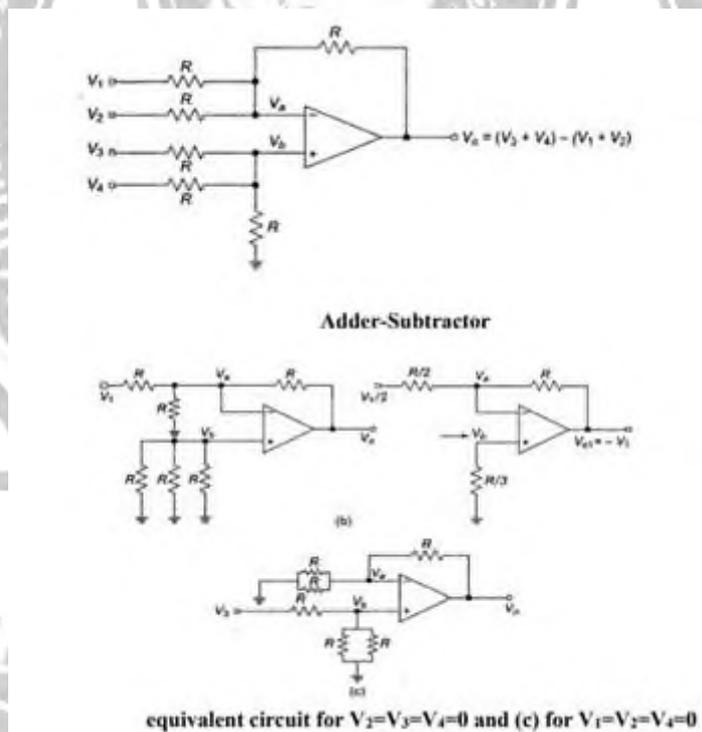

It is possible to perform addition and subtraction simultaneously with a single op-amp using the circuit shown in figure 2.16. The output voltage V_0 can be obtained by using superposition theorem. To find output voltage V_{01} due to V_1 alone, make all other input voltages V_2 , V_3 and V_4 equal to zero.

The simplified circuit is shown in figure 2.17. This is the circuit of an inverting amplifier and its output voltage is, $V_{01} = -R/(R/2) * V_1/2 = -V_1$ by Thevenin's

equivalent circuit at inverting input terminal). Similarly, the output voltage V_{02} due to V_2 alone is,

$$V_{02} = -V_2$$

Now, the output voltage V_{03} due to the input voltage signal V_3 alone applied at the (+) input terminal can be found by setting V_1 , V_2 and V_4 equal to zero.

$$V_{03} = V_3$$

The circuit now becomes a non-inverting amplifier as shown in fig.(c). So, the output voltage V_{03} due to V_3 alone is

$$V_{03} = V_3$$

Similarly, it can be shown that the output voltage V_{04} due to V_4 alone is

$$V_{04} = V_4$$


Thus, the output voltage V_o due to all four input voltages is given by

$$V_o = V_{01} = V_{02} = V_{03} = V_{04}$$

$$V_o = -V_1 - V_2 + V_3 + V_4$$

$$V_o = (V_3 + V_4) - (V_1 + V_2)$$

So, the circuit is an adder-subtractor.

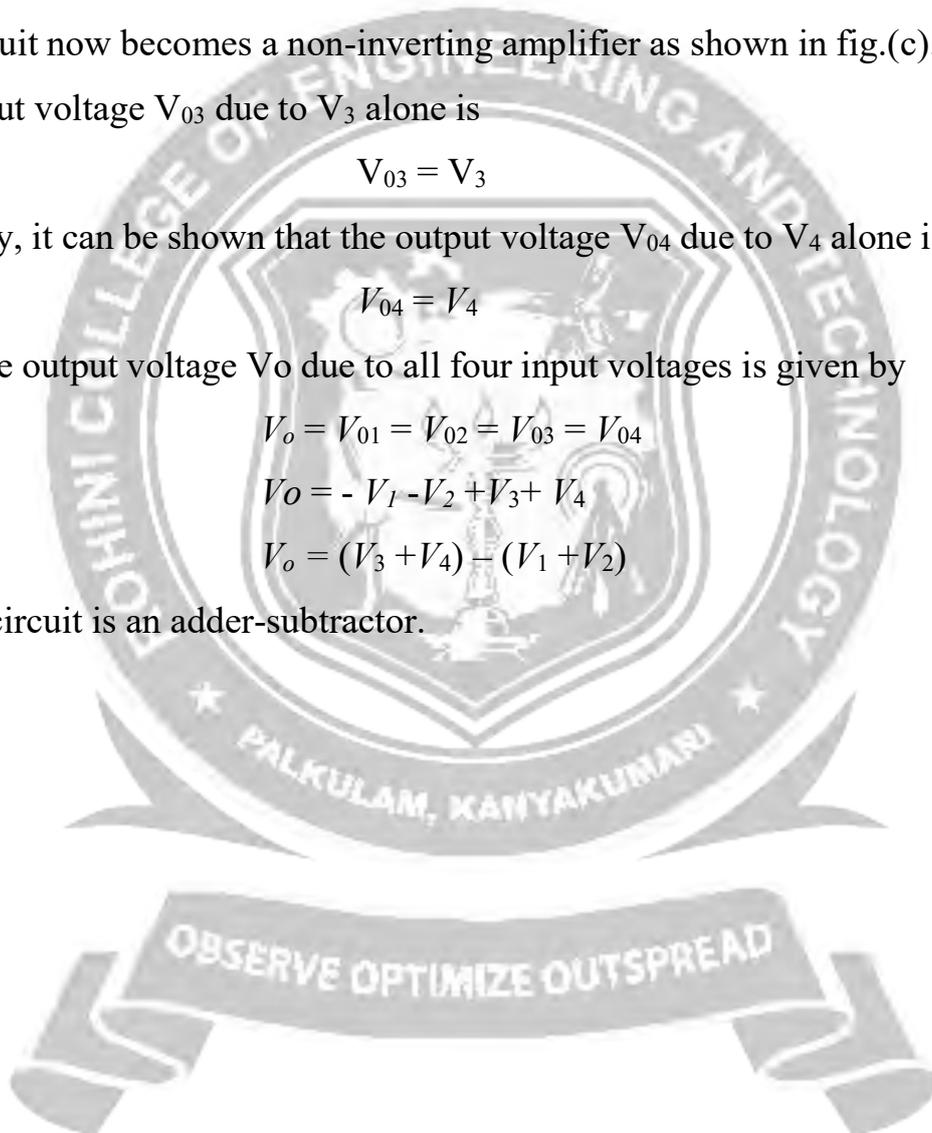


Comparator

A comparator compares a signal voltage on one input of an op-amp with a known voltage called a reference voltage on the other input. Comparators are used in circuits such as,

- Digital Interfacing
- Schmitt Trigger
- Discriminator
- Voltage level detector and oscillators

Non-inverting Comparator:

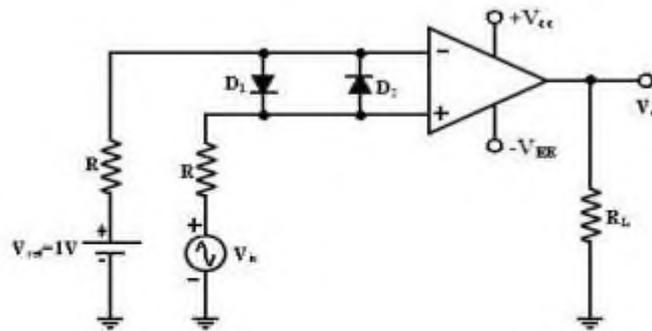

non-inverting comparator circuit

A fixed reference voltage V_{ref} of 1 V is applied to the negative terminal and time varying signal voltage V_{in} is applied to the positive terminal.

When V_{in} is less than V_{ref} the output becomes V_0 at $-V_{sat}$

$$[V_{in} < V_{ref} \Rightarrow V_0 (-V_{sat})].$$


When V_{in} is greater than V_{ref} , the (+) input becomes positive, the V_0 goes to $+V_{sat}$.

$$[V_{in} > V_{ref} \Rightarrow V_0 (+V_{sat})].$$

Thus the V_0 changes from one saturation level to another.

The diodes D_1 and D_2 protect the op-amp from damage due to the excessive input voltage V_{in} . Because of these diodes, the difference input voltage V_{id} of the op-amp diodes are called clamp diodes.

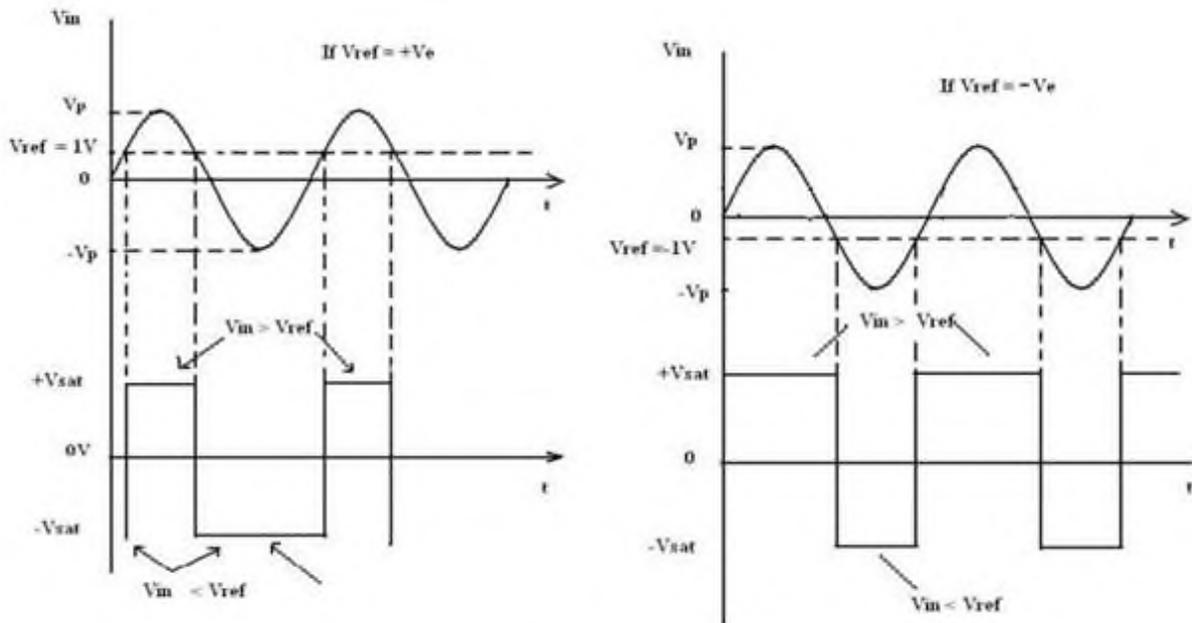
The resistance R in series with V_{in} is used to limit the current through D_1 and D_2 . To reduce offset problems, a resistance $R_{comp} = R$ is connected between the (-ve) input and V_{ref} .



Input and Output Waveforms of non-inverting comparator


Inverting Comparator:

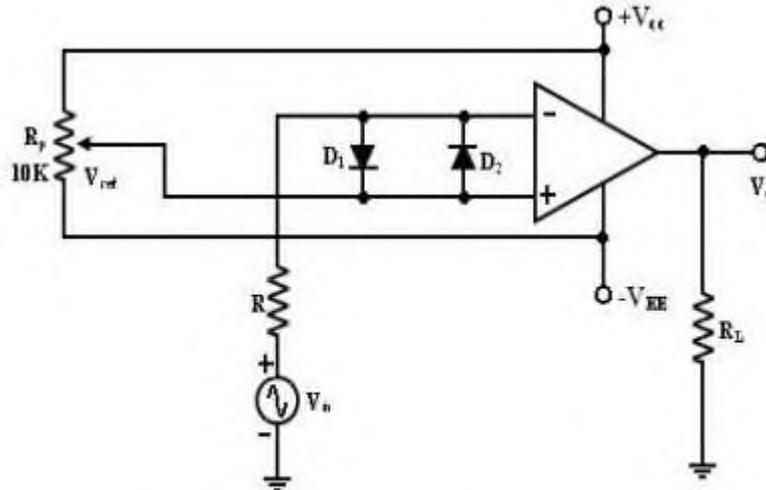This fig shows an inverting comparator in which the reference voltage V_{ref} is applied to the (+) input terminal and V_{in} is applied to the (-) input terminal.



Inverting comparator circuit

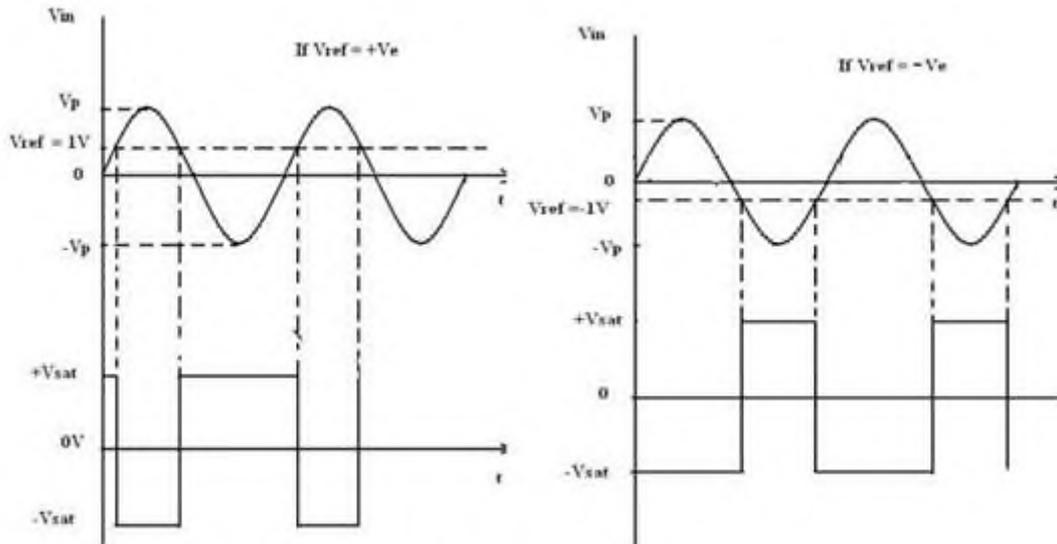
In this circuit V_{ref} is obtained by using a 10K potentiometer that forms a voltage divider with DC supply volt $+V_{cc}$ and -1 and the wiper connected to the input. As the wiper is moved towards $+V_{cc}$, V_{ref} becomes more positive. Thus a V_{ref} of a desired amplitude and polarity can be got by simply adjusting the 10k potentiometer.



Input and Output Waveforms of non-inverting comparator

Applications:

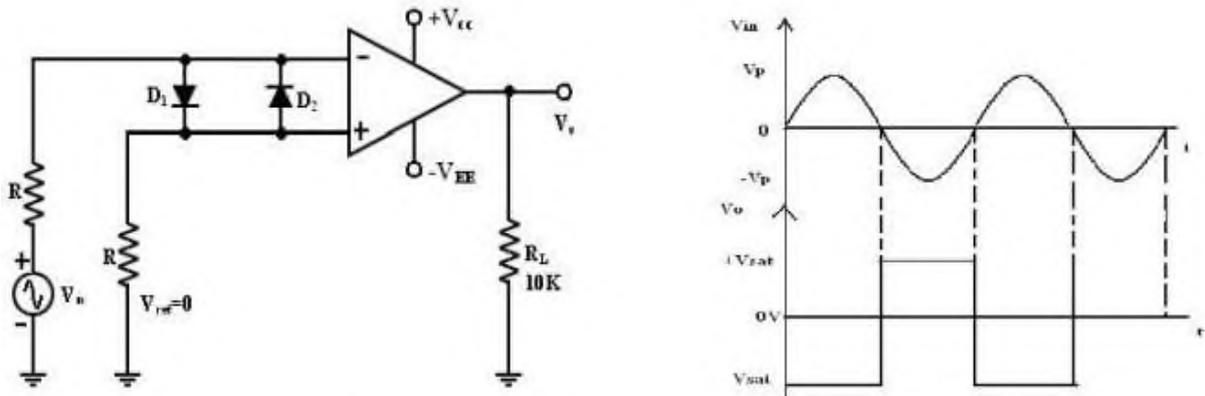Zero Crossing Detector: [Sine wave to Square wave converter]



Zero crossing detector circuit and input-output waveforms

One of the applications of comparator is the zero crossing detector or —sine wave to Square wave Converter. The basic comparator can be used as a zero crossing detector by setting V_{ref} is set to Zero. This Fig shows when in what direction an input signal V_{in} crosses zero volts. (i.e.) the o/p V_0 is driven into negative saturation when the input the signal V_{in} passes through zero in positive direction. Similarly, when V_{in} passes through Zero in negative direction the output V_0 switches and saturates positively.

Drawbacks of Zero- crossing detector:

In some applications, the input V_{in} may be a slowly changing waveform, (i.e) a low frequency signal. It will take V_{in} more time to cross 0V, therefore V_0 may not switch quickly from one saturation voltage to the other.

Because of the noise at the op-amp's input terminals the output V_0 may fluctuate between 2 saturations voltages $+V_{sat}$ and $-V_{sat}$. Both of these problems can be cured with the use of

regenerative or positive feedback that cause the output V_0 to change faster and eliminate any false output transitions due to noise signals at the input Inverting comparator with positive feedback This is known as Schmitt Trigger.

