

CMOS DEVICES

- A complementary CMOS inverter consists of a p-type and an n-type device connected in series.
- The DC transfer characteristics of the inverter are a function of the output voltage (V_{out}) with respect to the input voltage (V_{in}).

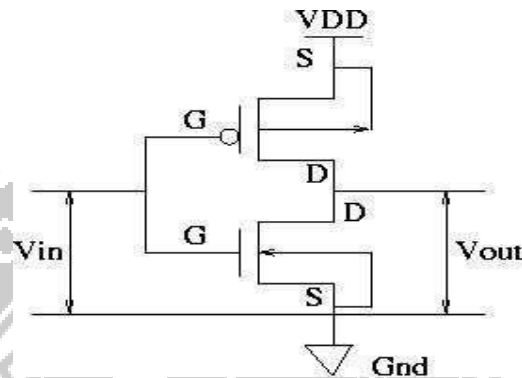


Fig 1.4.1 MOS Transistor

[Source: Neil H.E. Weste, CMOS VLSI Design ...]

- The MOS device first order Shockley equations describing the transistors in cut-off, linear and saturation modes can be used to generate the transfer characteristics of a CMOS inverter.
- Plotting these equations for both the n- and p-type devices produces the traces below.

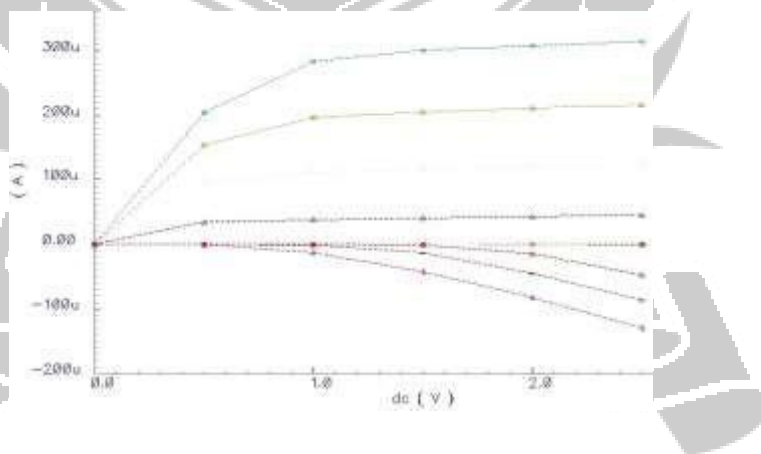


Fig 1.4.2 MOS Transistor IV Characteristics

[Source: Neil H.E. Weste, CMOS VLSI Design ...]

- The DC transfer characteristic curve is determined by plotting the common points of V_{gs} intersection after taking the absolute value of the p-device IV curves, reflecting superimposing them on the n- device IV curves.

- We basically solve for $V_{in(n-type)} = V_{in(p-type)}$ and $I_{ds(n-type)} = I_{ds(p-type)}$
- The desired switching point must be designed to be 50 % of magnitude of the supply voltage i.e. $V_{DD}/2$.
- Analysis of the superimposed n-type and p-type IV curves results in five regions, in which the inverter operates.
- **Region A** occurs when $0 \leq V_{in} \leq V_{t(n-type)}$.
 - The n-device is in cut-off ($I_{dsn} = 0$).
 - p-device is in linear region,
 - $I_{dsn} = 0$ therefore $-I_{dsp} = 0$
 - $V_{dsp} = V_{out} - V_{DD}$, but $V_{dsp} = 0$ leading to an output of $V_{out} = V_{DD}$.
- **Region B** occurs when the condition $V_{tn} \leq V_{in} \leq V_{DD}/2$ is met.
 - Here p-device is in its non-saturated region $V_{ds} \neq 0$.
 - n-device is in saturation

Saturation current I_{dsn} is obtained by setting $V_{gs} = V_{in}$ resulting in the equation:

- In **region B** I_{dsp} is governed by

voltages V_{gs} and V_{ds} described by:

- Saturation currents for the two devices are:
- **Region D** is defined by the inequality
- p-device is in saturation while n-device is in its non-saturation region.

- Equating the drain currents allows us to solve for V_{out} . (See supplemental notes for algebraic manipulations).
- In **Region E** the input condition satisfies:
- The p-type device is in cut-off: $I_{dsp}=0$
- The n-type device is in linear mode
- $V_{gsp} = V_{in} - V_{DD}$ and this is a more positive value compared to V_{tp} .
- $V_{out} = 0$

