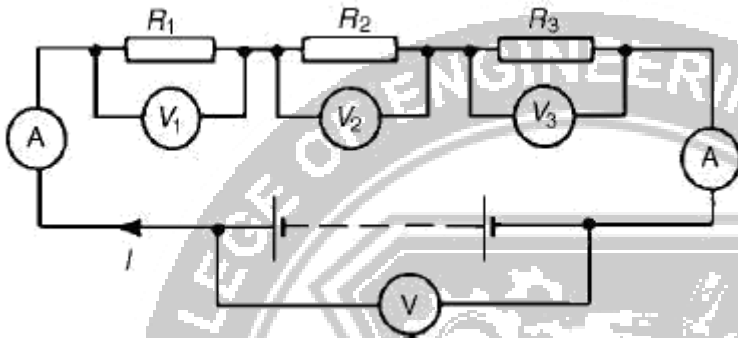


## Resistors in series and parallel circuits:

### Series circuits:

Figure shows three resistors  $R_1$ ,  $R_2$  and  $R_3$  connected end to end, i.e. in series, with a battery source of  $V$  volts. Since the circuit is closed a current  $I$  will flow and the p.d. across each resistor may be determined from the voltmeter readings  $V_1$ ,  $V_2$  and  $V_3$



### In a series circuit

(a) the current  $I$  is the same in all parts of the circuit and hence the same reading is found on each of the two ammeters shown, and

(b) the sum of the voltages  $V_1$ ,  $V_2$  and  $V_3$  is equal to the total applied voltage,  $V$ , i.e.

$$V = V_1 + V_2 + V_3$$

From Ohm's law:


$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3 \text{ and } V = IR \text{ where } R \text{ is the total circuit resistance.}$$

$$\text{Since } V = V_1 + V_2 + V_3$$

$$\text{then } IR = IR_1 + IR_2 + IR_3 \text{ Dividing throughout by } I \text{ gives } R = R_1 + R_2 + R_3$$

Thus for a series circuit, the total resistance is obtained by adding together the values of the separate resistances.

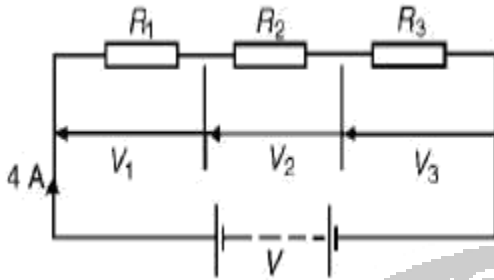**Problem 1:** For the circuit, determine (a) the battery voltage  $V$ , (b) the total resistance of the circuit, and (c) the values of resistance of resistors  $R_1$ ,  $R_2$  and  $R_3$ , given that the p.d.'s  $R_1$ ,  $R_2$  across and  $R_3$  are  $5V$ ,  $2V$  and  $6V$  respectively.



(a) Battery voltage  $V = V_1 + V_2 + V_3 = 5 + 2 + 6 = 13V$

(b) Total circuit resistance  $R = V / I$   
 $= 13 / 4 = 3.25 \Omega$


(c) Resistance  $R_1 = V_1 / I$   
 $= 5 / 4$

$= 1.25 \Omega$  Resistance  $R_2 = V_2 / I$

$= 2 / 4 = 0.5 \Omega$

Resistance  $R_3 = V_3 / I = 6 / 4 = 1.5 \Omega$

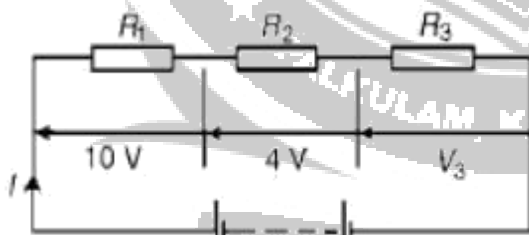**Problem 2.** For the circuit shown in Figure determine the p.d. across resistor  $R_3$ . If the total resistance of the circuit is  $100 \Omega$ , determine the current flowing through resistor  $R_1$ . Find also the value of resistor  $R_2$ .



P.d. across  $R_3$ ,  $V_3 = 25 - 10 - 4 = 11V$  Current  $I = V / R$


$= 25 / 100$

$= 0.25A$ , which is the current flowing in each resistor Resistance  $R_2 =$

$V_2 / I$

$= 4 / 0.25 = 16 \Omega$

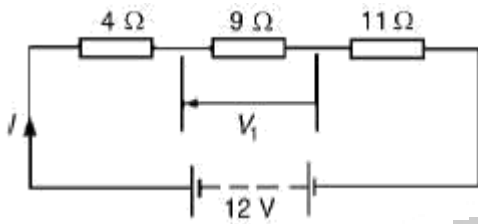**Problem 3:** A 12V battery is connected in a circuit having three series-connected resistors having resistances of  $4\ \Omega$ ,  $9\ \Omega$  and  $11\ \Omega$ . Determine the current flowing through, and the p.d. across the  $9\ \Omega$  resistor. Find also the power dissipated in the  $11\ \Omega$  resistor.



Total resistance  $R=4 + 9 + 11=24\ \Omega$  Current  $I = V/ R$

$$= 12/24$$

$=0.5A$ , which is the current in the  $9\ \Omega$  resistor.

P.d. across the  $9\ \Omega$  resistor,  $V_1 = I \times 9 = 0.5 \times 9$

$$= 4.5V$$


Power dissipated in the  $11\ \Omega$  resistor,  $P = I^2R=0.5^2(11)$

$$= 0.25(11)$$

$$= 2.75W$$

### PARALLEL NETWORKS:

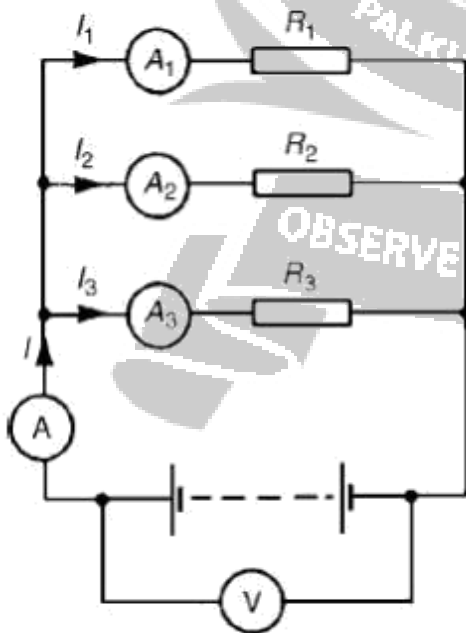**Problem 1:** Figure shows three resistors,  $R_1$ ,  $R_2$  and  $R_3$  connected across each other, i.e. in parallel, across a battery source of  $V$  volts.



**In a parallel circuit:**

(a) the sum of the currents  $I_1$ ,  $I_2$  and  $I_3$  is equal to the total circuit current,  $I$ , i.e.  
 $I = I_1 + I_2 + I_3$ , and

the source p.d.,  $V$  volts, is the same across each of the

From Ohm's law:

$$I_1 = V/R_1$$

$$I_2 = V/R_2$$

$$I_3 = V/R_3 \text{ and } I = V/R$$

where  $R$  is the total circuit resistance. Since  $I = I_1 + I_2 + I_3$

then

$V/R = V/R_1 + V/R_2 + V/R_3$  Dividing throughout by  $V$  gives:


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

This equation must be used when finding the total resistance  $R$  of a parallel circuit. For the special case of two resistors in parallel

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

OBSERVE OPTIMIZE OUTSPREAD

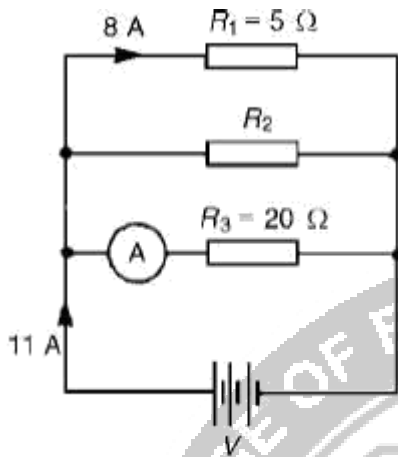
**Problem 2:** For the circuit shown in Figure , determine (a) the reading on the ammeter, and (b) the value of resistor R2.



P.d. across R1 is the same as the supply voltage V.  
Hence supply voltage,  $V = 8 \times 5 = 40V$

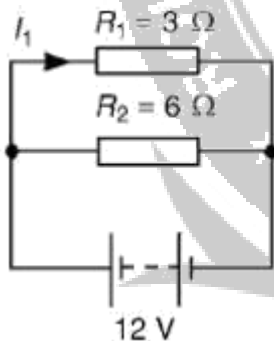(a) Reading on ammeter,  $I = \frac{V}{R_3} = \frac{40}{20} = 2A$

Current flowing through R2  
 $= 11 - 8 - 2 = 1A$  Hence,  $R_2 = \frac{V}{I_2} = \frac{40}{1} = 40 \Omega$




(a) The total circuit resistance R is given by  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} =$

$\frac{1}{3} + \frac{1}{6}$   $\frac{1}{R} = \frac{2}{6} + \frac{1}{6} = \frac{3}{6}$  Hence,  $R = \frac{6}{3} = 2 \Omega$

(b) Current in the 3 Ω resistance,  $I_1 = \frac{V}{R_1} = \frac{12}{3} = 4A$

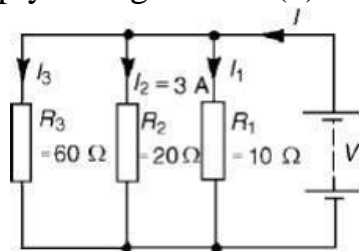**Problem 3:** For the circuit shown in Figure find (a) the value of the supply voltage  $V$  and (b) the value of current  $I$ .



(a) P.d. across  $20\ \Omega$  resistor =  $I_2 R_2 = 3 \times 20 = 60\text{V}$ , hence supply voltage  $V = 60\text{V}$  since the circuit is connected in parallel.

(b) Current

$$I_1 = V/R_1 = 60/10 = 6\text{A};$$


$$I_2 = 3\text{A}$$

$$I_3 = V/R_3 = 60/60 = 1\text{A}$$

Current  $I = I_1 + I_2 + I_3$  and hence  $I = 6 + 3 + 1 = 10\text{A}$  Alternatively,

$1/R = 1/60 + 1/20 + 1/10 = 1 + 3 + 6/60 = 10/60$  Hence total resistance  $R = 60/10 = 6\ \Omega$  Current  $I = V/R = 60/6 = 10\text{A}$

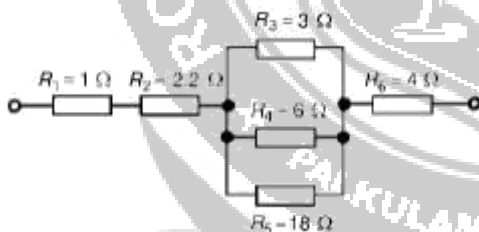**Problem 4:** Find the equivalent resistance for the circuit shown in Figure



$R_3, R_4$  and  $R_5$  are connected in parallel and their equivalent resistance  $R$  is given by:  $1/R = 1/3 + 1/6 + 1/18 = 6 + 3 + 1/18 = 10/18$

Hence  $R = 18/10 = 1.8\ \Omega$

The circuit is now equivalent to four resistors in series and the equivalent circuit resistance =  $1 + 2.2 + 1.8 + 4 = 9\ \Omega$