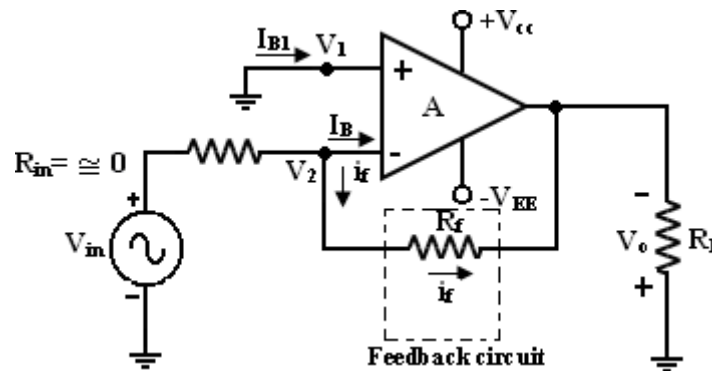


Voltage Shunt Feedback Amplifier:[Inverting Amplifier]

The input voltage drives the inverting terminal, and amplified as well as inverted output signal also applied to the inverting input via feedback resistor R_F .

Note:

Non-inverting terminal is grounded and feedback circuit has R_F and extra resistor R_I is connected in series with the input signal source V_{in} .

We derive the formula for

1. Voltage gain
2. Input and output resistance
3. Bandwidth
4. Total output offset voltage.

1. Closed – loop voltage gain A_F :

A_F of volt shunt feedback amplifier can be obtained by writhing KCL eqn at the input node V_2 .

$$i_{in} = i_F + I_B \text{ ----- (12.a)}$$

Since R_i is very large, the input bias current is negligibly small.

$$(i.e) \frac{V_{in} - V_2}{R_i} = \frac{V_2 - V_0}{R_F} \text{ ----- (12.b)}$$

Consider, from eqn,

$$V_1 - V_2 = -V_0 / A$$

Since $V_1 = 0V$

$$V_2 = -V_0 / A$$

Sub this value of V_2 in eqn (12.b) and rearranging,

$$\frac{V_{in} + V_0 / A}{R_i} = \frac{-(V_0 / A) - V_0}{R_F}$$

$$A_F = \frac{V_0}{V_{in}} = - \frac{AR_F}{R_i + R_F + AR_i} \text{ (exact) ----- (13)}$$

The –ve sign indicates that the input and output signals are out of phase 180° . (or opposite polarities).

Because of this phase inversion the diagram is known as Inverting amplifier with feedback. Since the internal gain A of the op-amp is very large (α) , $AR_i \gg R_i + R_F$, (i.e) eqn (13)

$$A_F = V_0 / V_{in} = -R_F / R_1 \text{ (Ideal)}$$

To express eqn (13) in terms of eqn(6). To begin with, we divide both numerator and denominator of eqn (13) by $(R_1 + R_F)$


$$A_F = AR_F / R_1 + R_F$$

$$\frac{AR_F}{1 + AR_1 (R_1 + R_F)} \quad \text{---(15)}$$

$$A_F = - AR / 1 + AB)$$

$$\text{Where } K = R_F / (R_1 + R_F)$$
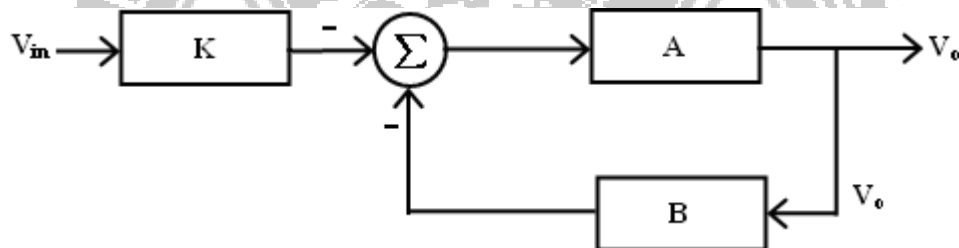
$$B = R_1 / (R_1 + R_F) \text{ Gain of feedback.}$$



The comparison of eqn (15) with feedback (6) indicates that in addition to the phase inversion (- sign), the closed loop gain of the inverting amplifier is K times the closed loop gain of the Non-inverting amplifier where $K < 1$. To derive an ideal closed loop gain, we can use Eqn 15 as follows, If $AB \gg 1$, then $(1+AB) = AB$ and $A_F = K/B = -R_F/R_1$ ---- (16)

2. Input Resistance with feedback:

Easiest method of finding the input resistance is to millerize the feedback resistor R_F .

(i.e) Split R_F in to its 2 Miller components as shown in fig.


In this circuit, the input resistance with feedback R_{if} is then

$$R_{if} = R_1 + R_F$$

$$\frac{R_1}{1+A} \parallel (R_i) \quad \text{---(18)}$$


Since R_i and A are very large.
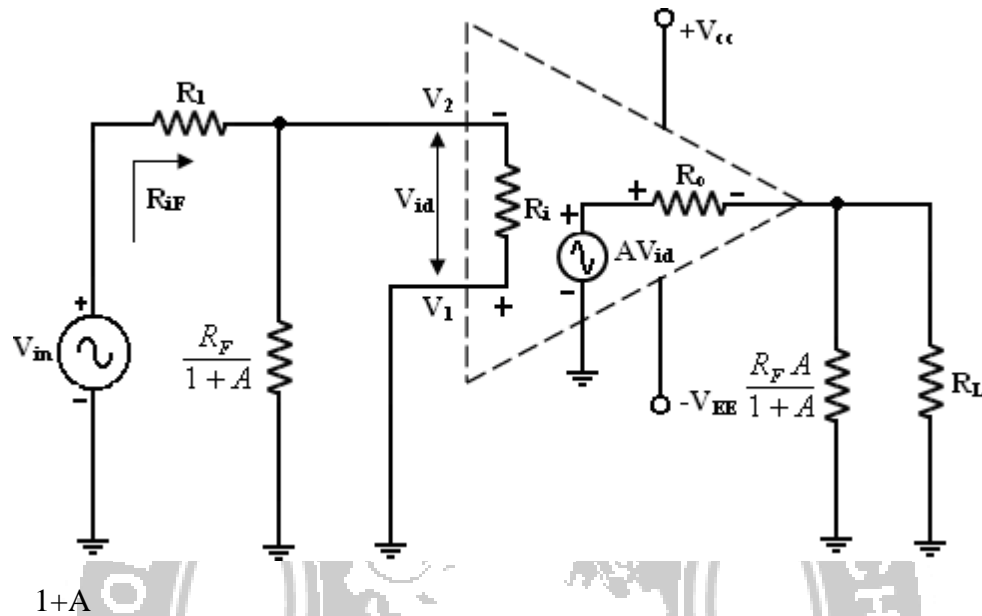
$$R_1 + R_F \parallel (R_1) \rightarrow 0\Omega$$



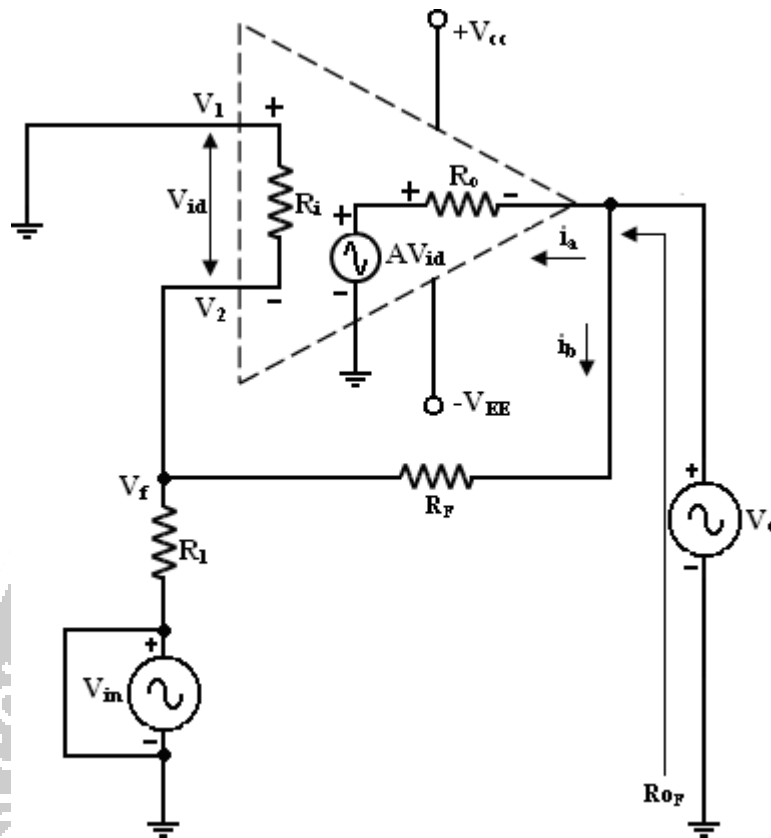3. Output Resistance with feedback:

The output resistance with feedback R_{OF} is the resistance measured at the output terminal of the feedback amplifier. Thevenin's circuit is exactly for the same as that of Non-inverting amplifier because the output resistance R_{OF} of the inverting amplifier must be identical to that of non – inverting amplifier.



R_0 = Output Resistance of the op-amp

A = Open loop volt gain of the op-amp

B = Gain of the feedback circuit.

4. Bandwidth with Feedback:

The gain Bandwidth product of a single break frequency op-amp is always constant.

Gain of the amplifier with feedback < gain without feedback

The bandwidth of amplifier with feedback f_F must be larger than that without feedback.

$$f_F = f_0 (1+AB) \text{ ----- (21.a)}$$

f_0 = Break frequency of the op-amp

= unity gain Bandwidth

UGB

$$\text{-----} = \text{-----}$$

Open- loop voltage gain

A

Sub this value of f_0 in eqn (21.a)

$$f_F = UGB \text{-----} (1+AB)A$$

$$f_F = UGB (K) \text{-----}(21.b)A_F$$

$$\text{Where } K = R_F / (R_1 + R_F) ; A_F = AK / (1+AB)$$

Eqn 10.b and 21.b => same for the bandwidth.

Same closed loop gain the closed loop bandwidth for the inverting amplifier is

< that of Non –inverting amplifier by a factor of $K(<1)$

5. Total output offset voltage with feedback:

When the temp & power supply are fixed, the output offset voltage is a function of the gain of an op-amp.

Gain of the feedback < gain without feedback.

The output offset volt with feedback < without feedback.

Total Output offset Voltage with f/b = Total output offset volt without f/b- $1+AB$

$$V_{out} = \pm V_{sat} \text{-----} \text{----}(22)1+AB$$

$\pm V_{sat}$ = Saturation Voltage

A = open-loop volt

gain of the op-amp

B = Gain of the f/b

circuit

$$B = R_1 / (R_1 + R_F)$$

In addition, because of the –ve f/b,

1. Effect of noise
2. Variations in supply voltages
3. Changes in temperature on the output voltage of inverting amplifier are reduced.