

5.5 Feedback Circuit

The function of the feedback circuit is to return a fraction of the output voltage to the input of the amplifier feedback circuit of negative voltage feedback amplifier. It is essentially a potential divider consisting of resistances R_1 and R_2 . The output voltage of the amplifier is fed to this potential divider which gives the feedback voltage to the input.

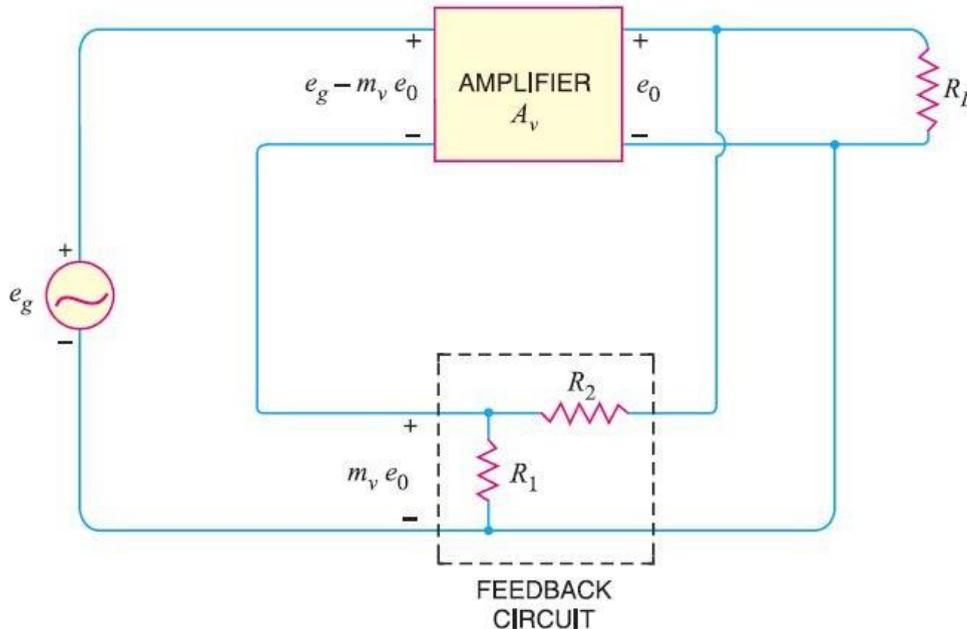


Figure: 5.5.1 Feedback Circuit

[Source: "Electronic devices and circuits" by "Balbir Kumar, Shail.B.Jain, and Page: 162]

Principles of Negative Current Feedback

In this method, a fraction of output current is feedback to the input of the amplifier. In other words, the feedback current (I_f) is proportional to the output current (I_{out}) of the amplifier. Fig. 5.5.2 shows the principles of negative current feedback. This circuit is called current-shunt feedback circuit. A feedback resistor R_f is connected between input and output of the amplifier. This amplifier has a current gain of A_i without feedback. It means that a current I_1 at the input terminals of the amplifier will appear as $A_i I_1$ in the output circuit i.e., $I_{out} = A_i I_1$.

Now a fraction m_i of this output current is feedback to the input through R_f . The fact that arrowhead shows the feed current being fed forward is because it is negative feedback.

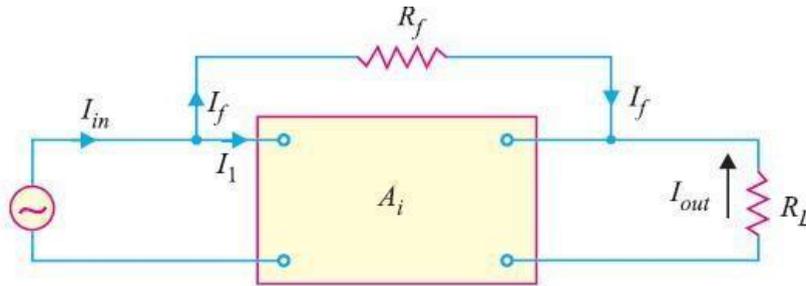


Figure: 5.5.2 Negative Current Feedback

[Source: "Electronic devices and circuits" by "Balbir Kumar, Shail.B.Jain, and Page: 162]

The following points may be noted carefully:

- (i) The current gain of the amplifier without feedback is A_i . However, when negative current feedback is applied, the current gain is reduced by a factor $(1 + m_i A_i)$.
- (ii) The feedback fraction (or current attenuation) m_i has a value between 0 and 1.
- (iii) The negative current feedback does not affect the voltage gain of the amplifier.