

Common Source Amplifier With Fixed Bias

Figure 3.2.1 shows Common Source Amplifier With Fixed Bias. The coupling capacitor C_1 and C_2 which are used to isolate the d.c biasing from the applied ac signal act as short circuits for ac analysis.

 


Figure 3.2.1 Common Source Amplifier With Fixed Bias

Diagram Source Electronic Tutorials

The following figure 3.2.2 shows the low frequency equivalent model for Common Source Amplifier With Fixed Bias. It is drawn by replacing all capacitors and d.c supply voltages with short circuit. JFET with its low frequency a.c Equivalent circuit

 


Figure 3.2.2 Common Source Amplifier With Fixed Bias

Diagram Source Brain Kart

low frequency equivalent model for Common Source Amplifier With Fixed Bias

Input Impedance Z_i

$$Z_i = R_G$$

Output Impedance Z_o

 


Figure 3.2.2

Figure 3.2.3 Equivalent Circuit model of JFET for output

Diagram Source Brain Kart

It is the impedance measured looking in figure 3.2.3 from the output side with input voltage V_i equal to Zero. As $V_i=0, V_{gs}=0$ and hence $g_m V_{gs}=0$. And it allows current source to be replaced by an open circuit. So,

$$Z_o = R_D || r_d$$

If the resistance r_d is sufficiently large compared to R_D , then

$$Z_o \approx R_D \quad \because r_d \gg R_D$$

Voltage Gain A_v :

The voltage gain $A_v = \frac{V_{ds}}{V_{gs}} = \frac{V_o}{V_i}$

Looking at Fig. we can write

$$V_o = -g_m V_{gs} (r_d \parallel R_D)$$

As we know $V_i = V_{gs}$ we can write

$$V_o = -g_m V_i (r_d \parallel R_D)$$

$$\therefore A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

and if $r_d \gg R_D$,

$$A_v \approx -g_m R_D$$

Table summarizes performance of common source amplifier with fixed bias.

Parameter	Exact	With $r_d \gg R_D$
Z_i	R_G	R_G
Z_o	$R_D \parallel r_d$	R_D
A_v	$-g_m (R_D \parallel r_d)$	$-g_m R_D$

Common source amplifier with self bias (Bypassed R_s)

Figure 3.2.4 shows Common Source Amplifier With self Bias. The coupling capacitor C_1 and C_2 which are used to isolate the d.c biasing from the applied ac signal act as short circuits for ac analysis. Bypass capacitor C_s also acts as a short circuits for low frequency analysis.

 


Figure 3.2.4 Common Source Amplifier With self Bias

Diagram Source Brain Kart

The following figure 3.2.5 shows the low frequency equivalent model for Common Source Amplifier With self Bias.

 


Figure 3.2.5 Common Source Amplifier With self Bias

Diagram Source Brain Kart

i) Input impedance Z_i :

$$Z_i = R_G$$

ii) Output impedance Z_o :

$$Z_o = r_d || R_D$$

if $r_d \gg R_D$

$$Z_o \approx R_D$$

iii) Voltage gain A_v :

$$A_v = -g_m (r_d || R_D)$$

If $r_d \gg R_D$

$$A_v = -g_m R_D$$

The low frequency equivalent model for Common Source Amplifier With self Bias. The negative sign in the voltage gain indicates there is a 180° phase shift between input and output voltages.

Common source amplifier with self bias (unbypassed R_s)

 


Fig3.7 Common source amplifier model of JFET

Figure 3.2.6 Common Source Amplifier model of JFET

Diagram Source Brain Kart

Now R_s will be the part of low frequency equivalent model as shown in figure 3.2.6

 


Figure 3.2.7 Small signal model for Common source amplifier model of JFET

Diagram Source Brain Kart

Figure 3.2.7 Input Impedance Z_i

$$Z_i = R_G$$

Output Impedance Z_o

It is given by

$$Z_o = Z_o' \parallel R_D$$

where $Z_o' = \left. \frac{V_o}{I_d} \right|_{V_i=0}$

$$Z_o = [r_d + R_s (\mu + 1)] \parallel R_D$$

$$Z_o = [r_d + R_s (g_m r_d + 1)] \parallel R_D$$

Voltage gain (A_v)

It is given by

$$A_v = \frac{V_o}{V_i}$$

We know that,

$$V_o = -I_d R_D$$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m r_d R_D}{r_d + R_s + R_D + g_m R_s r_d}$$

Dividing numerator and denominator by r_d we get,

$$\therefore A_v = \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_s + \frac{R_s + R_D}{r_d}}$$

If $r_d \gg R_s + R_D$

$$A_v = \frac{V_o}{V_i} = \frac{-g_m R_D}{1 + g_m R_s}$$

Table summarizes performance of common source amplifier with self bias.

Parameter	Bypassed R_S		Unbypassed R_S	
	Exact	$r_d \gg R_D$	Exact	$r_d \gg R_D$
Z_i	R_G	R_G	R_G	R_G
Z_o	$R_D \parallel r_d$	R_D	$[r_d + R_S(g_m r_d + 1)] \parallel R_D$ or $[r_d + R_S(\mu + 1)] \parallel R_D$	$[r_d + R_S(g_m r_d + 1)] \parallel R_D$ or $[r_d + R_S(\mu + 1)] \parallel R_D$
A_v	$-g_m(R_D \parallel r_d)$	$-g_m R_D$	$\frac{-g_m R_D}{1 + g_m R_S + \frac{R_S + R_D}{r_d}}$	$\frac{-g_m R_D}{1 + g_m R_S}$

Common source amplifier with Voltage divider bias (Bypassed R_S)

Figure 3.2.8 shows Common Source Amplifier With voltage divider Bias. The coupling capacitor C_1 and C_2 which are used to isolate the d.c biasing from the applied ac signal act as short circuits for ac analysis. Bypass capacitor C_S also acts as a short circuits for low frequency analysis.

 


Figure 3.2.8 Common Source Amplifier With voltage divider Bias (Bypassed R_S)

Diagram Source Brain Kart

The following figure 3.2.9 shows the low frequency equivalent model for Common Source Amplifier With voltage divider Bias

 


Figure 3.2.9 low frequency equivalent model for Common Source Amplifier With voltage divider Bias

Diagram Source Brain Kart

The parameters are given by

$$\begin{aligned}
 R_G &= R_1 \parallel R_2 \\
 Z_i &= R_G \\
 &= R_1 \parallel R_2 \\
 Z_o &= r_d \parallel R_D \\
 &\approx R_D \\
 A_v &= -g_m (r_d \parallel R_D) \\
 &\approx -g_m R_D
 \end{aligned}$$

if $r_d \gg R_D$

If $r_d \gg R_D$

The negative sign in the voltage gain indicates there is a 180° phase shift between input and output voltages.

Common source amplifier with Voltage divider bias (unbypassed R_s)

Figure 3.2.10 shows small signal model of Common source amplifier with Voltage divider bias(without Bypassed R_s).

 


Figure 3.2.10 small model of Common source amplifier with Voltage divider bias(without Bypassed R_s)

Diagram Source Brain Kart

Now R_s will be the part of low frequency equivalent model as shown in figure 3.2.11.

 


Figure 3.2.11 small model of Common source amplifier with Voltage divider bias(without Bypassed R_s)

Diagram Source Brain Kart

It is important to note that, here, $R_G = R_1 || R_2$.

$$Z_i = R_G = R_1 || R_2$$

$$Z_o' = r_d + g_m R_s r_d + R_s$$

or $Z_o' = r_d + R_s (\mu + 1)$

$$Z_o = [r_d + g_m R_s r_d + R_s] || R_D$$

or $Z_o = [r_d + R_s (\mu + 1)] || R_D$

$$A_v = \frac{-g_m R_D}{1 + g_m R_s + \frac{R_s + R_D}{r_d}}$$

Where A_v is the Voltage Gain.