

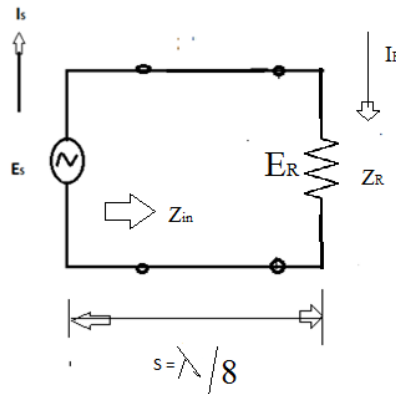
THE EIGHT WAVE LINE: ($\lambda/8$)

Fig: 3.1.1 The eight wave line

Fig 3.1.1 shows the circuit diagram of a transmission line with finite length $\lambda/8$ the input voltage is E_s and current I_s .

The input impedance of the circuit is Z_{in} The receiving end voltage and current is E_R and I_R .

The distance between sending and receiving end $S = \lambda/8$

We know, the input impedance of the lossless line is given by,

- $z_{in} = \frac{E_s}{I_s} = R_0 \left[\frac{Z_R + jR_0 \tan \beta s}{R_0 + jZ_R \tan \beta s} \right]$
- Sub, $S = \frac{\lambda}{8}$, $\beta = \frac{2\pi}{\lambda}$ in above

$$z_{in} = R_0 \left[\frac{Z_R + jR_0 \tan\left(\frac{2\pi}{\lambda}\right)\left(\frac{\lambda}{8}\right)}{R_0 + jZ_R \tan\left(\frac{2\pi}{\lambda}\right)\left(\frac{\lambda}{8}\right)} \right]$$

$$z_{in} = R_0 \left[\frac{Z_R + jR_0 \tan\left(\frac{\pi}{4}\right)}{R_0 + jZ_R \tan\left(\frac{\pi}{4}\right)} \right]$$

$$z_{in} = R_0 \left[\frac{Z_R + jR_0}{R_0 + jZ_R} \right]$$

$$|z_{in}| = |R_0| \left[\frac{|Z_R + jR_0|}{|R_0 + jZ_R|} \right]$$

$$|z_{in}| = R_0 \left[\frac{\sqrt{R_0^2 + Z_R^2}}{R_0^2 + Z_R^2} \right]$$

$$|z_{in}| = R_0$$

Thus the eighth wave line is generally used to transformer any resistance Z_R an impedance z_{in} having its magnitude equal to characteristic resistance R_0 of the line.