

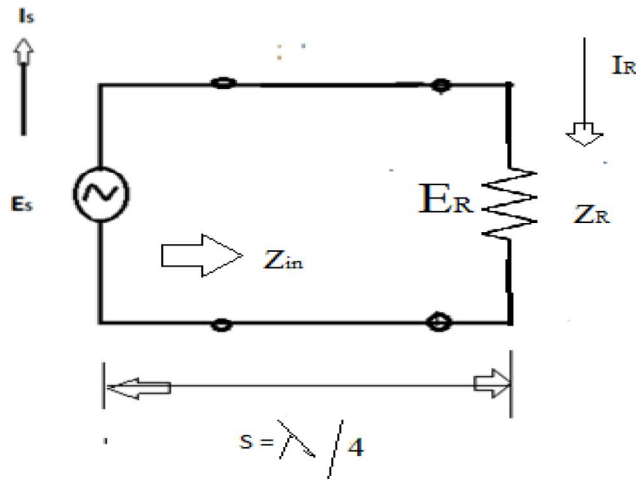
THE QUARTER WAVE LINE:

Fig: 3.1.2 Quarter wave section as a impedance inverter

Fig 3.1.2 shows the circuit diagram of a transmission line with finite length $\frac{\lambda}{4}$ the input voltage is E_s and current I_s .

The input impedance of the circuit is Z_{in}

The receiving end voltage and current is E_R and I_R .

The distance between sending and receiving end $S = \frac{\lambda}{4}$

We know, the input impedance of the lossless line is given by,

$$Z_{in} = \frac{E_s}{I_s} = R_0 \left[\frac{Z_R + jR_0 \tan \beta s}{R_0 + jZ_R \tan \beta s} \right]$$

Sub, $S = \frac{\lambda}{4}$, $\beta = \frac{2\pi}{\lambda}$ in above equ,

$$Z_{in} = R_0 \left[\frac{Z_R + jR_0 \tan \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda}{4} \right)}{R_0 + jZ_R \tan \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda}{4} \right)} \right]$$

$$Z_{in} = R_0 \left[\frac{Z_R + jR_0 \tan \left(\frac{\pi}{2} \right)}{R_0 + jZ_R \tan \left(\frac{\pi}{2} \right)} \right]$$

$$Z_{in} = R_0 \frac{\tan \left(\frac{\pi}{2} \right) \left[\frac{-Z_R}{\tan \left(\frac{\pi}{2} \right)} + jR_0 \right]}{\tan \left(\frac{\pi}{2} \right) \left[\frac{R_0}{\tan \left(\frac{\pi}{2} \right)} + jZ_R \right]}$$

$$Z_{in} = R_0 \left[\frac{\frac{1}{\infty} + jR_0}{\frac{1}{\infty} + jZ_R} \right]$$

$$Z_{in} = \frac{R_0^2}{Z_R}$$

The input impedance equation is similar to the equation of transformer.

Thus the quarter wave line can be used as a transformer for impedance matching to the load Z_R with input impedance Z_{in} .

A quarter wave transformer can transfer low impedance into high impedance and vice versa.

So, it can be considered as impedance inverter. The short circuit quarter wave line behaves like a open circuit in the other end.

While, the open circuited quarter wave line will behave like short circuit in the other end.

APPLICATION:

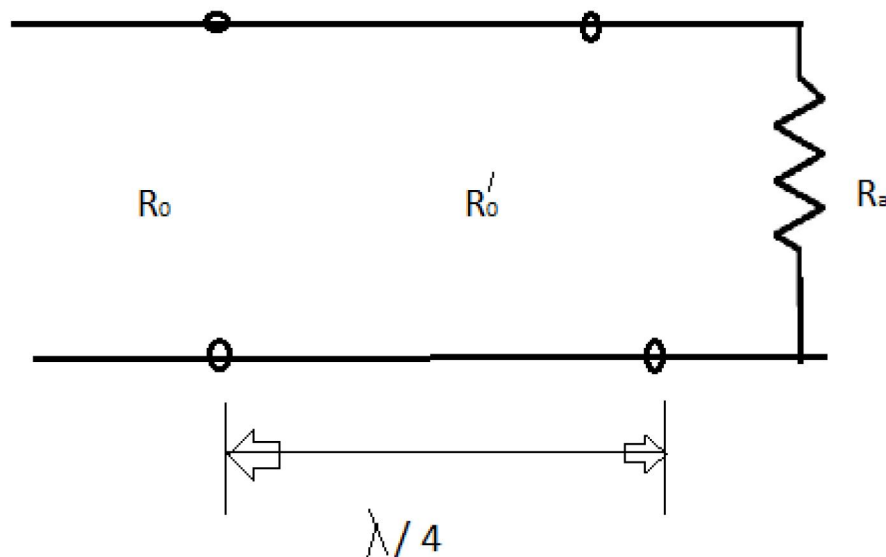


Fig: 3.1.3 Quarter wave line as-insulator

In Fig 3.1.3 the major application of $\frac{\lambda}{4}$ line is impedance transformer is coupling a transmission line to a resistive load such as an antenna. From the input impedance equation of $\frac{\lambda}{4}$ line.

$$Z_{in} = \frac{R_0^2}{Z_R}$$

If antenna is a load having a resistance of R_a the quarter wave section is designed such that its characteristic impedance R'_0 transforms antenna resistance R_a to the characteristic impedance of the line R_0 .

$$R_0 = \frac{R_0'^2}{R_a}$$

$$R_0'^2 = R_0 R_a$$

$$R'_0 = \sqrt{R_0 R_a}$$

