

2.3 Continuous conduction

Let us assume that the armature current is continuous over the whole range of operation. Typical voltage and current waveforms are shown in Fig for semi-converter and full-converter systems, respectively. The thyristors are symmetrically triggered. In the semi-converter system shown in Fig. thyristor S_1 is triggered at an angle α and S_2 at an angle $\alpha + \pi$ with respect to the supply voltage v . In the full-converter system shown in Fig. thyristors S_1 and S_3 are simultaneously triggered at α , thyristors S_2 and S_4 are triggered at $\pi + \alpha$.

In Fig. the motor is connected to the input supply for the period $\alpha < \omega t < \pi$ through S_1 and D_2 , and the motor terminal voltage e_a is the same as the supply input voltage v . Beyond π , e_a tends to reverse as the input voltage changes polarity. This will forward-bias the free-wheeling diode and DFW will start conducting. The motor current i_a , which was flowing from the supply through S_1 is transferred to DFW (i.e., S_1 commutates). The motor terminals are shorted through the free-wheeling diode during $\pi < \omega t < (\pi + \alpha)$, making e_o zero. Energy from the supply is therefore delivered to the armature

Circuit when the thyristor conducts (α to π). This energy is partially stored in the inductance, partially stored in the kinetic energy (K.E.) of the moving system, and partially used to supply the mechanical load. During the free-wheeling period, π to $\pi + \alpha$, energy is recovered from the inductance and is converted to mechanical form to supplement the K.E. in supplying the mechanical load. The free-wheeling armature current continues to produce electromagnetic torque in the motor. No energy is feedback to the supply during this period.

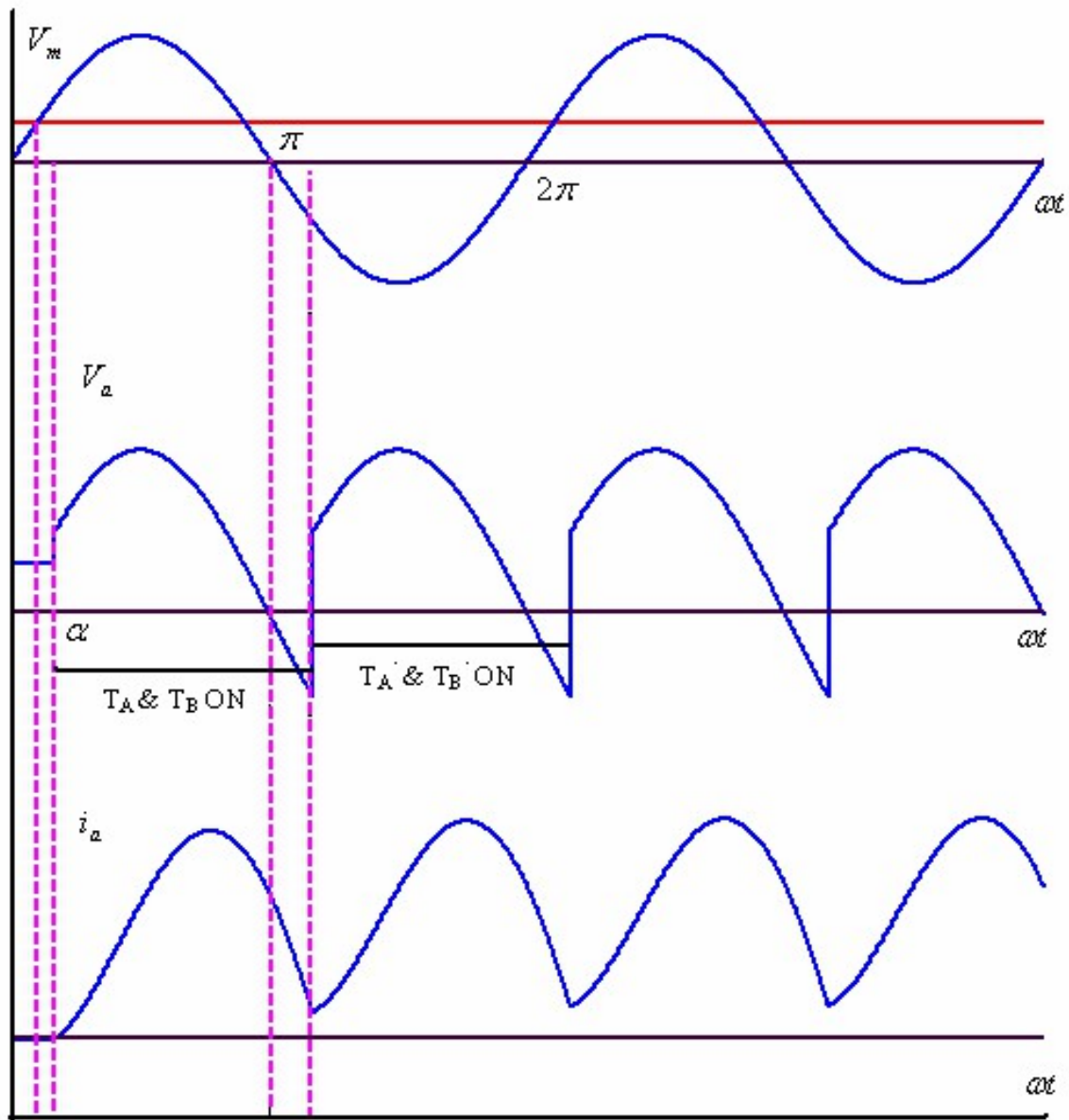


Figure 2.3.1 Continuous conduction waveform

(Source: "Fundamentals of Electrical Drives" by G.K.Dubey, page-108)

In Fig. the motor is always connected to the input supply through the thyristors. Thyristors S1 and S3 conduct during the interval $\alpha < \omega t < (\pi + \alpha)$ and connect the motor to the supply. At $\pi + \alpha$, thyristors S2 and S4 are triggered. Immediately the supply voltage appears across the thyristors S1 and S3 as a reverse-bias voltage and turns them off. This is called natural or line commutation. The motor current i_a , which was flowing from the supply through S1 and S3 is transferred to S2 and S4. During α to π , energy flows from the input supply to the motor (both v and i_a

are positive, and e_o and i_o are positive, signifying positive power flow). However, during $7T$ to $7T + a$, some of the motor system energy is feedback to the input supply (v and I have opposite polarities and likewise e_a and i_o' signifying reverse power flow). Voltage and current waveforms are shown for a firing angle greater than 90° . The average motor terminal voltage E_o is negative. If the motor back emf E_g is reversed, it will behave as a de-generator and will feed power back to the ac supply. This is known as the inversion operation of the converter, and this mode of operation is used in the regenerative braking of the motor.

