

3.3 ANALOG MULTIPLIER ICs

Analog multiplier is a circuit whose output voltage at any instant is proportional to the product of instantaneous value of two individual input voltages. Important applications of these multipliers are multiplication, division, squaring and square – rooting of signals, modulation and demodulation. These analog multipliers are available as integrated circuits consisting of op-amps and other circuit elements. The Schematic of a typical analog multiplier, namely, AD633 is shown in figure 3.3.1.

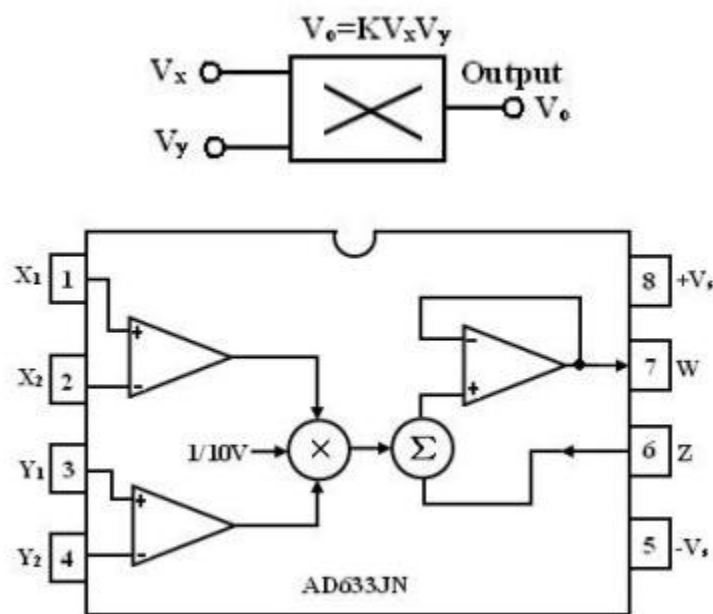


Figure 3.3.1 Schematic of Analog Multiplier IC and its symbol

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

The AD633 multiplier is a four – quadrant analog multiplier.

- It possesses high input impedance; this characteristic makes the loading effect on the signal source negligible.
- It can operate with supply voltages ranging from $\pm 18\text{V}$.
- IC does not require external components.
- The typical range of the two input signals is $\pm 10\text{V}$.

SCHEMATIC REPRESENTATION OF A MULTIPLIER

The schematic representation of an analog multiplier is shown in figure 3.3.1. The output V_0 is the product of the two inputs V_x and V_y is divided by a reference voltage V_{ref} . Normally, the reference voltage V_{ref} is internally set to 10V. Therefore, $V_0 = V_x V_y / 10$. In other words, the basic input – output relationship can be defined by $KV_x V_y$ when $K = 1/10$, a constant. Thus for peak input voltages of 10V, the peak magnitude of output voltage is $1/10 * 10 * 10 = 10V$. Thus, it can be noted that, as long as $V_x < 10V$ and $V_y < 10V$, the multiplier output will not saturate.

MULTIPLIER QUADRANTS

The transfer characteristics of a typical four-quadrant multiplier are shown in figure 3.3.2. Both the inputs can be positive or negative to obtain the corresponding output as shown in the transfer characteristics.

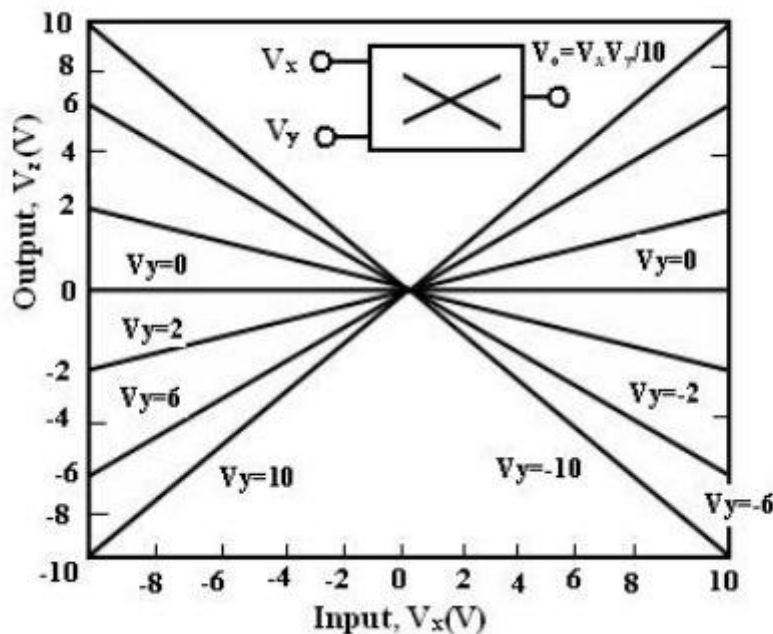


Figure 3.3.2. Transfer Characteristics of a typical four-quadrant multiplier

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

APPLICATIONS OF MULTIPLIER ICs

The multiplier ICs are used for the following purposes:

1. Voltage Squarer
2. Frequency doublers
3. Voltage divider
4. Square rooter
5. Phase angle detector
6. Rectifier

VOLTAGE SQUARER

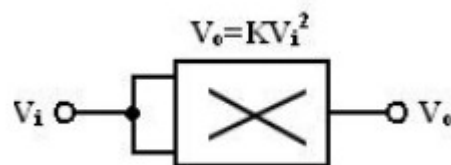


Figure 3.3.3. Voltage squarer Circuit

[source: "Linear Integrated Circuits" by S.Salivahanan & V.S. Kanchana Bhaskaran, Page-408]

Figure 3.3.3 shows the multiplier IC connected as a squaring circuit. The inputs can be positive or negative, represented by any corresponding voltage level between 0 and 10V. The input voltage V_i to be squared is simply connected to both the input terminals, and hence we have, $V_x = V_y = V_i$ and the output is $V_o = KV_i^2$. The circuit thus performs the squaring operation. This application can be extended for frequency doubling applications.

FREQUENCY DOUBLERS

Figure 3.3.4 a). shows the squaring circuit connected for frequency doubling operation. A sine-wave signal V_i has a peak amplitude of A_v and frequency of f Hz. Then, the output voltage of the doublers circuit is given by

$$v_o = \frac{A_v \sin 2\pi ft * A_v \sin 2\pi ft}{10} = \frac{A_v^2}{10} \sin^2 2\pi ft = \frac{A_v^2}{20} (1 - \cos 4\pi ft)$$

Assuming a peak amplitude A_v of 5V and frequency f of 10KHz, $V_o = 1.25 - 1.25 \cos 2\pi(20000)t$. The first term represents the dc term of 1.25V peak amplitude. The input and output waveforms are shown in figure. The output waveforms ripple with twice the input frequency in the rectified output of the input signal. This forms the principle of application of analog multiplier as rectifier of ac signals. Figure 3.3.4 b) Input-output waveform of frequency doubler.

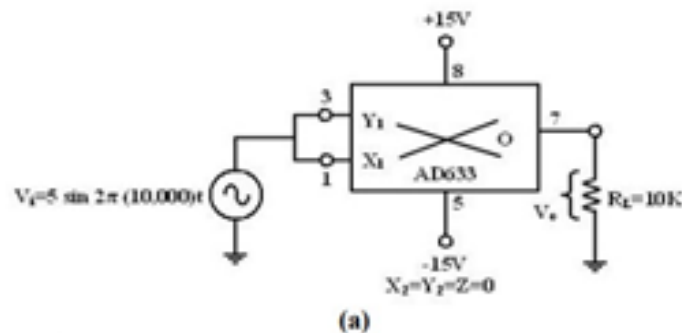


Figure 3.3.4 a) Frequency Doubler circuit diagram

[source: "Linear Integrated Circuits" by S.Salivahanan & V.S. Kanchana Bhaskaran, Page-408]

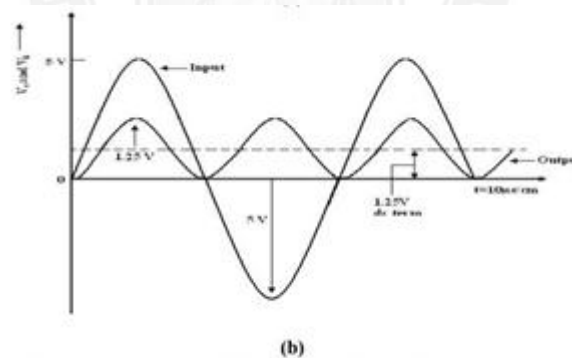


Figure 3.3.4 b) Input-output waveform

[source: "Linear Integrated Circuits" by S.Salivahanan & V.S. Kanchana Bhaskaran, Page-408]

The dc component of output V_o can be removed by connecting a $1\mu\text{F}$ coupling capacitor between the output terminal and a load resistor, across which the output can be observed.

VOLTAGE DIVIDER

In voltage divider circuit the division is achieved by connecting the multiplier in the feedback loop of an op-amp. The voltages V_{den} and V_{num} represent the two input voltages, V_{dm} forms one input of the multiplier, and output of op-amp V_{oA} forms the second input. The output

V_{OA} forms the second input. The output V_{OM} of the multiplier is connected back of op- amp in the feedback loop. Then the characteristic operation of the multiplier gives

$$V_{om} = KV_{OA} V_{dm} \text{ -----(1)}$$

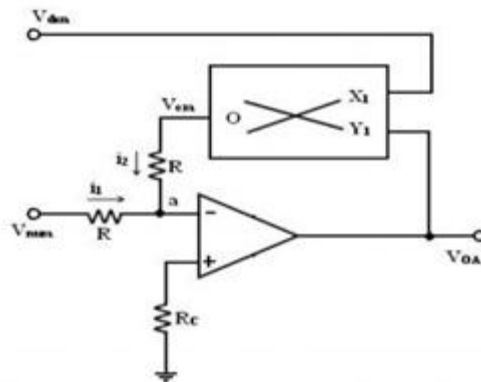


Figure 3.3.5.Voltage Divider Circuit

[source: "Linear Integrated Circuits" by S.Salivahanan & V.S. Kanchana Bhaskaran, Page-409]

As shown in figure 3.3.5 no input signal current can flow into the inverting input terminal of op-amp, which is at virtual ground. Therefore, at the junction a, $i_1 + i_2 = 0$, the current $i_1 = V_{num} / R$, where R is the input resistance and the current $i_2 = V_{om} / R$. With virtual ground existing at a,

$$i_1 + i_2 = V_{num} / R + V_{om} / R = 0$$

$$KV_{OA} V_{den} = - V_{num}$$

or

$$v_{OA} = - v_{num} / KV_{den}$$

where V_{num} and V_{den} are the numerator and denominator voltages respectively. Therefore, the voltage division operation is achieved. V_{num} can be a positive or negative voltage and V_{den} can have only positive values to ensure negative feedback. When V_{dm} is changed, the gain $10/V_{dm}$ changes, and this feature is used in automatic gain control (AGC) circuits.

SQUARE ROOTER

The divider voltage can be used to find the square root of a signal by connecting both inputs of the multiplier to the output of the op-amp. Substituting equal in magnitude but

opposite in polarity (with respect to ground) to V_i . But we know that V_{om} is one- term (Scale factor) of $V_0 * V_0$ or

$$-V_i = V_{om} = V^2/10$$

Solving for V_0 and eliminating $\sqrt{-1}$ yields. $V_0 = \sqrt{10|V_i|}$

Eqn. states that V_0 equals the square root of 10 times the absolute magnitude of V_i . The input voltage V_i must be negative, or else, the op-amp saturates. The range of V_i is between -1 and -10V. Voltages less than -1V will cause inaccuracies in the result. The diode prevents negative saturation for positive polarity V_i signals. For positive values of V_i the diode connections are reversed.

PHASE ANGLE DETECTOR

The multiplier configured for phase angle detection measurement is shown in figure 3.3.6. When two sine-waves of the same frequency are applied to the inputs of the multiplier, the output V_0 has a dc component and an AC component.

The trigonometric identity shows that

$$\sin A \sin B = 1/2 (\cos (A-B) - \cos (A+B)).$$

When the two frequencies are equal, but with different phase angles, e.g. $A=2\pi ft + \theta$ for signal V_x and $B= 2\pi ft$ for signal V_y , then using the identity

$$\begin{aligned} [\sin (2\pi ft + \theta)][\sin 2\pi ft] &= 1/2[\cos -\cos(4\pi ft + \theta)] \\ &= 1/2(\text{dc- the double frequency term}) \end{aligned}$$

Therefore, when the two input signals V_x and V_y are applied to the multiplier, V_0 (dc) is given by

$$v_v(dc) = \frac{v_{xp}v_{yp}}{20} \cos\theta$$

where V_{xp} and V_{yp} are the peak voltage amplitudes of the signals V_x and V_y . Thus, the output V_0 (dc) depends on the factor $\cos \theta$. A dc voltmeter can be calibrated as a phase angle meter when the product of V_{xp} and V_{yp} is made equal to 20. Then, a (0-1) V range dc voltmeter can

directly read $\cos \theta$, with the meter calibrated directly in degrees from a cosine table. The input and output waveforms are shown in figure 3.3.7.

Then the above eqn becomes V_0 (dc) = $\cos \theta$, if we make the product $V_{xp} V_{yp} = 20$ or in other words, $V_{xp} = V_{yp} = 4.47V$.

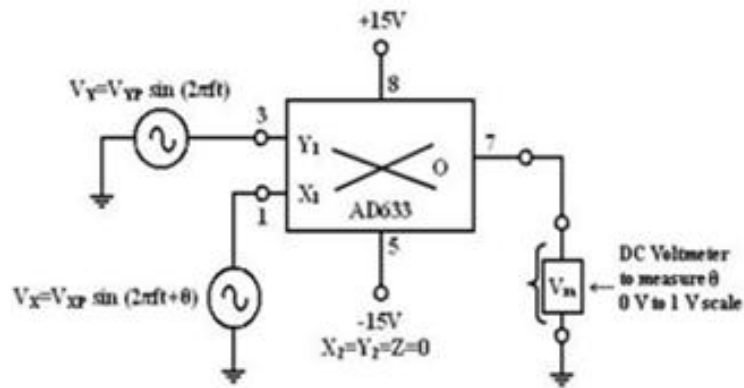


Figure 3.3.6 Phase angle measurement circuit diagram

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]

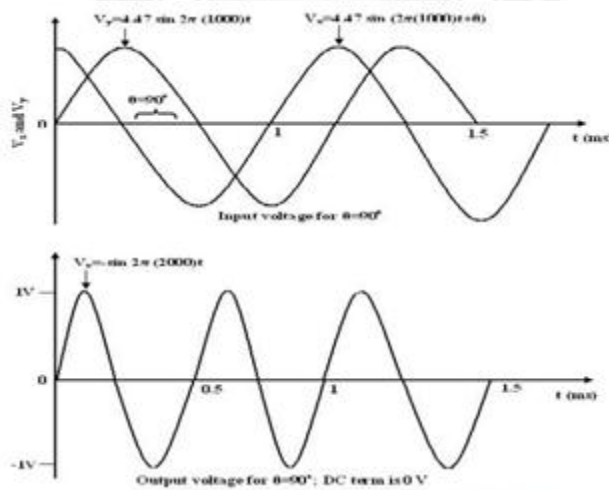


Figure 3.3.7. Input-output waveform

[source: https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/]