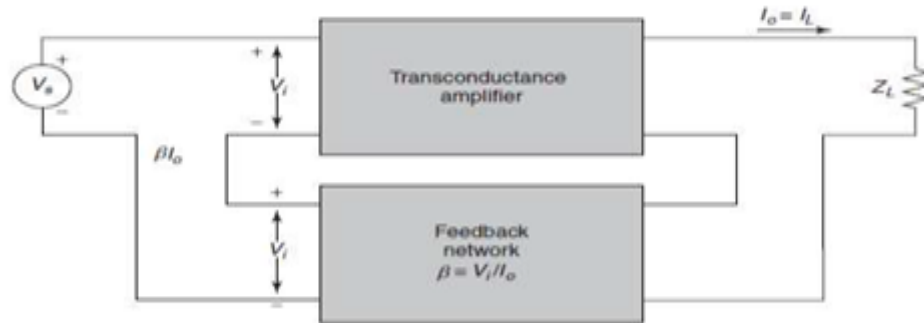


## 1.5 ANALYSIS OF FEEDBACK AMPLIFIER

### CURRENT-SERIES (OR) SERIES-SERIES FEEDBACK AMPLIFIER

- Trans-conductance feedback amplifier provides an output current  $I_o$  which is proportional to the input voltage  $V_s$ . The feedback signal is the voltage  $V_f$ , Here added to  $V_s$  at the input of the amplifier.




**Fig.1.5.1 . Current – Series Amplifier**

(Source: *Microelectronics by J. Millman and A. Grabel, , 2nd ed., Page-240*)

#### Input & Output resistance:

Input resistance:

- Step 1: Draw the equivalent Circuit for Current Series amplifier

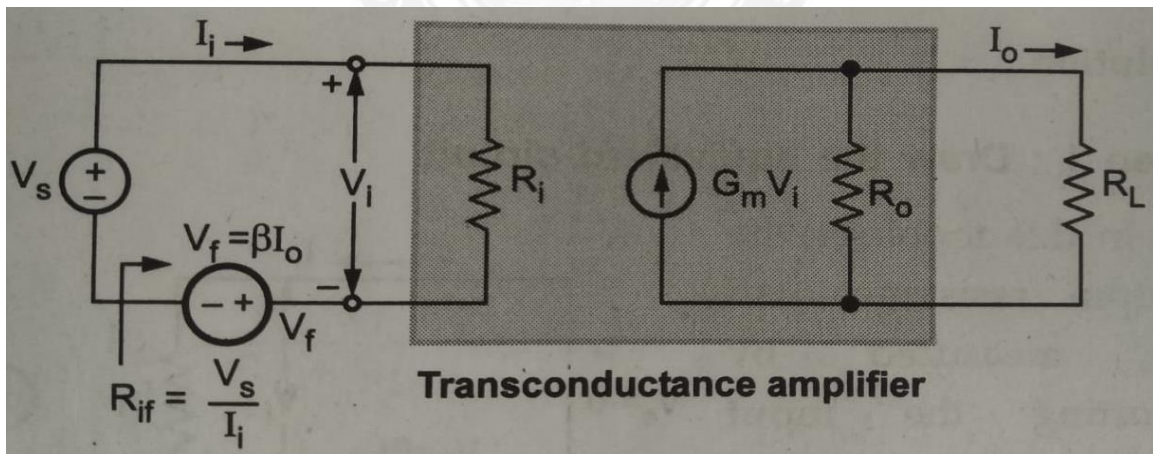

**Fig.1.5.2 . Current – Series Amplifier-input resistance**

(Source: *Microelectronics by J. Millman and A. Grabel, , 2nd ed., Page-240*)

Looking in fig1.5.2 the input resistance with feedback is given  $R_{if} = V_s / I_i$

- Step 2: Obtain expression for  $V_s$

Applying KVL to the input side,

$$V_s - I_i R_i - V_f = 0$$

$$V_s = I_i R_i + V_f = I_i R_i + \beta I_o \quad \text{----- (1)}$$

- Step 3: Obtain expression for  $I_o$  in terms of  $V_i$

Output Current  $I_o$  is given by

$$I_o = G_m V_i R_o / (R_o + R_L)$$

where  $G_M = G_m R_o / (R_o + R_L)$

$$I_o = G_M V_i = G_M I_i R_i \quad \text{----- (2)}$$

$G_m$  is open Circuit Transconductance gain without feedback and  $G_M$  is Transconductance without feedback taking the load  $R_L$  into account

- Step 4: Obtain expression for  $R_{if}$


Sub value of  $I_o$  from eqn (2) in eqn (1)

$$V_s = I_i R_i + \beta G_M I_i R_i = I_i (R_i + \beta G_M R_i)$$

$$R_{if} = V_s / I_i = R_i + \beta G_M R_i$$

Output resistance:

- Step 1: Draw the equivalent Circuit

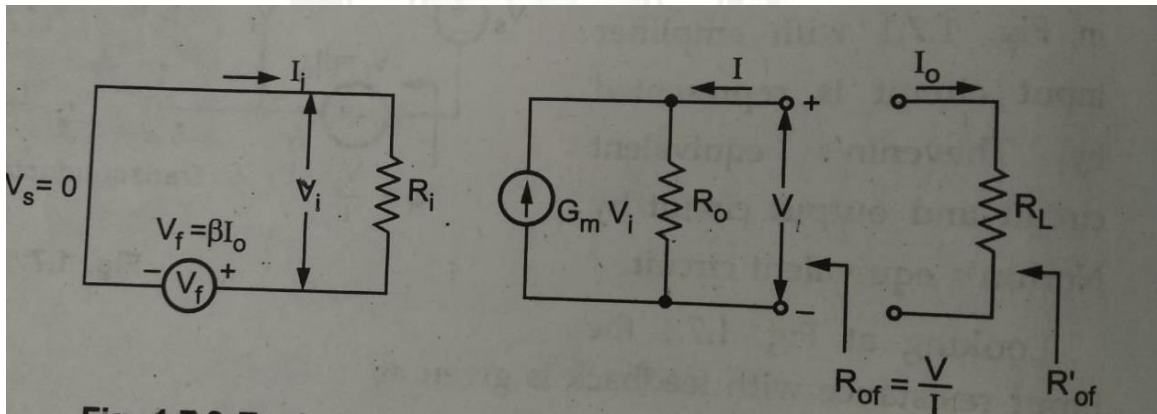

**Fig.1.5.3 . Current – Series Amplifier-output resistance**

(Source: *Microelectronics by J. Millman and A. Grabel, , 2nd ed., Page-241*)

Output resistance can be measured by shorting the input source  $V_s = 0$  and looking into the output terminals with  $R_L$  disconnected

- Step 2: Obtain expression for  $I$  in terms of  $V$

Applying KCL to the output Node,

$$I = (V / R_o) - G_m V_i \quad \text{----- (1)}$$

Input voltage is given by

$$V_i = - V_f = - \beta I_o$$

$$V_i = \beta I \quad \therefore I_o = -I \quad \text{----- (2)}$$

Sub value of  $V_i$  from eqn (2) in eqn (1)

$$I = (V / R_o) - G_m \beta I$$

$$V / R_o = I + G_m \beta I = I (1 + G_m \beta)$$

- Step 3: Obtain expression for  $R_{of}$

$$R_{of} = V / I$$

$$R_{of} = R_o (1 + \beta G_m)$$

- Step 4: Obtain expression for  $R'_{of}$

$$R'_{of} = R_{of} \parallel R_L = R_o R_L / (R_o + R_L + \beta A_v R_L)$$

Dividing num and den by  $(R_o + R_L)$

$$R'_{of} = R'_o (1 + \beta G_m) / (1 + \beta G_M)$$

$$R'_o = R_o R_L / (R_o + R_L)$$


$$G_M = G_m R_o / (R_o + R_L)$$

### Transistorized Analysis of feedback amplifiers:

1. Identify the type of feedback
2. Find input circuit
3. Find output circuit
4. Replace transistor by its h-parameter equivalent circuit.
5. Find open loop voltage gain
6. Indicate  $v_o$  and  $v_f$  and calculate  $\beta$
7. Calculate  $D$ ,  $A_{vf}$ ,  $R_{if}$ ,  $R_{of}$ , and  $R'_{of}$

### VOLTAGE-SHUNT (OR) SHUNT-SHUNT FEEDBACK AMPLIFIER

- The voltage-shunt or shunt-shunt feedback amplifier provides an output voltage  $V_o$  in proportion to the input current  $I_s$ . The input current  $I_i$  of the basic amplifier is the algebraic sum of  $I_s$  and the feedback current  $I_f$ .

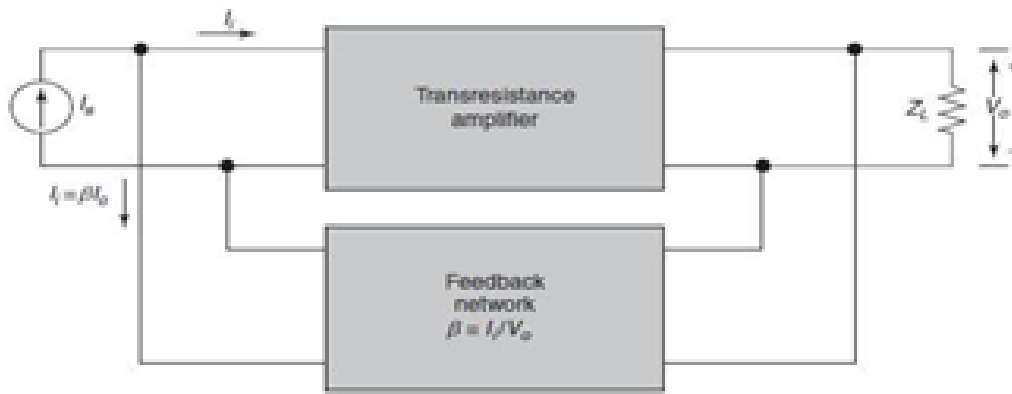


**Fig 1.5.4.Voltage-Shunt Amplifier**

(Source: Microelectronics by J. Millman and A. Grabel, , 2nd ed., Page-252)

### Input Resistance:

- Step 1: Draw the equivalent Circuit for Voltage Shunt amplifier

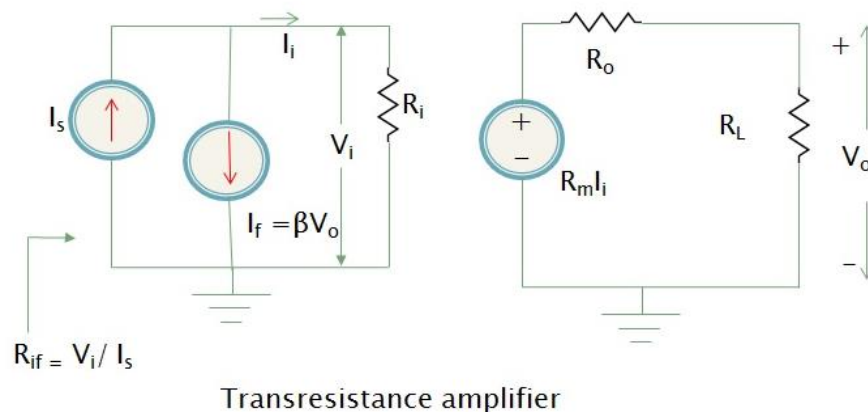

**Fig 1.5.5.Voltage-Shunt Amplifier-input resistance**

(Source: Microelectronics by J. Millman and A. Grabel, , 2nd ed., Page-252)

Looking in fig 1.5.5 the input resistance with feedback is given  $R_{if} = V_i / I_s$

- Step 2: Obtain expression for  $I_s$

Applying KCL to the input node,

$$I_s = I_i + I_f = I_i + \beta V_o \quad \text{----- (1)}$$

Expression for  $V_o$  in terms of  $I_i$

Output Voltage  $V_o$  is given by

$$V_o = R_m I_i R_o / (R_o + R_L)$$

where  $R_M = R_m R_o / (R_o + R_L)$

$$V_o = R_M I_i \quad \text{----- (2)}$$

$R_m$  is open Circuit Transresistance gain without feedback and  $R_M$  is Transresistance without feedback taking the load  $R_L$  into account

- Step 3: Obtain expression for  $R_{if}$


Sub value of  $V_o$  from eqn (2) in eqn (1)

$$I_s = I_i + \beta R_M I_i = I_i (1 + \beta R_M)$$

$$R_{if} = V_i / I_s = V_i / I_i (1 + \beta R_M)$$

### Output resistance:

- Step 1: Draw the equivalent Circuit

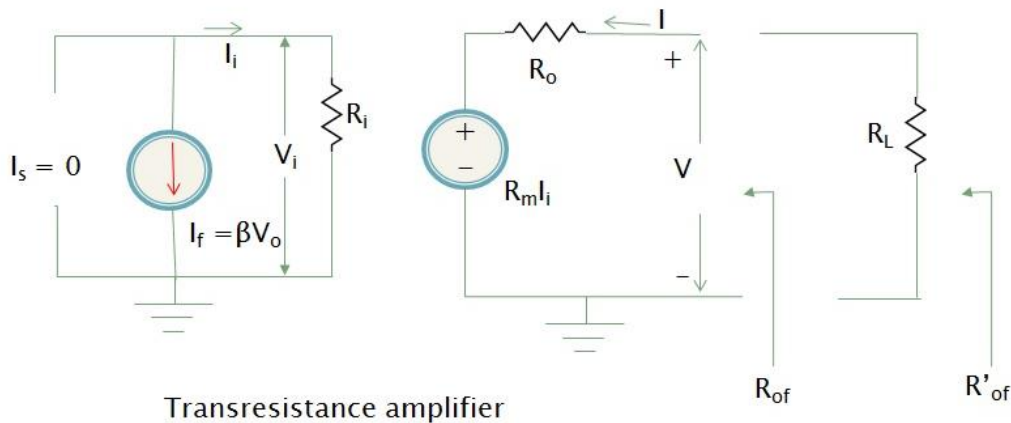

**Fig 1.5.6. Voltage-Shunt Amplifier-output resistance**

(Source: Microelectronics by J. Millman and A. Grabel, 2nd ed., Page-252)

Output resistance can be measured by opening the input source  $I_s = 0$  and looking into the output terminals with  $R_L$  disconnected

- Step 2: Obtain expression for  $I$  in terms of  $V$ ,

Applying KVL to the output Side,

$$R_m I_i + I R_o - V = 0$$

$$I = (V - R_m I_i) / R_o \quad \text{----- (1)}$$

Input Current is given by

$$I_i = - I_f = - \beta V \quad \text{----- (2)}$$

Sub value of  $I_i$  from eqn (2) in eqn (1)

$$I = (V + R_m \beta V) / R_o$$

$$I = V (1 + R_m \beta) / R_o$$

- Step 3: Obtain expression for  $R_{of}$

$$R_{of} = V / I$$

$$R_{of} = R_o / (1 + \beta R_m)$$

- Step 3: Obtain expression for  $R'_{of}$

$$R'_{of} = R_{of} \parallel R_L = R_o R_L / (R_o + R_L (1 + \beta R_m))$$

$$R'_{of} = R'_o (1 + \beta R_m) \quad R'_o = R_{of} R_L / (R_{of} + R_L)$$

Dividing num and denominator by  $(R_o + R_L)$


$$R'_o = R_{of} R_L / (R_{of} + R_L)$$

### Transistorized Analysis of feedback amplifiers:

1. Identify the type of feedback
2. Find input circuit
3. Find output circuit
4. Replace transistor by its h-parameter equivalent circuit.
5. Find open loop voltage gain
6. Indicate  $v_o$  and  $v_f$  and calculate  $\beta$
7. Calculate  $D$ ,  $A_{vf}$ ,  $R_{if}$ ,  $R_{of}$ , and  $R'_{of}$

### SHUNT-SERIES (OR) CURRENT-SHUNT FEEDBACK AMPLIFIER

- The current-shunt feedback amplifier, supplies an output current  $I_o$  which is proportional to the input current  $I_i$ . This makes it a current amplifier.
- The feedback signal is the current if the input current of the basic amplifier is  $I_i = I_s + I_f$  and the output current is  $I_o = I$

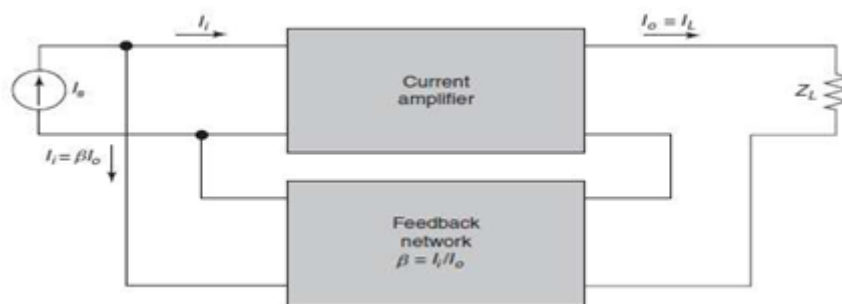


**Fig: 1.5.7 Current -Shunt Amplifier**

(Source: Microelectronics by J. Millman and A. Grabel, , 2nd ed., Page-255)

### Input & Output resistance:

#### Input resistance:

- Step 1: Draw the equivalent Ckt for Voltage Series Shunt amplifier

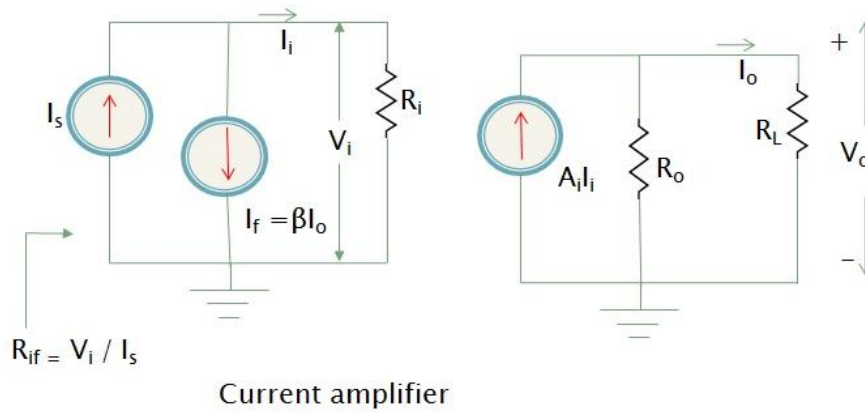

**Fig: 1.5.8 Current -Shunt Amplifier-input resistance**

(Source: *Microelectronics by J. Millman and A. Grabel, 2nd ed., Page-256*)

Looking in fig 1.5.8 the input resistance with feedback is given  $R_{if} = V_i / I_s$

- Step 2: Obtain expression for  $I_s$

Applying KCL to the input node ,

$$I_s = I_i + I_f = I_i + \beta I_o \quad \text{----- (1)}$$

- Step 3: Obtain expression for  $I_o$  in terms of  $I_i$

Output Current  $I_o$  is given by

$$I_o = A_i I_i R_o / (R_o + R_L)$$

$$\text{Where } A_I = A_i R_o / (R_o + R_L)$$

$$I_o = A_I I_i \quad \text{----- (2)}$$

$A_i$  is open Circuit Current gain without feedback and  $A_I$  is Current gain without feedback taking the load  $R_L$  into account

- Step 3: Obtain expression for  $R_{if}$


Sub value of  $I_o$  from eqn (2) in eqn (1)

$$I_s = I_i + \beta A_I I_i = I_i (1 + \beta A_I)$$

$$R_{if} = V_i / I_s = V_i / I_i (1 + \beta A_I)$$

### Output resistance:

- Step 1: Draw the equivalent Ckt

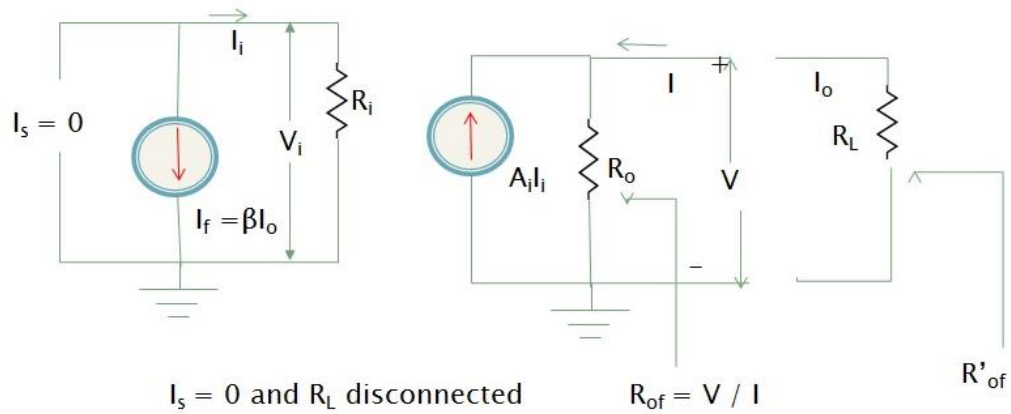

**Fig: 1.5.9 Current -Shunt Amplifier-output resistance**

(Source: *Microelectronics by J. Millman and A. Grabel, 2nd ed., Page-256*)

Output resistance can be measured by shorting the input source  $I_s = 0$  and looking into the output terminals with  $R_L$  disconnected

- Step 2: Obtain expression for  $I$  in terms of  $V$

Applying KCL to the output node,

$$I = (V / R_o) - A_i I_i \quad \text{----- (1)}$$

Input Current is given by

$$I_i = - I_f = - \beta I_o = \beta I \quad \text{----- (2)}$$

Sub value of  $I_i$  from eqn (2) in eqn (1)

$$I = (V / R_o) - A_i \beta I$$

$$V / R_o = I + A_i \beta I = I (1 + \beta A_i)$$

- Step 3: Obtain expression for  $R_{of}$

$$R_{of} = V / I$$

$$R_{of} = R_o (1 + \beta A_i)$$

- Step 4: Obtain expression for  $R'_{of}$

$$R'_{of} = R_{of} \parallel R_L$$

$$R'_{of} = R_o (1 + \beta A_i) / (1 + \beta A_i)$$

Dividing num and den by  $(R_o + R_L)$

$$R'_{of} = R_o R_L / (R_o + R_L)$$

### Transistorized Analysis of feedback amplifiers:

1. Identify the type of feedback
2. Find input circuit



3. Find output circuit
4. Replace transistor by its h-parameter equivalent circuit.
5. Find open loop voltage gain
6. Indicate  $v_o$  and  $v_f$  and calculate  $\beta$
7. Calculate  $D$ ,  $A_{vf}$ ,  $R_{if}$ ,  $R_{of}$ , and  $R'_{of}$

