

UNIT II

PHASE-CONTROLLED CONVERTERS


- 2-pulse,3-pulse and 6-pulseconverters
- Performance parameters
- Effect of source inductance
- Gate Circuit Schemes for Phase Control
- Dual converters.

RECTIFIER

Rectifier are used to convert A.C to D.C supply.

Rectifiers can be classified as single phase rectifier and three phase rectifier. Single phase rectifier are classified as 1- Φ half wave and 1- Φ full wave rectifier. Three phase rectifier are classified as 3- Φ half wave rectifier and 3- Φ full wave rectifier. 1- Φ Full wave rectifier are classified as 1- Φ mid point type and 1- Φ bridge type rectifier. 1- Φ bridge type rectifier are classified as 1- Φ half controlled and 1- Φ full controlled rectifier. 3- Φ full wave rectifier are again classified as 3- Φ mid point type and 3- Φ bridge type rectifier. 3- Φ bridge type rectifier are again divided as 3- Φ half controlled rectifier and 3- Φ full controlled rectifier.

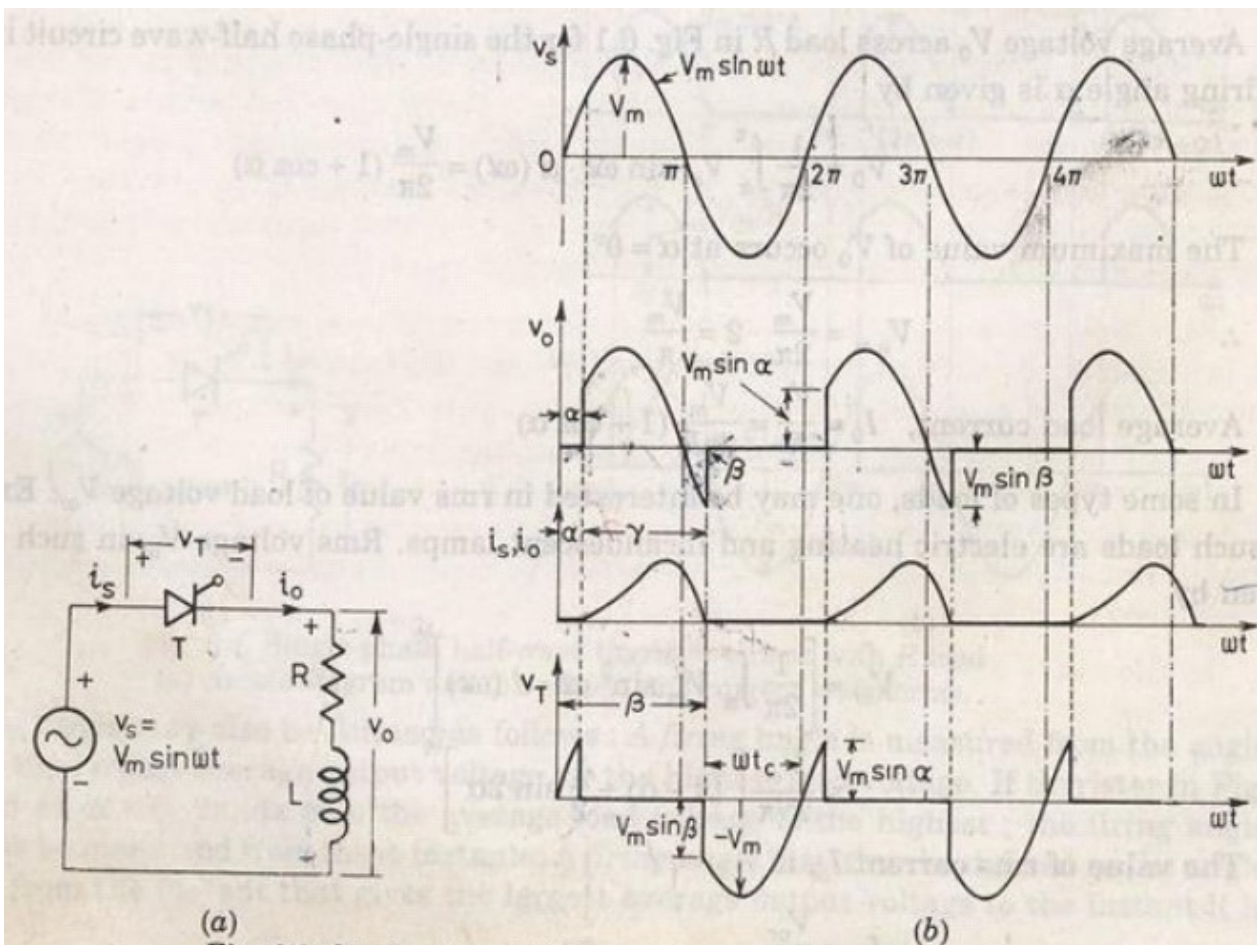Single phase half wave circuit with R-L load



Output current i_o rises gradually. After some time i_o reaches a maximum value and then begins to decrease.

At π , $v_o=0$ but i_o is not zero because of the load inductance L . After π interval SCR is reverse biased but load current is not less than the holding current.

At $\beta > \pi$, i_o reduces to zero and SCR is turned off.

At $2\pi + \beta$ SCR triggers again

α is the firing angle.

β is the extinction angle.

ν conduction angle $\nu = \beta - \alpha$

Analysis for V_T

$$V_m \sin \omega t = Ri_o + L \frac{di_o}{dt}$$

$$i_s = \frac{V_m}{\sqrt{R^2 + X^2}} \sin(\omega t - \phi)$$

Where,

$$\phi = \tan^{-1} \frac{X}{R}$$

$$X = \omega L$$

The transient component can be obtained as

$$Ri_t + L \frac{di_t}{dt} = 0$$

$$\text{So } i_t = Ae^{-(Rt/L)}$$

$$i_o = i_s + i_t$$

Therefore,

$$\omega t = \beta, i_0 = 0;$$

$$\text{So } \sin(\beta - \alpha) = \sin(\alpha - \beta) e^{-(\beta - \alpha)/(\omega L)}$$

β can be obtained from the above equation.

The average load voltage can be given by


$$V_0 = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t)$$

$$\frac{V_m}{2\pi} (\cos(\alpha) - \cos(\beta))$$

Average load current

$$I_0 = \frac{V_m}{2\pi R} (\cos \alpha - \cos \beta)$$


Single phase full converter

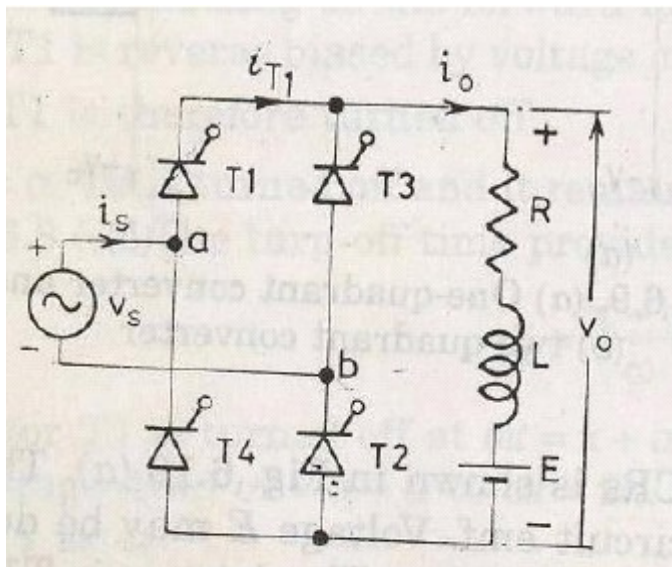


$$V_0 = \frac{1}{\pi} \int_{\alpha}^{\pi+\beta} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{2V_m}{\pi} \cos \alpha$$

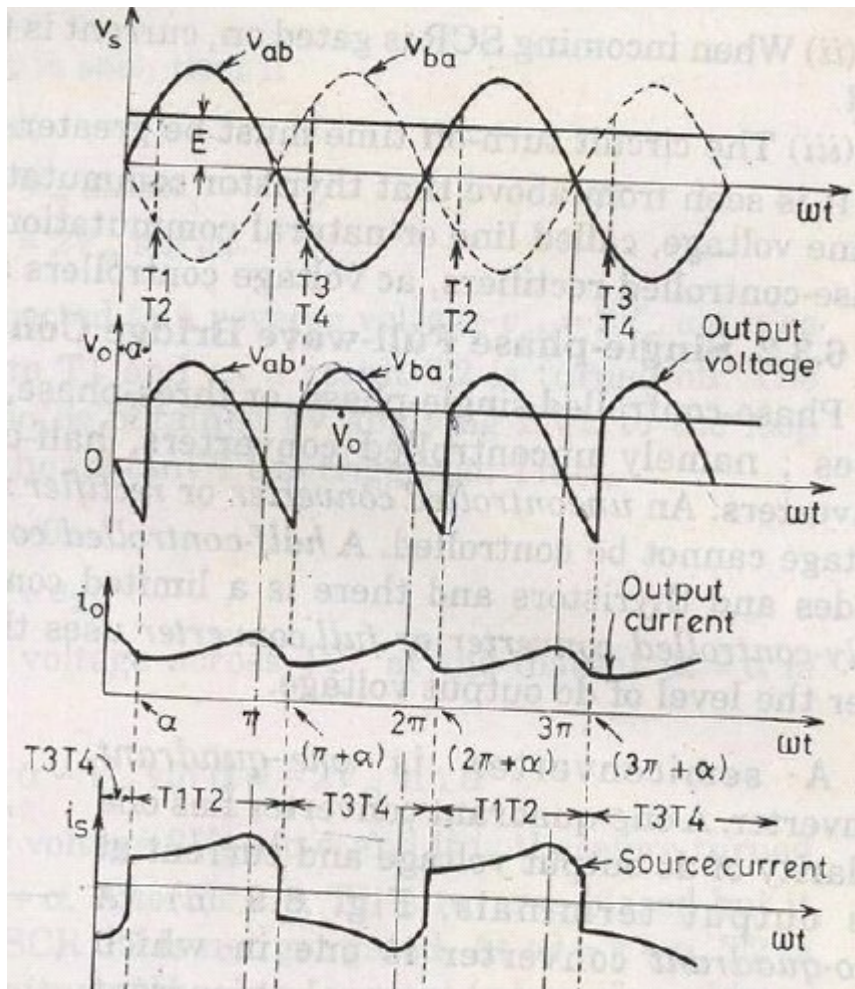T₁, T₂ triggered at α and π radian latter T₃, T₄ are triggered.



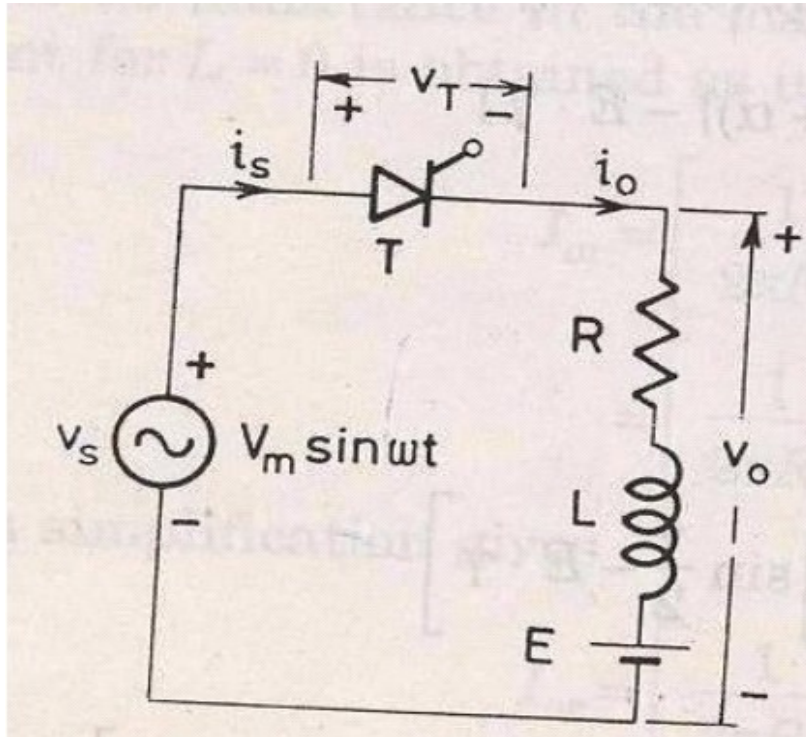Single phase half wave circuit with RLE load



The minimum value of firing angle is

$$V_m \sin(\omega t) = E$$

So,

$$\theta_1 = \sin^{-1} \frac{E}{V_m}$$


Maximum value of firing angle

The voltage differential equation is

$$V_m \sin(\omega t) = R i_o + L \frac{d i_o}{d t} + E$$

Due to source volt
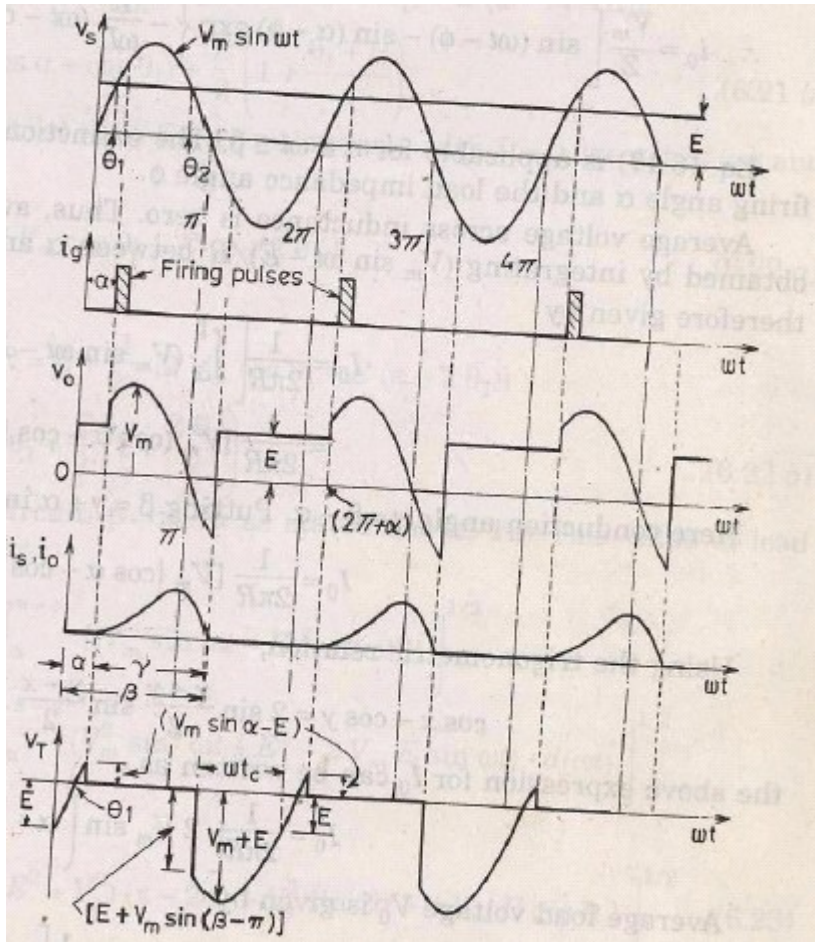
$$i_{s1} = \frac{V_m}{Z} \sin(\omega t - \phi)$$



Due to DC counter emf

$$i_{s2} = -(E / R)$$

$$i_T = Ae^{-(R/L)t}$$

Thus the total current is given by

$$i_0 = \frac{V_m}{Z} [\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\{-\frac{R}{\omega L}(\omega t - \alpha)\}} - \frac{E}{R} [1 - e^{\{-\frac{R}{\omega L}(\omega t - \alpha)\}}]]$$

$$i_{s1} + i_{s2} + i_t$$

$$= \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + Ae^{-(R/L)t}$$

$$i_{s0} = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + Ae^{-(R/L)t}$$

$$\text{At } \omega t = \alpha, i_0 = 0$$

$$A = \left[\frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{-R\alpha/L\omega}$$

Average voltage across the inductance is zero. Average value of load current is

$$I_0 = \frac{1}{2\pi R} \int_{\alpha}^{\beta} (V_m \sin \omega t - E) d(\omega t)$$

$$= \frac{1}{2\pi R} [V_m (\cos \alpha - \cos \beta) - E(\beta - \alpha)]$$

$$\text{Conduction angle } \nu = \beta - \alpha$$

$$\Rightarrow \beta = \alpha + \nu$$

$$I_0 = \frac{1}{2\pi R} [V_m (\cos \alpha - \cos(\alpha + \nu)) - E(\nu)]$$

$$\cos A - \cos B = 2 \sin \frac{A+B}{2} \sin \frac{A-B}{2}$$

So

$$I_0 = \frac{1}{2\pi R} \left[2V_m \sin\left(\alpha + \frac{\nu}{2}\right) \sin \frac{\nu}{2} - E\nu \right]$$

If load inductance L is zero then

$$\begin{aligned}
 v &= E + I_0 R \\
 &= E + \frac{1}{2\pi} [2V_m \sin(\alpha + \frac{v}{2}) \sin \frac{v}{2} - E.v] \\
 &= E(1 - \frac{v}{2\pi}) + [\frac{V_m}{\pi} \sin(\alpha + \frac{v}{2}) \sin \frac{v}{2}]
 \end{aligned}$$

So average current will be

$$I_0 = \frac{1}{2\pi R} [V_m (\cos \alpha - \cos(\pi - \theta_1)) - E(\pi - \theta_1 - \alpha)]$$

$$\text{So } V_0 = E + I_0 R$$

$$= \frac{V_m}{2\pi} (\cos \alpha + \cos \theta_1) + \frac{E}{2} (1 + \frac{\theta_1 + \alpha}{\pi})$$

For no inductance rms value of load current

$$\beta = \theta_2$$

$$\text{And } v = \beta - \alpha = \theta_2 - \alpha$$

$$\text{But } \theta_2 = \pi - \theta_1$$

$$\text{So } \beta = \theta_2 = \pi - \theta_1$$

$$\text{And } v = \pi - \theta_1 - \alpha$$

$$I_0 = \left[\frac{1}{2\pi R^2} \int_{\alpha}^{\pi - \alpha} (V_m \sin(\omega t) - E)^2 d(\omega t) \right]^{1/2}$$

Power delivered to load

$$P = I_{or}^2 R + I_0 E$$

Supply power factor

$$Pf = \frac{I_{or}^2 R + I_0 E}{V_s I_{or}}$$

The three phase fully controlled bridge converter

The three phase fully controlled bridge converter has been probably the most widely used power electronic converter in the medium to high power applications. Three phase circuits are preferable when large power is involved. The controlled rectifier can provide controllable out put dc voltage in a single unit instead of a three phase autotransformer and a diode bridge rectifier. The controlled rectifier is obtained by replacing the diodes of the uncontrolled rectifier with thyristors. Control over the output dc voltage is obtained by controlling the conduction interval of each thyristor. This method is known as phase control and converters are also called “phase controlled converters”. Since thyristors can block voltage in both directions it is possible to reverse the polarity of the output dc voltage and hence feed power back to the ac supply from the dc side. Under such condition the converter is said to be operating in the “inverting mode”. The thyristors in the converter circuit are commutated with the help of the supply voltage in the rectifying mode of operation and are known as “Line commutated converter”. The same circuit while operating in the inverter mode requires load side counter emf. for commutation and are referred to as the “Load commutated inverter”.


In phase controlled rectifiers though the output voltage can be varied continuously the load harmonic voltage increases considerably as the average value goes down. Of course the magnitude of harmonic voltage is lower in three phase converter compared to the single phase circuit. Since the frequency of the harmonic voltage is higher smaller load inductance leads to continuous conduction. Input current wave shape become rectangular and contain 5th and higher order odd harmonics. The

displacement angle of the input current increases with firing angle. The frequency of the harmonic voltage and current can be increased by increasing the pulse number of the converter which can be achieved by series and parallel connection of basic 6 pulse converters. The control circuit become considerably complicated and the use of coupling transformer and / or interphase reactors become mandatory.

With the introduction of high power IGBTs the three phase bridge converter has all but been replaced by dc link voltage source converters in the medium to moderately high power range. However in very high power application (such as HV dc transmission system, cycloconverter drives, load commutated inverter synchronous motor drives, static scherbius drives etc.) the basic B phase bridge converter block is still used. In this lesson the operating principle and characteristic of this very important converter topology will be discussed in source depth.


Operating Principle of 3 phase fully controlled bridge converter

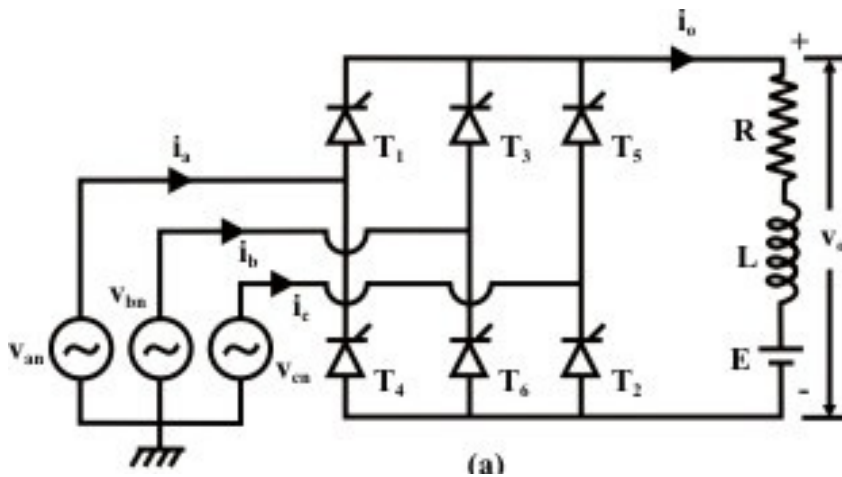A three phase fully controlled converter is obtained by replacing all the six diodes of an uncontrolled converter by six thyristors as shown in Fig. (a)



Device Mode	V_{T1}	V_{T2}	V_{T3}	V_{T4}	V_{T5}	V_{T6}	V_o
T_1T_2	0	0	V_{ba}	V_{ca}	V_{ca}	V_{cb}	V_{ac}
T_2T_3	V_{ab}	0	0	V_{ca}	V_{cb}	V_{cb}	V_{bc}
T_3T_4	V_{ab}	V_{ac}	0	0	V_{cb}	V_{ab}	V_{ba}
T_4T_5	V_{ac}	V_{ac}	V_{bc}	0	0	V_{ab}	V_{ca}
T_5T_6	V_{ac}	V_{bc}	V_{bc}	V_{ba}	0	0	V_{cb}
T_6T_1	0	V_{bc}	V_{ba}	V_{ba}	V_{ca}	0	V_{ab}
NONE	-	-	-	-	-	-	E

(b)

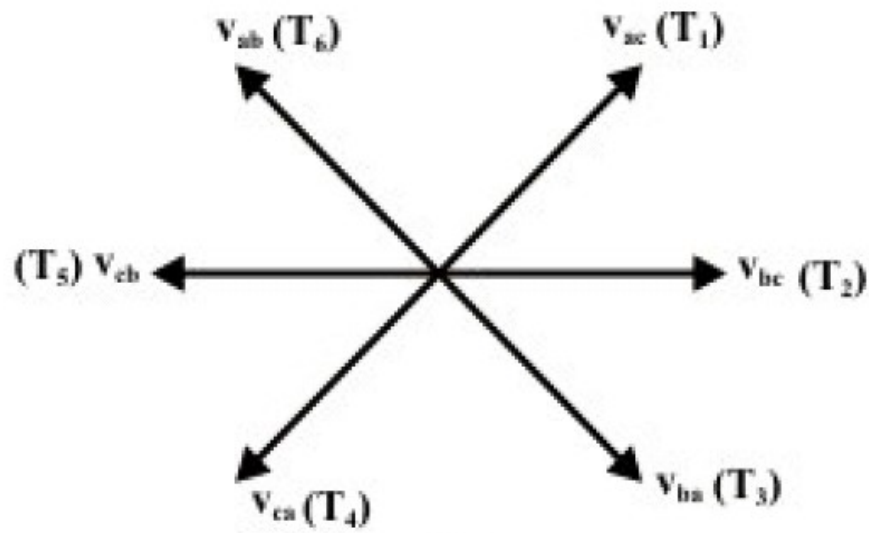

(c)

For any current to flow in the load at least one device from the top group (T_1, T_3, T_5) and one from the bottom group (T_2, T_4, T_6) must conduct. It can be argued as in the case of an uncontrolled converter only one device from these two groups will conduct.


Then from symmetry consideration it can be argued that each thyristor conducts for 120° of the input cycle. Now the thyristors are fired in the sequence $T_1 \rightarrow T_2 \rightarrow T_3 \rightarrow T_4 \rightarrow T_5 \rightarrow T_6 \rightarrow T_1$ with 60° interval between each firing. Therefore thyristors on the same phase leg are fired at an interval of 180° and hence can not conduct simultaneously. This leaves only six possible conduction mode for the converter in the continuous conduction mode of operation. These are $T_1T_2, T_2T_3, T_3T_4, T_4T_5, T_5T_6, T_6T_1$. Each conduction mode is of 60° duration and appears in the sequence mentioned.

The conduction table of Fig. (b) shows voltage across different devices and the dc output voltage for each conduction interval. The phasor diagram of the line voltages appear in Fig.(c). Each of these line voltages can be associated with the firing of a thyristor with the help of the conduction table-1. For example the thyristor T_1 is fired at the end of T_5T_6 conduction interval. During this period the voltage across T_1 was v_{ac} .

Therefore T_1 is fired α angle after the positive going zero crossing of v_{ac} . Similar observation can be made about other thyristors. The phasor diagram of Fig. (c) also confirms that all the thyristors are fired in the correct sequence with 60° interval between each firing.

Fig. shows the waveforms of different variables (shown in Fig. (a)). To arrive at the waveforms it is necessary to draw the conduction diagram which shows the interval of conduction for each thyristor and can be drawn with the help of the phasor diagram of fig. (c). If the converter firing angle is α each thyristor is fired " α " angle after the positive going zero crossing of the line voltage with which it's firing is associated. Once the conduction diagram is drawn all other voltage waveforms can be drawn from the line voltage waveforms and from the conduction table of fig.(b).

Similarly line currents can be drawn from the output current and the conduction diagram. It is clear from the waveforms that output voltage and current waveforms are periodic over one sixth of the input cycle. Therefore this converter is also called the "six pulse" converter. The input current on the other hand contains only odds harmonics of the input frequency other than the triplex ($3^{rd}, 9^{th}$ etc.) harmonics. The next section will analyze the operation of this converter in more details.

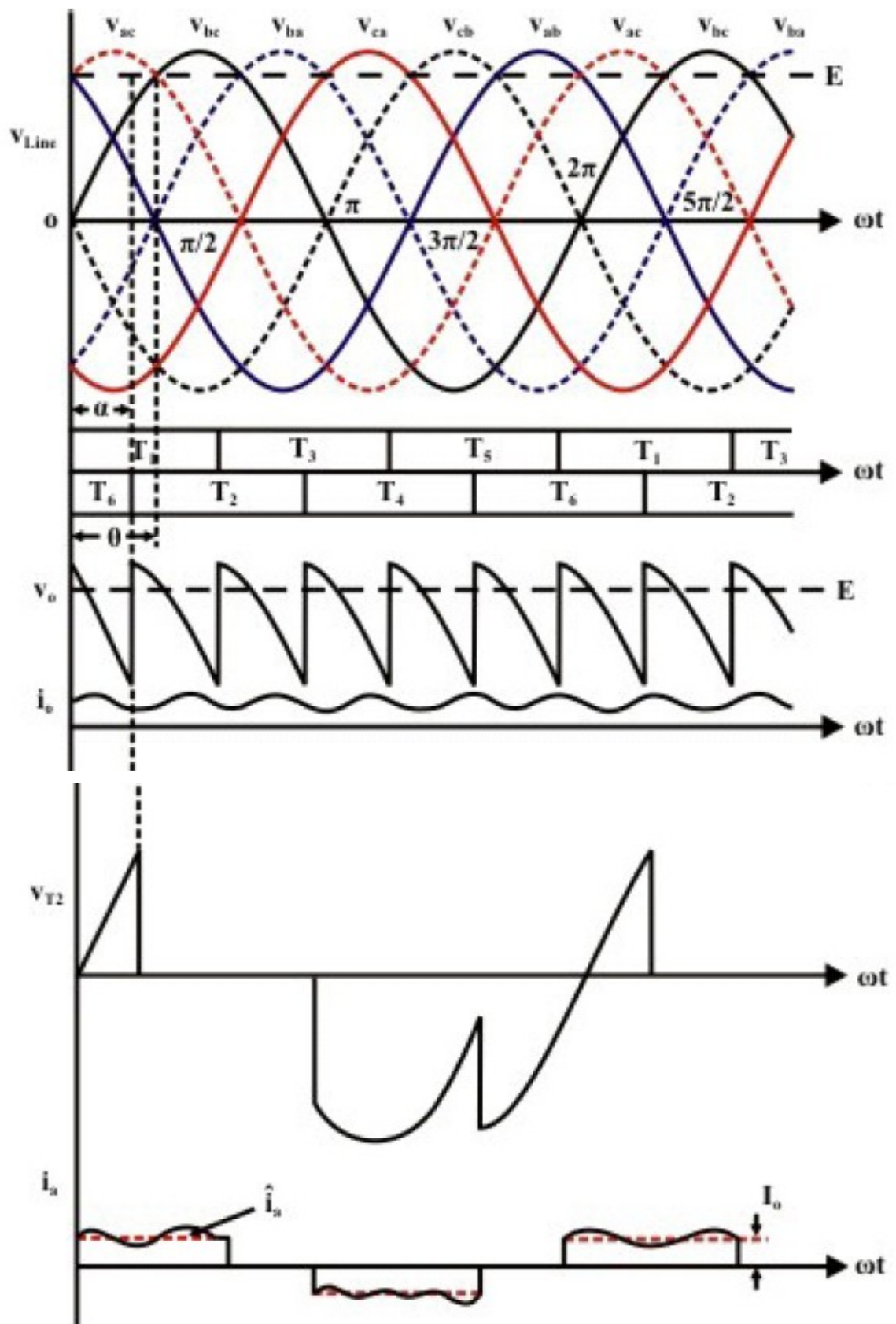

Waveforms of three phase fully controlled converter

Analysis of the converter in the rectifier mode

$$v_0 = V_0 + \sum_{K=1,2}^{\alpha} V_{AK} \cos 6 K \omega t + \sum_{K=1,2}^{\alpha} V_{BK} \sin 6 K \omega t \quad (1)$$

$$\begin{aligned} V_0 &= \frac{3}{\pi} \int_{\alpha}^{\alpha+\frac{\pi}{3}} v_0 d\omega t = \frac{3\sqrt{2}}{\pi} V_L \int_{\alpha}^{\alpha+\frac{\pi}{3}} \sin\left(\omega t + \frac{\pi}{3}\right) d\omega t \\ &= \frac{3\sqrt{2}}{\pi} V_L \cos \alpha \end{aligned} \quad (2)$$

$$\begin{aligned} V_{AK} &= \frac{6}{\pi} \int_{\alpha}^{\alpha+\frac{\pi}{3}} v_0 \cos 6 K \omega t d\omega t \\ &= \frac{6}{\pi} \int_{\alpha}^{\alpha+\frac{\pi}{3}} \sqrt{2} V_L \sin\left(\omega t + \frac{\pi}{3}\right) \cos 6 \omega t d\omega t \\ &= \frac{3\sqrt{2}}{\pi} V_L \left[\frac{\cos(6K+1)\alpha}{6K+1} - \frac{\cos(6K-1)\alpha}{6K-1} \right] \end{aligned} \quad (3)$$

The output voltage waveform can be written as

$$\begin{aligned} V_{BK} &= \frac{6}{\pi} \int_{\alpha}^{\alpha+\frac{\pi}{3}} v_0 \sin 6 K \omega t d\omega t \\ &= \frac{6}{\pi} \int_{\alpha}^{\alpha+\frac{\pi}{3}} \sqrt{2} V_L \sin\left(\omega t + \frac{\pi}{3}\right) \sin 6 \omega t d\omega t \\ &= \frac{3\sqrt{2}}{\pi} V_L \left[\frac{\sin(6K+1)\alpha}{6K+1} - \frac{\sin(6K-1)\alpha}{6K-1} \right] \\ V_{ORMS} &= \sqrt{\frac{3}{\pi} \int_{\alpha}^{\alpha+\frac{\pi}{3}} v_0^2 d\omega t} = V_L \left[1 + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha \right]^{\frac{1}{2}} \end{aligned} \quad (4)$$

The input phase current i_a is expressed as

$$\begin{aligned}
i_a &= i_0 & \alpha \leq \omega t \leq \alpha + \frac{\pi}{3} \\
i_a &= -i_0 & \alpha + \frac{2\pi}{3} \leq \omega t \leq \alpha + \frac{4\pi}{3} \\
i_a &= i_0 & \alpha + \frac{5\pi}{3} \leq \omega t \leq \alpha + 2\pi \\
i_a &= 0 & \text{otherwise}
\end{aligned}$$

From Fig. it can be observed that i_0 itself has a ripple at a frequency six times the input frequency. The closed form expression of i_0 , as will be seen later is some what complicated. However, considerable simplification in the expression of i_a can be obtained if i_0 is replaced by its average value I_0 . This approximation will be valid provided the ripple on i_0 is small, i.e, the load is highly inductive. The modified input current waveform will then be i_a which can be expressed in terms of a fourier series as

$$i_a \approx \hat{i}_a = \frac{I_{A0}}{2} + \sum_{n=1}^{\infty} I_{An} \cos n\omega t + \sum_{n=1}^{\infty} I_{Bn} \sin n\omega t \quad (5)$$

Where

$$I_{A0} = \frac{1}{2\pi} \int_{\alpha}^{\alpha+2\pi} i_a d\omega t = 0 \quad (6)$$

$$\begin{aligned}
I_{An} &= \frac{1}{\pi} \int_{\alpha}^{\alpha+2\pi} i_a \cos n\omega t \quad n \neq 0 \\
&= \frac{4I_0}{n\pi} \cos \frac{n\pi}{6} \sin \frac{n\pi}{2} \cos n\alpha \quad (7)
\end{aligned}$$

$$\begin{aligned}
\therefore I_{An} &= (-1)^K \frac{2\sqrt{3}I_0}{(6K \pm 1)\pi} \sin \left(K\pi \pm \frac{\pi}{2} \right) \cos(6K \pm 1)\alpha \\
&\text{for } n = 6K \pm 1, K = 0, 1, 2, 3 \dots \quad (8)
\end{aligned}$$

$I_{An} = 0$ otherwise.

$$\begin{aligned}
I_{Bn} &= \frac{1}{\pi} \int_{\alpha}^{\alpha+2\pi} i_s \sin n\omega t \, d\omega t \\
&= \frac{4I_0}{n\pi} \cos \frac{n\pi}{6} \sin n\alpha \sin \frac{n\pi}{2}
\end{aligned} \quad (9)$$

$$\begin{aligned}
\therefore I_{Bn} &= (-1)^K \frac{2\sqrt{3}I_0}{(6K \pm 1)\pi} \sin\left(K\pi \pm \frac{\pi}{2}\right) \sin(6K \pm 1)\alpha \\
&\quad \text{for } n = 6K \pm 1, K = 0, 1, 2, \dots
\end{aligned} \quad (10)$$

$$I_{Bn} = 0 \quad \text{otherwise.}$$

$$\therefore i_s = \sum_{k=0}^{\infty} \frac{(-1)^K 2\sqrt{3}I_0}{(6K \pm 1)\pi} \sin\left(K\pi \pm \frac{\pi}{2}\right) \cos[(6K \pm 1)(\omega t - \alpha)] \quad (11)$$

in particular i_{s1} = fundamental component of i_s

$$= \frac{2\sqrt{3}}{\pi} I_0 \cos(\omega t - \alpha) \quad (12)$$

$$\text{From Fig.} \quad v_m = \frac{\sqrt{2}V_L}{\sqrt{3}} \cos \omega t \quad (13)$$

$$\therefore \text{ displacement angle } \phi = \alpha \quad \therefore \text{ displacement factor} = \cos \alpha \quad (14)$$

$$\text{distortion factor} = \frac{I_{s1}}{I_s} = \left(\frac{\sqrt{6}}{\pi}\right)^{I_0} / \sqrt{\frac{2}{3}} I_0 = \frac{3}{\pi} \quad (15)$$

$$\therefore \text{ Power factor} = \text{Displacement factor} \times \text{Distortion factor} = \frac{3}{\pi} \cos \alpha \quad (16)$$

The closed form expression for i_0 in the interval

$$\alpha \leq \omega t \leq \alpha + \frac{\pi}{3}$$

in this interval

$$Ri_0 + L \frac{di_0}{dt} + E = v_0 = \sqrt{2}V_L \sin\left(\omega t + \frac{\pi}{3}\right) \quad (17)$$

$$i_0 = I_1 e^{\frac{(\omega t - \alpha)}{\tan\phi}} + \frac{\sqrt{2}V_L}{Z} \sin\left(\omega t + \frac{\pi}{3} - \phi\right) - \frac{E}{R} \quad (18)$$

Where $Z = \sqrt{R^2 + \omega^2 L^2}$, $\tan\phi = \frac{\omega L}{R}$

$$\therefore R = Z \cos\phi, E = \sqrt{2}V_L \sin\theta \quad (\text{from Fig. 13.2}) \quad (19)$$

$$\therefore i_0 = I_1 e^{\frac{(\omega t - \alpha)}{\tan\phi}} + \frac{\sqrt{2}V_L}{Z} \left[\sin\left(\omega t + \frac{\pi}{3} - \phi\right) - \frac{\sin\theta}{\cos\phi} \right] \quad (20)$$

Since i_0 is periodic over $\pi/3$

$$i_0|_{\omega t = \alpha} = i_0|_{\omega t = \alpha + \frac{\pi}{3}} \quad (21)$$

$$\begin{aligned} \therefore I_1 + \frac{\sqrt{2}V_L}{Z} \left[\sin\left(\alpha + \frac{\pi}{3} - \phi\right) - \frac{\sin\theta}{\cos\phi} \right] \\ = I_1 e^{\frac{\pi}{3\tan\phi}} + \frac{\sqrt{2}V_L}{Z} \left[\sin\left(\alpha + \frac{2\pi}{3} - \phi\right) - \frac{\sin\theta}{\cos\phi} \right] \end{aligned}$$

OR $I_1 = \frac{\sqrt{2}V_L}{Z} \frac{\sin(\phi - \alpha)}{1 - e^{\frac{\pi}{3\tan\phi}}} \quad (22)$

$$\therefore i_0 = \frac{\sqrt{2}V_L}{Z} \left[\frac{\sin(\phi - \alpha)}{1 - e^{\frac{\pi}{3\tan\phi}}} e^{\frac{(\omega t - \alpha)}{\tan\phi}} + \sin\left(\omega t + \frac{\pi}{3} - \phi\right) - \frac{\sin\theta}{\cos\phi} \right] \quad (23)$$

To find out the condition for continuous conduction it is noted that in the limiting case of continuous conduction.

$$i_0|_{\min=0}, \quad \text{Now if } \theta \leq \alpha + \frac{\pi}{3} \text{ then } i_0 \text{ is minimum at } \omega t = \alpha. \quad \therefore \text{Condition}$$

for continuous conduction is $i_0|_{\omega t = \alpha} \geq 0$. However discontinuous conduction is rare in these conversions and will not be discussed any further.

Exercise

1. A three phase fully controlled bridge converter operating from a 3 phase 220 V, 50 Hz supply is used to charge a battery bank with nominal voltage of 240 V. The battery bank has an internal resistance of 0.01Ω and the battery bank voltage varies by $\pm 10\%$ around its nominal value between fully charged and uncharged condition. Assuming continuous conduction find out.

- (i) The range of firing angle of the converter.
- (ii) The range of ac input power factor.
- (iii) The range of charging efficiency.

When the battery bank is charged with a constant average charging current of 100 Amps through a 250 mH lossless inductor.

Answer: The maximum and minimum battery voltages are,

$$V_{B \text{ Min}} = 0.9 \times V_{B \text{ Nom}} = 216 \text{ volts and}$$

$$V_{B \text{ Max}} = 1.1 \times V_{B \text{ Nom}} = 264 \text{ volts respectively.}$$

Since the average charging current is constant at 100 A.

$$V_{0 \text{ Max}} = V_{B \text{ Max}} + 100 \times R_B = 264 + 100 \times 0.01 = 265 \text{ volts}$$

$$V_{0 \text{ Min}} = V_{B \text{ Min}} + 100 \times R_B = 216 + 100 \times 0.01 = 217 \text{ volts.}$$

$$(i) \text{ But } V_{0 \text{ Max}} = V_{0 \text{ Min}} \cos \alpha \therefore \alpha_{\text{Min}} = 26.88^\circ$$

$$V_{0 \text{ Min}} = V_{0 \text{ Max}} \cos \alpha \therefore \alpha_{\text{Max}} = 43.08^\circ$$

- (ii) Input power factor is maximum at minimum α and vice versa

$$\therefore \text{p.f. max} = \text{Distortion factor} \times \text{Displacement factor} \Big|_{\text{Max}} = \frac{3}{\pi} \times \cos \alpha_{\text{min}} = 0.85$$

$$\text{p.f. Min} = \frac{3}{\pi} \times \cos \alpha_{\text{Max}} = 0.697$$

(iii) Power loss during charging = $I_{\text{ORMs}}^2 R_B$

But $I_{\text{ORMs}}^2 = I_0^2 + I_1^2 + I_2^2 + \dots$ and $I_K \approx \frac{V_K}{6K\omega L} = \frac{\sqrt{V_{AK}^2 + V_{BK}^2}}{6\sqrt{2}K\omega L}$

For $\alpha = \alpha_{\text{Min}}$

$$V_{A1} = 0.439 \text{ V}, \quad V_{B1} = 48.48 \text{ V}, \quad I_1 = 0.073 \text{ Amps}$$

$$V_{A2} = 10.76, \quad V_{B2} = 20.15 \text{ V}, \quad I_2 = 0.017 \text{ Amps.}$$

$$\therefore J_{\text{ORMs}}^2 \approx 100^2 + (0.073)^2 + (0.017)^2 = 10000.00562$$

$$\therefore P_{\text{loss}} = 100 \text{ watts.}$$

$$\text{At } \alpha_{\text{Min}}, \quad P_0 = I_0 \times V_{B \text{ Max}} = 26400 \text{ watts.}$$

$$\therefore \text{Charging efficiency} = \frac{26400}{26400 + 100} = 99.6\%$$

Similarly for $\alpha_{\text{Max}}, \quad I_{\text{ORMs}}^2 \approx I_0^2$

$$\therefore P_{\text{loss}} = 100 \text{ watts}$$

$$P_0 = I_0 \times V_{B \text{ Min}} = 21600 \text{ watts.}$$

$$\therefore \text{Charging efficiency} = \frac{21600}{21600 + 100} = 99.54\%$$

2. A three phase fully controlled converter operates from a 3 phase 230 V, 50 Hz supply through a Y/ Δ transformer to supply a 220 V, 600 rpm, 500 A separately excited dc motor. The motor has an armature resistance of 0.02 Ω . What should be the transformer turns ratio such that the converter produces rated motor terminal voltage at 0° firing angle. Assume continuous conduction. The same converter is now used to brake the motor regeneratively in the reverse direction. If the thyristors are to be provided with a minimum turn off time of 100 μs , what is the maximum reverse speed at which rated braking torque can be produced.

Answer: From the given question

$$L32V=220\pi \therefore V_L = 162.9 \text{ V}$$

Where V_L is the secondary side line and also the phase voltage since the secondary side is Δ connected.

$$\text{Primary side phase voltage} = \frac{230}{\sqrt{3}} \text{ V} = 132.79 \text{ V}$$

$$\therefore \text{Turns ratio} = \frac{132.79}{162.9} = 1:1.2267.$$

During regenerative braking in the reverse direction the converter operates in the inverting mode.

$$tq|_{\text{Min}} = 100\mu\text{S} \quad \therefore \quad \beta_{\text{Min}} = \omega tq|_{\text{Min}} = 1.8^\circ$$

$$\therefore \alpha_{\text{Max}} = 180 - \beta_{\text{Min}} = 178.2^\circ$$

\therefore Maximum negative voltage that can be generated by the converter is

$$\frac{3\sqrt{2}}{\pi} V_L \cos 178.2^\circ = -219.89 \text{ V}$$

For rated braking torque $I_a = 500 \text{ A}$

$$\therefore E_b = V_a - I_a r_a = -229.89 \text{ V}.$$

At 600 RPM $E_b = 220 - 500 \times 0.02 = 210 \text{ V}.$

$$\therefore \text{Max reverse speed is } \frac{229.89}{210} \times 600 = 656.83 \text{ RPM}.$$

Higher pulse number converters and dual converter:

The three phase fully controlled converter is widely used in the medium to moderately high power applications. However in very large power applications (such as HV DC transmission systems) the device ratings become impractically large. Also the relatively low frequency (6th in the dc side, 5th and 7th in the ac side) harmonic voltages and currents produced by this converter become unacceptable. Therefore several such converters are connected in series parallel combination in order to increase the voltage / current rating of the resulting converter. Furthermore if the component converters are controlled properly some lower order harmonics can be eliminated both from the input and output resulting in a higher pulse converter.

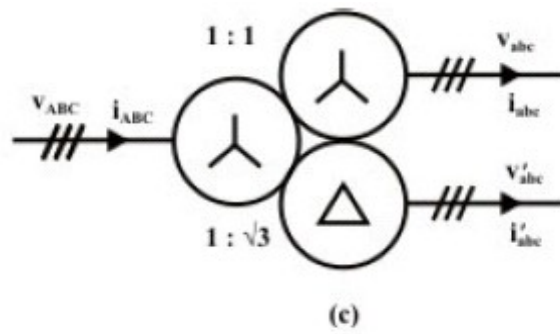
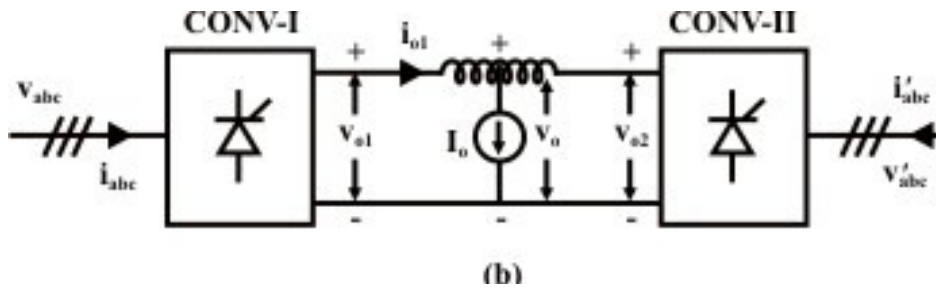
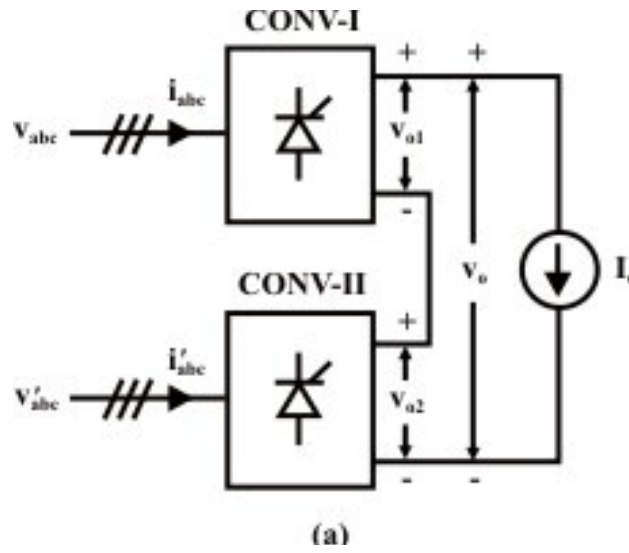


Fig. : Series and parallel connection of 6 phase converters
 (a) Series connection,
 (b) parallel connection,
 (c) Transformer connection.

Fig. (a) schematically represents series connection of two six pulse converters where as Fig. (b) can be considered to be a parallel connection. The inductance in between the converters has been included to limit circulating harmonic current. In both these figures CONV – I and CONV – II have identical construction and are also fired at the same firing angle α . Their input supplies also have same magnitude but displaced in phase by an angle ϕ . Then one can write

$$v_{o1} = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha + \sum_{K=1}^{\infty} V_{AK} \cos 6K\omega t + \sum_{K=1}^{\infty} V_{BK} \sin 6K\omega t$$

$$v_{o2} = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha + \sum_{K=1}^{\infty} V_{AK} \cos 6K(\omega t - \phi) + \sum_{K=1}^{\infty} V_{BK} \sin 6K(\omega t - \phi)$$

Therefore for Fig 13.4(a)

$$v_o = v_{o1} + v_{o2} = \frac{6\sqrt{2}}{\pi} V_L \cos\alpha + 2 \sum_{K=1}^{\infty} \cos 3K\phi [V_{AK} \cos 3K(2\omega t - \phi) + V_{BK} \sin 3K(2\omega t - \phi)]$$

Now if $\cos 3K\phi = 0$ for some K then the corresponding harmonic disappear from the fourier series expression of v_o .

In particular if $\phi = 30^\circ$ then $\cos 3K\phi = 0$ for $K = 1, 2, 3, 5, \dots$

This phase difference can be obtained by the arrangement shown in Fig. (c).

Then

$$v_o = \frac{6\sqrt{2}}{\pi} V_L \cos\alpha + 2 \sum_{m=1}^{\infty} [V_{Am} \cos 12m\omega t + V_{Bm} \sin 12m\omega t]$$

It can be seen that the frequency of the harmonics present in the output voltage has the form $12\omega, 24\omega, 36\omega, \dots$

Similarly it can be shown that the input side line current i_{ABC} have harmonic



frequency of the form

$11\omega, 13\omega, 23\omega, 25\omega, 35\omega, 37\omega, \dots$

Which is the characteristic of a 12 pulse converter.

In a similar manner more number of 3 phase 6 pulse converters can be connected in series / parallel and the ϕ angle can be adjusted to obtain 18 and 24 pulse converters.

One of the shortcomings of a three phase fully controlled converter is that although it can produce both positive and negative voltage it can not supply current in both directions. However, some applications such as a four quadrant dc motor drive require this capability from the dc source. This problem is easily mitigated by connecting another three phase fully controlled converter in anti parallel as shown in Fig. 13.5 (a). In this figure converter-I supplies positive load current while converter-II supplies negative load current. In other words converter-I operates in the first and fourth quadrant of the output $v - i$ plane whereas converter-II operates in the third and fourth quadrant. Thus the two converters taken together can operate in all four quadrants and is capable of supplying a four quadrant dc motor drive. The combined converter is called the Dual converter.

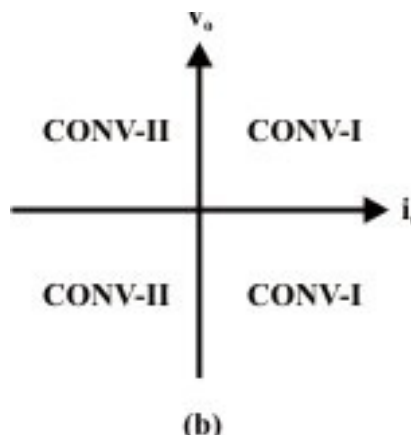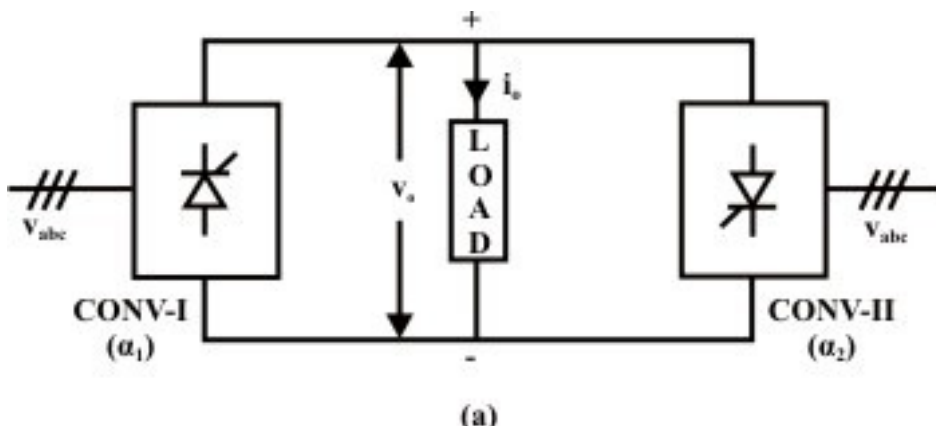

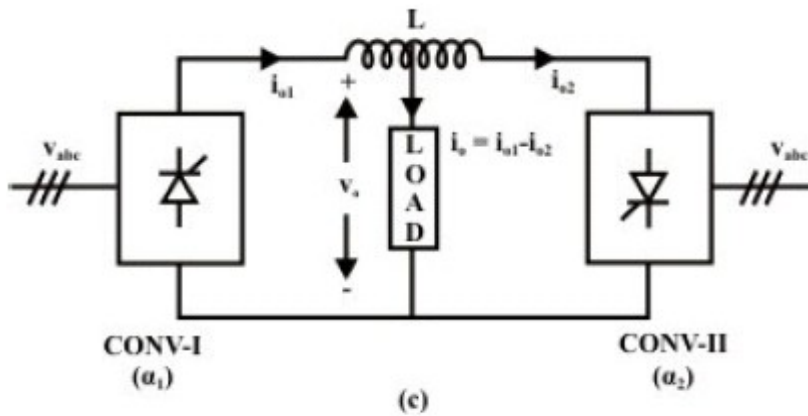


Fig. : Dual converter circuits
 (a) non circulating type
 (b) output V-I plane
 (c) circulating current type

Obviously since converter-I and converter-II are connected in antiparallel they must produce the same dc voltage. This requires that the firing angles of these two converters be related as

$$\alpha_2 = \pi - \alpha_1 \quad (13.30)$$

Although Equation 13.30 ensures that the dc voltages produced by these converters are equal the output voltages do not match on an instantaneous basis. Therefore to avoid a direct short circuit between two different supply lines the two converters must never be gated simultaneously. Converter-I receives gate pulses when the load current is positive. Gate pulses to converter-II are blocked at that time. For negative load current converter-II thyristors are fired while converter-I gate pulses are blocked. Thus there is no circulating current flowing through the converters and therefore it is called the non-circulating current type dual converter. It requires precise sensing of the zero crossing of the output current which may pose a problem particularly at light load due to possible discontinuous conduction. To overcome this problem an interphase reactor may be incorporated between the two converters. With the interphase reactor in place both the converters can be gated simultaneously with $\alpha_2 = \pi - \alpha_1$. The resulting converter is called the circulating current type dual converter.

Gate Drive circuit for three phase fully controlled converter



Several schemes exist to generate gate drive pulses for single phase or three phase converters. In many application it is required that the output of the converter be proportional to a control voltage. This can be achieved as follows.

In either single or three phase converters

$$V_o \propto \cos \alpha \quad \text{or} \quad \alpha = \cos^{-1} V_o / V_i$$

$$V_o \propto v_c \quad \alpha = \cos^{-1} v_c / V_i$$

The following circuit can be used to generate “ α ” according to equation

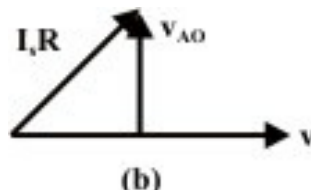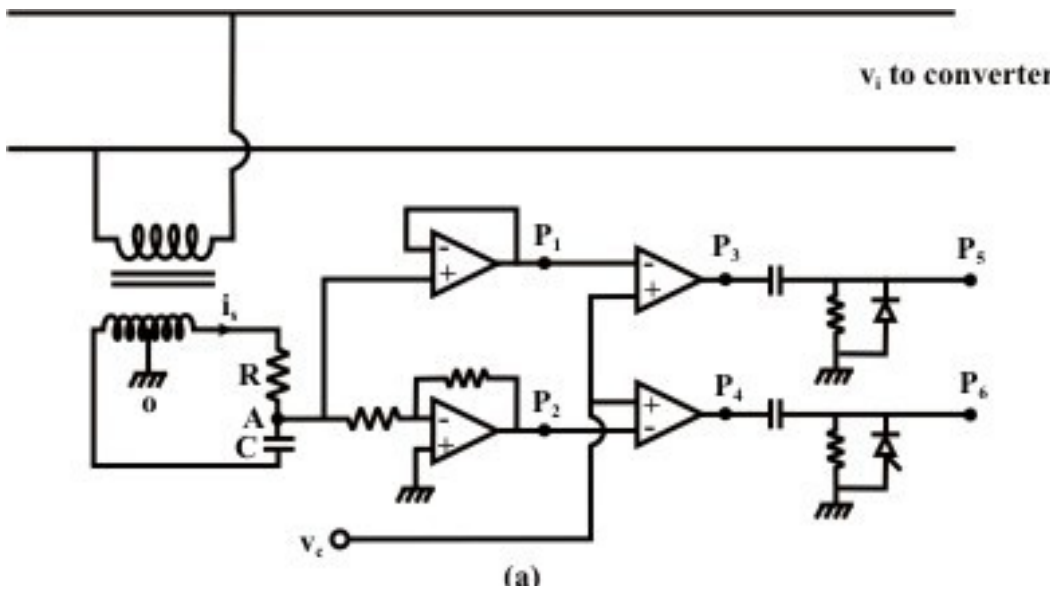


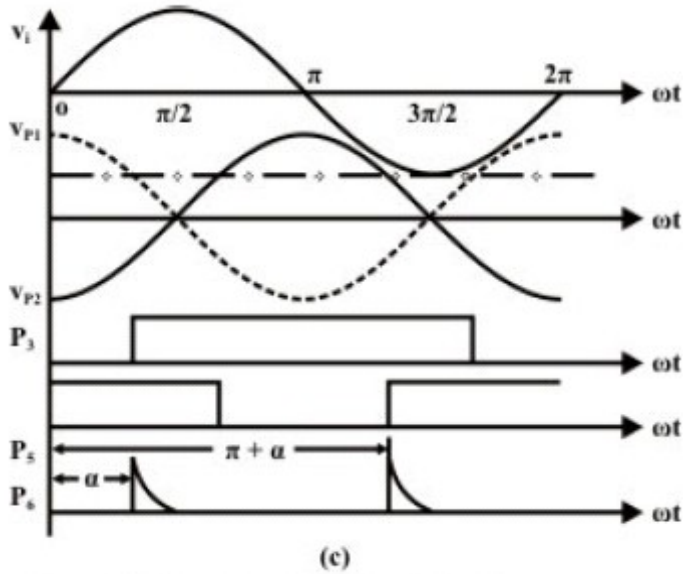
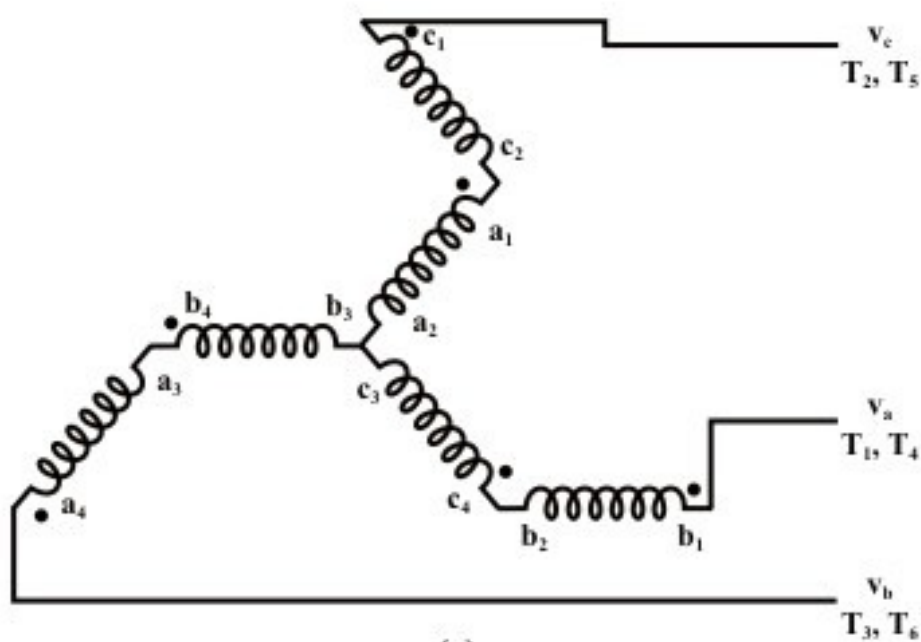


Fig. Triggering circuit for single phase converter
 (a) circuit diagram
 (b) phasor diagram
 (c) waveforms

In the circuit of Fig. (a) a phase shift network is used to obtain a waveform leading v_i by 90° . The phasor diagram of the phase shift circuit is shown in Fig. (b). The output of the phase shift waveform (and its inverse) is compared with v_c . The firing pulse is generated at the point when these two waveforms are equal. Obviously at this instant

$$v_c \propto V_i \cos \alpha \quad \text{or} \quad \alpha = \cos^{-1} v_c / V_i$$

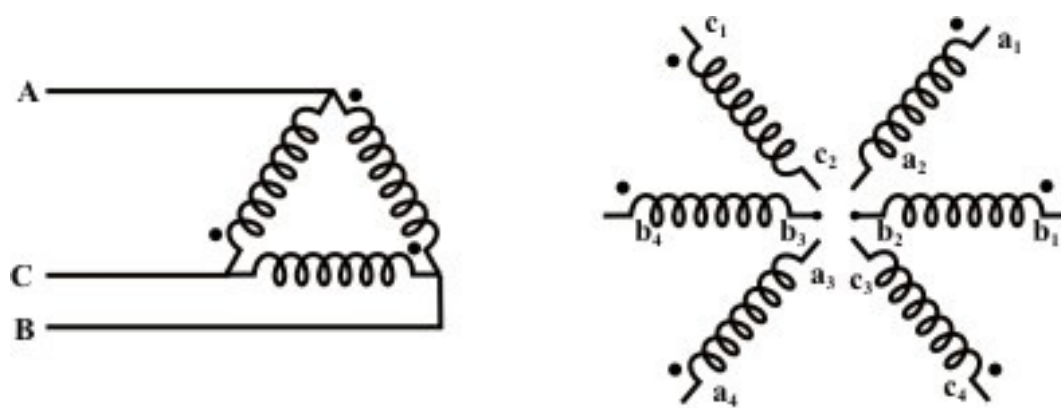Therefore this method of generation of converter firing pulses is called “inverse cosine” control. The output of the phase shift network is called carrier waveform. Similar technique can be used for three phase converters. However the phase shift network here consists of a three phase signal transformer with special connections as shown in Fig.



(a)

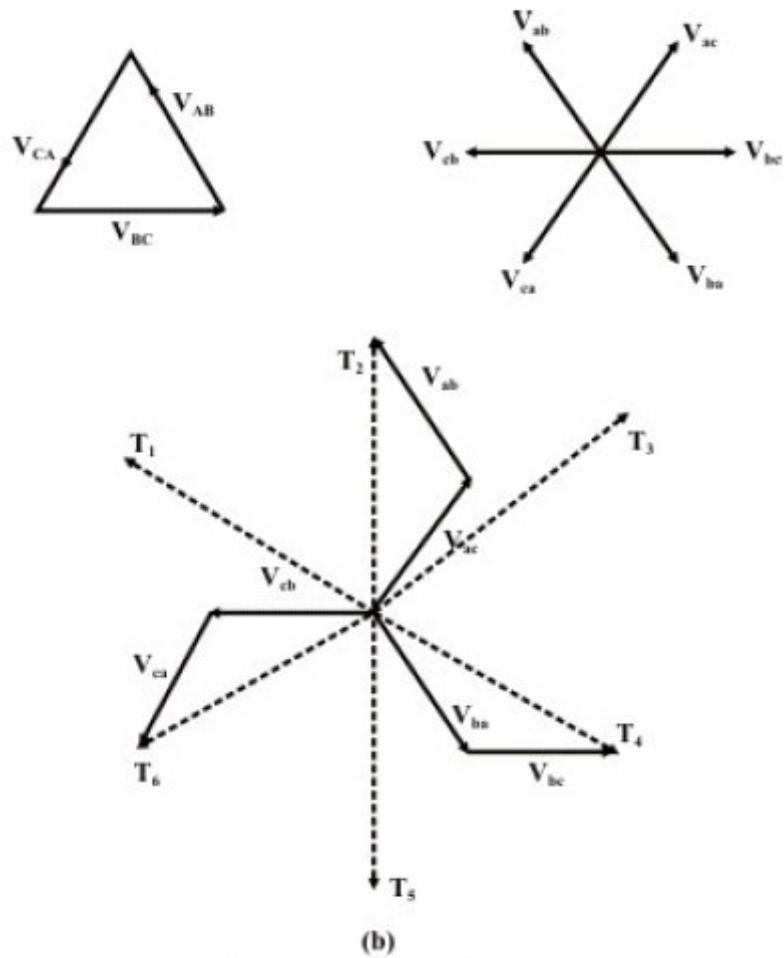


Fig. 1 : Carrier wave generation three phase converters
 (a) Transformer connection
 (b) phasor diagram.

The signal transformer uses three single phase transformer each of which has two secondary windings. The primary windings are connected in delta while the secondary windings are connected in zigzag. From Fig. (c) T_2 is fired α angle after the positive going zero crossing of v_{bc} . Therefore, to implement inverse cosine the carrier wave for T_2 must lead v_{bc} by 90° . This waveform is obtained from zigzag connection of the winding segments a_1a_2 and c_1c_2 as shown in Fig. (a). The same figure also shows the zigzag connection for other phase. The voltage across each zigzag phase can be used to fire two thyristors belonging to the same phase leg using a circuit similar to Fig. (a). The phase shift network will not be required in this case.